

RADIO

ESTABLISHED 1917



Radio, Sound
and Electronics

★
July, 1942

NUMBER 170

25¢ IN U.S.A.

Why doesn't somebody
tell me these things?



is an ideal source for
transformers to specifications

With improvements in materials, structural design, and production methods, UTC is producing, today, transformers which even a year ago would have been considered impossible. As a typical example of such development is a transformer recently supplied to a customer for *one cycle operation* having the following characteristics:

- Primary impedance 10 ohms.
- Secondary inductance 250,000 Hys.
- Impedance ratio 75,000 : 1.
- Self-resonant point above 7 cycles.
- Weight under 8 pounds.

In addition to these difficult characteristics, this unit operates at—160 DB signal level and hum shielding was developed to provide negligible hum pick-up to signal ratio.

MAY WE ASSIST YOU IN YOUR PROBLEM?

The same design experience and engineering ingenuity shown in the above example can be applied to your application. May we have an opportunity to cooperate?

UNITED TRANSFORMER CO.
150 VARICK STREET ★ NEW YORK, N. Y.



Panoramic **RECEPTION!** **THE VISIBLE SPECTRUM OF RADIO FREQUENCIES**

Research and development engineering in the Hallicrafters laboratories goes constantly forward . . . keeping ahead of the fast moving pace of today's defense requirements for communications equipment.

Panoramic reception is only one of the many new developments Hallicrafters will be the first to introduce when short wave equipment is again available for civilian use.

the hallicrafters co.
 CHICAGO, U. S. A.
Keep Communications Open!

Published monthly (and copyrighted 1942) by Editors and Engineers, 404 North Wesley Ave., Mt. Morris, Ill. Send all notices on Form 3578 to Editorial and Executive Offices, 77 Bedford St., Stamford, Conn. Entered as second-class matter, Sept. 26, 1939, at Santa Barbara, Calif., under the Act of March 3, 1879. Additional entry at Mt. Morris, Ill. All rights reserved. Title registered in U. S. Patent Office. Printed in U. S. A.

EDITORIAL

THE REACTIVATION OF AMATEUR RADIO

◀ In view of the restrictions on amateur radio activities, an OEM statement issued on June 11th proved of academic interest only. On that date the Defense Communications Board recommended to the War Production Board and the Federal Communications Commission that, with regard to the construction of certain radio facilities, there be immediately placed into effect the following policy:

1) No future authorizations involving the use of any materials shall be issued by the Federal Communications Commission nor shall further materials be allocated by the War Production Board, to construct or to change the transmitting facilities of any Amateur or Class 3 Experimental Station.

2) No future authorizations involving the use of any materials shall be issued by the Federal Communications Commission nor shall further materials be allocated by the War Production Board, to construct or to change the transmitting facilities of any Aeronautical Fixed (domestic) Station, Itinerant Aircraft Station, Flying School Station, or station operating in the *Emergency* and Miscellaneous Radio Services; provided, however, that upon proper showing that any such station serves as essential military need or a *vital public need*, which cannot otherwise be met, the Commission and the War Production Board will take action commensurate with the importance of the particular facility in question.

But the foregoing takes on practical interest in view of a joint release by the ODC and FCC on June 13th, with regard to war emergency radio service for civilian defense units. Under authority granted in Order No. 9 of the Defense Communications Board, the two agencies are collaborating their activities relative to proposed emergency civilian defense radio systems to be available in the event air raids damage or destroy other means of communication, the two-way radio systems to be operated by


civilian radio technicians, including radio amateurs.

Thousands of compact radio stations to be constructed and operated under prescribed restrictions largely by persons who have had amateur radio experience are expected to augment the services of the OCD organizations throughout the nation. It is anticipated that the two-way stations will be constructed of parts amateurs and others now have on hand. The transmitters will use not more than 25 watts input power, and operate on assigned frequencies above 112 megacycles. Provision has been made for testing during blackouts and other mobilization trials. Printed manuals designed to facilitate administrative operation will be distributed by the OCD, through its regional offices.

Officials at the Communications Commission explained that blanket licenses for all civilian defense radio stations within a civil defense operations area would be granted to an "instrumentality of local government" when the equipment is in the possession or control of the local government. A "radio aide" for the local instrumentality must be certified and appointed in accordance with FCC rules. Separate operator licenses designated "War Emergency Service Operator Permits" will be issued to persons assigned to operate each radio station. However, it was emphasized at the FCC that no individual operator permit of this special class will be issued unless the applicant first holds a regular FCC operator license or permit, and only after the FCC has been satisfied in regard to the integrity and loyalty of each applicant for a War Emergency Service Operator Permit.

Thousands of amateurs have been waiting for just such an opportunity to be of service in such manner as they are able. The opportunity is now at hand, and we are sure the most will be made of it.

—M.I.M.

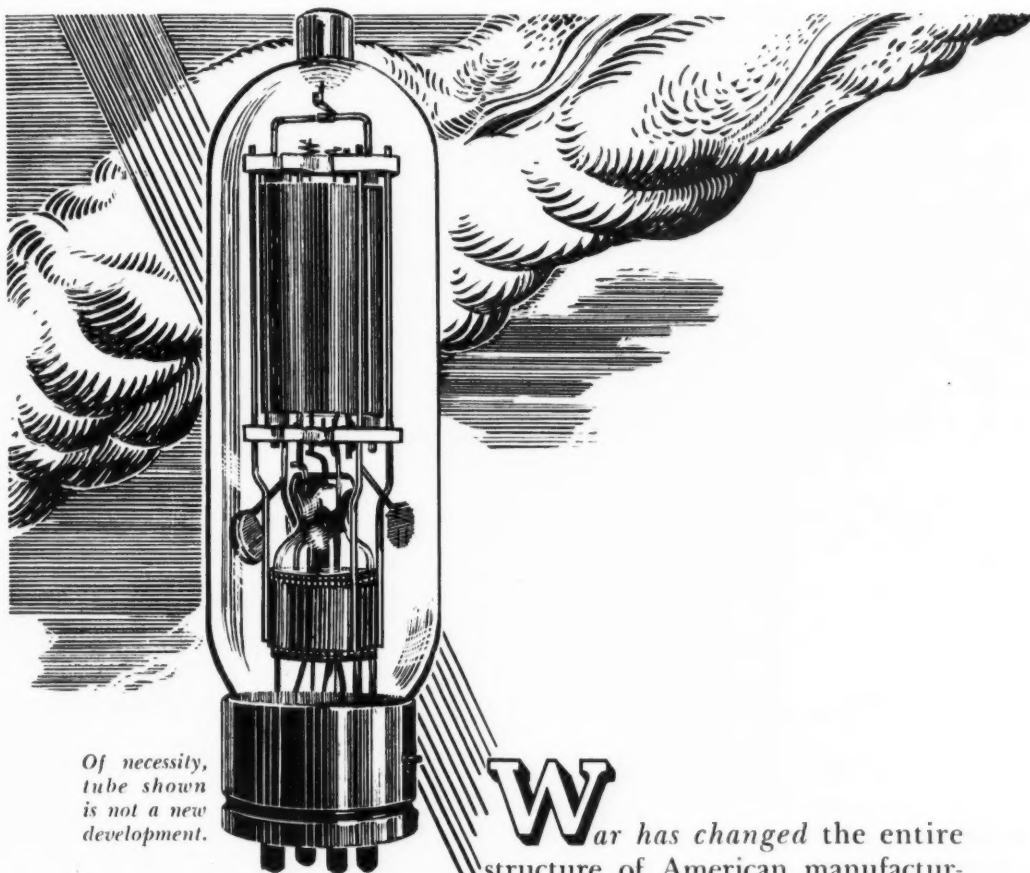

*Of necessity,
tube shown
is not a new
development.*

W

*ar has changed the entire
structure of American manufactur-*

ing with resultant shifting in engineering point of view. Electronic designers are conquering problems never before presented.

Many defense developments will — when presented to the post-war commercial market — make unheard of changes in electronic scope.

“Secret weapon” is a hackneyed phrase, but would be justified when applied to any number of new applications of electronics. “RADAR,” the u. h. f. aviation locator, may, for instance, be standard equipment on commercial aircraft after the war. Yet it is only one phase of the new developments.


The Raytheon laboratories are well in the vanguard of those developing new devices and usages. When the war is brought to a successful conclusion the RAYTHEON name will mean more than ever before to the engineering world.

Raytheon Manufacturing Co.

WALTHAM AND NEWTON, MASSACHUSETTS

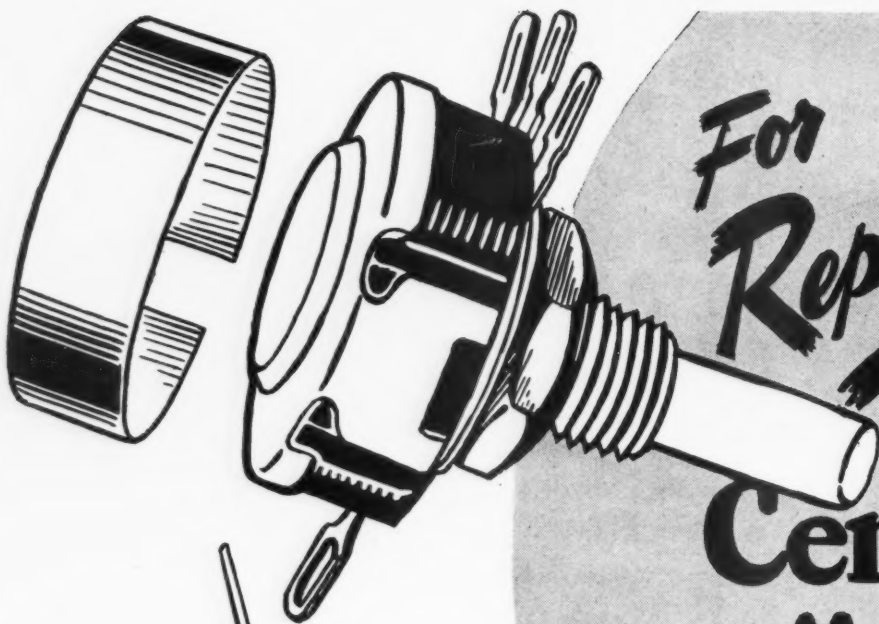**DEVOTED TO RESEARCH AND THE MANUFACTURING OF TUBES
FOR THE NEW ERA OF ELECTRONICS**





*For
Replacements*

Centralab MIDGET RADIOHM

● These are the days when the service man is king . . . and when the SERVICE DEPARTMENT is fast becoming the most important part of your organization. Keep up your good name and reputation by using CENTRALAB parts wherever possible . . . The MIDGET Radiohm, small in size, fits well in crowded chassis as solder lugs do not project far beyond the control radius of $17/32"$. Available single, dual or triple, plain or tapped, with or without switch.

CENTRALAB, A Division of Globe-Union Inc., Milwaukee, Wis.



"The large control efficiency is due to the long straight path of the famous wall type resistor. You get certain, smooth, flawless attenuation. ALWAYS SPECIFY CENTRALAB"

OLD MAN CENTRALAB

RADIO

the worldwide authority . . .

Published by
EDITORS and
ENGINEERS

Publication office: 404 North Wesley Avenue, Mount Morris, Illinois. Editorial and executive offices: 77 Bedford Street, Stamford, Connecticut. Telephone: Stamford 4-7319.

Editor

M. L. MUHLEMAN

Business Staff

K. V. R. Lansingh, Publisher

A. McMullen, Business Manager
and Treasurer

Lee Robinson, Advertising Manager
(N.Y.C. Adv. Office: 500 Fifth Ave.
Phone: LACKawanna 4-4493)

L. Slade, Circulation Manager

CORRESPONDENCE and ORDERS should be sent only to our home office. MANUSCRIPTS, if unsolicited and unusable, will not be returned unless accompanied by a stamped, self-addressed envelope.

ADVERTISING copy, copy instructions, cuts and plates (fully mounted and mortised), and duplicate space order, should be sent to "RADIO", Kable Brothers, Mt. Morris, Illinois; send original space order, rate inquiries, and general advertising correspondence to Stamford.

SUBSCRIPTION RATES (in U.S. funds): Two years, \$5.00, or \$3.00 yearly in U.S.A. (plus tax in Illinois). To Canada (inclusive of current taxes), Pan-American countries, and Spain, \$0.50 per year additional. Elsewhere, \$1.00 per year additional. Twelve issues yearly; back issues are not included in subscriptions.

NOTE: Because of wartime censorship restrictions, we must reserve the right to withhold from foreign subscribers any issue the regular domestic edition of which is not approved by the authorities for export without changes. In such cases subscriptions will be extended so that each subscriber will eventually receive the number of issues to which he is entitled.

IF YOU MOVE, notify us in advance; we cannot replace copies sent to your old address. Notice must be received by the 20th of the month preceding the cover date of first issue to go to the new address.

Photo Credits

Page	Credits
Cover.....	Norman Kaphan & Western Electric Co.
8 to 13.....	G. O. Crowley
13.....	General Electric Co.
19 to 23.....	Bradpix
52.....	RCA Mfg. Co., Inc.

JULY 1942

No. 270

Table of Contents

COVER

Dynamic view of the tank coil in the output stage of WHN's new 50-kw. transmitter recently placed in operation.

ARTICLES

Radio in Aviation—Gerald O. Crowley.....	8
Low-Frequency R-F Oscillators—Rufus P. Turner.....	14
Portable Bomb Detector—Frank A. Bramley.....	17
A Versatile Speech Console—Cortlandt Van Rensselaer.....	19
The Cathode-Ray Oscilloscope, Part IV—Jay Boyd.....	24
Electronic Voltmeters—John H. Potts.....	30
Radio Design Worksheet: No. 3—Tuned R-F Circuits.....	35
Q. & A. Study Guide.....	36
Radio-Electronic Bibliography: 3—Crystallography—F. X. Rettenmeyer	37
Theory of Cathode-Ray Oscilloscope—Jay Boyd.....	45

MISCELLANEOUS

Editorial	4
New Circular Antenna.....	13
New Products.....	50
New Method of Packing Radio Tubes.....	52
News	58
Foreign References on Crystallography.....	61
Advertising Index.....	66




CLOSE-UP OF THE FIVE-TOWER RADIO RANGE STATION.

RADIO IN AVIATION

GERALD O. CROWLEY

Senior Control Tower Operator (CAA)

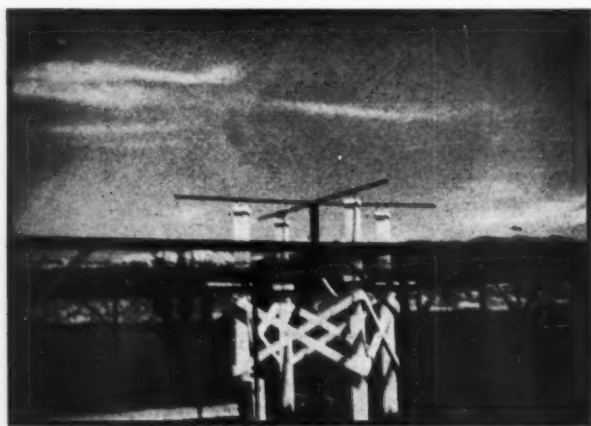Introduced originally for communication purposes, aviation radio has outgrown its swaddling clothes and assumed new facets embracing a complexity of duties and uses of the utmost importance to the safe guidance of aircraft in flight. Perhaps



Close-up of the radiating system of the 75-megacycle "Z" marker station, with its four horizontal dipoles. See Fig. 2 for pattern.

no other single factor has contributed so greatly to the rapid progress of air transportation since the county fair curio stage of 1919. The modern airliner, in addition to its short-wave radio transmitter and receiver for communication with ground stations, carries radio equipment and devices performing lesser-known tasks with an uncanny degree of accuracy and dependability.

At the altitudes and speeds of which airplanes are now capable, much of the airliner's flight path is above clouds or overcast. Visual reference to landmarks which serve as check points for slower aircraft flying closer to the ground is only rarely possible. Governing the flight altitude of aircraft in this manner, therefore, has become a practice of the past. Now the airline pilot depends upon the modern system of navigation by the use of radio aids.

Radio Range Stations

The major radio aid to navigation is the vast network of radio range stations whose "on-course" signals mark out the country's transcontinental airways. Range stations serve also as voice communi-

cation stations of the Civil Aeronautics Administration, transmitting weather reports and traffic information to pilots en route. Contrary to popular belief, the range station does not—in a true sense—emit a “beam” for pilots to follow. *Fig. 1* shows a portion of the radiation pattern of a range station using Adcock, vertical radiators. It will be noted that the “on-course” signal actually results from the overlapping of the signals radiated from the corner towers. The center tower emits a non-directive, continuous-wave signal at the assigned frequency of the station in the 200-to 400-kc. band. The N and A towers radiate in the pattern shown an unmodulated signal 1,020 cycles higher than the assigned frequency. The beat note resulting from this frequency difference is heard in the receiver as an audio note of 1,020 cycles. The N and A signals are keyed alternately with their code letters so spaced that when heard together the result is an unbroken audio note. This is the on-course signal, and occurs in the shaded portions of the diagram where the N and A signals overlap.

For voice communication the modulation is applied to the signals radiated from the center tower, resulting in simultaneous voice and range transmissions. Separation of the two signals is accomplished



One of the 120-foot vertical towers forming a part of the radio range station.

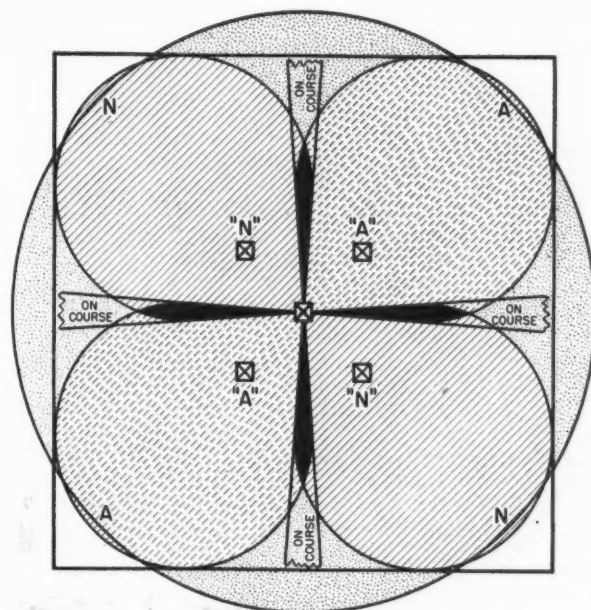


Fig. 1. Radiation pattern of radio range with Adcock vertical tower radiators. Center tower pattern, stippled; A towers, broken cross lines; N towers, full cross lines.

at the receiver through the use of band-pass and band-elimination filters. Where the range is intended for navigation purposes only, the center tower is omitted—the signal from the corner towers being directly modulated at 1,020 cycles. This also applies to the loop type stations, which, because of their undesirable night-time characteristics, are rapidly being replaced with the vertical tower type stations.

"Cone of Silence"

A pilot letting down through an overcast to land at an airport must first establish his position over the range station—this being the starting point for standard instrument letdown procedures. The radiation pattern of the range station provides him with one indication by an entire absence of range signals directly above the station. Called the “cone of silence,” this is illustrated in *Fig. 2*. Supplementing this negative indication is the signal from the “Z” marker transmitter.

The “Z” type marker station transmits on a frequency of 75 mc. Its radiation pattern is cone-shaped and follows roughly the pattern of the cone of silence above the range station. This pattern is achieved by arranging four horizontal dipoles, as shown in the photograph, and feeding opposite pairs equal currents in phase. Antenna power is approximately five watts. The signal is modulated at 3,000 cycles and provides pilots with visual as well as aural indication when crossing the station.

Also transmitting on 75 mc. are the fan-marker, or “FM” type stations. These stations are located on one or more legs of important radio ranges at



Cockpit of a Douglas DC-3 transport plane. At top of photo is the ADF tuning head. Frequency change switch at top right. In foreground is master radio panel and ADF Azimuth indicator.

distances of roughly twenty miles from the station. They serve as radio check points for the pilot making an instrument letdown and provide positive identification of range legs. The horizontal radiation pattern of this type station is elliptical in shape, with the major axis approximately four times the minor axis. Four horizontal dipoles arranged as shown in Fig. 3, give this pattern, the major axis being perpendicular to the line of the radiators. With an antenna power of 100 watts the usable signal area is three by twelve miles, and is effective to an altitude of 20,000 feet. The signal is modulated at 3,000 cycles and keyed in a series of from one to four dashes. Visual indication to the pilot when crossing the station is provided in the same manner as for the "Z" type marker station.

"M" Markers

Another type of marker station is located along the airways at points where a pilot would ordinarily change over from one range to another. Called the "M" type marker, its signals are non-directive and appear as interference on the frequency of the range station signal. The stations are low-powered and can be heard for a distance of about fifteen miles.

They remind pilots to change the tuning of their range receiver to the frequency of the next range station. They serve also as secondary CAA communication stations, providing voice facilities on 278 kc.

278 kc. is also the transmitting frequency assigned to airport control towers. The control towers contact aircraft approximately ten minutes flying time from the field and issue landing instructions, traffic information, etc. Tower transmitters are authorized to use a power output of 15 watts, although often the transmitters are capable of up to 100 watts output. Full power is utilized when a directive antenna system is available and the transmitter may do double duty as a runway localizer. In this service the transmitter performs as a miniature range station, its on-course signal projected directly down the runway to be used. Modern u.h.f. blind landing systems now undergoing extensive testing are expected to replace entirely the low-frequency runway localizers.

Plane Equipment

To make full use of these radio navigation aids, and to maintain two-way radio communication with CAA and company ground stations, the modern airliner is fitted with an imposing complement of radio

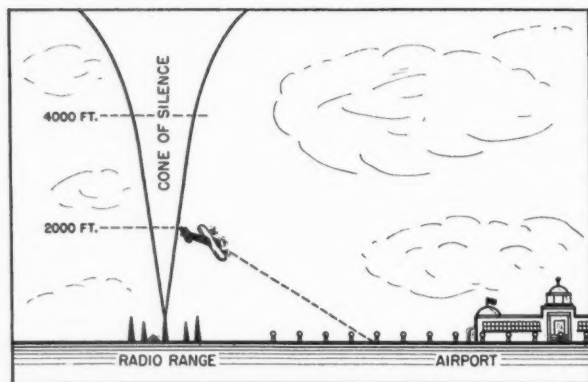


Fig. 2. Cone of silence above radio range station.

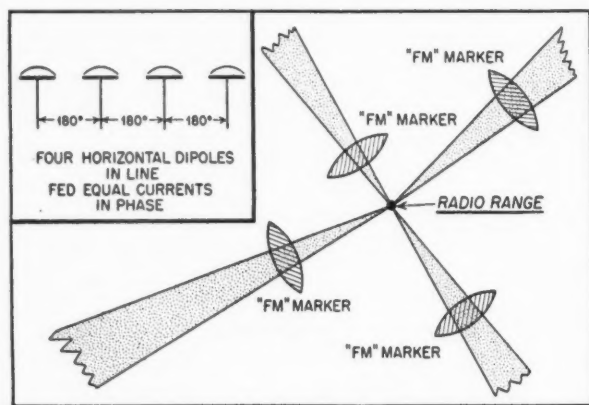



Fig. 3. Fan markers on legs of radio range. The antenna system is shown in box in upper left corner.

equipment. A typical setup in a Douglas DC-3 twenty-one passenger transport includes the following:

- 1—Range receiver.
- 2—U.h.f. marker receiver.
- 3—Automatic direction finder.
- 4—Multiple-channel transmitter-receiver.
- 5—Interphone amplifier.
- 6—Power source for above units.
- 7—Antennas—a total of six.
- 8—Static discharge cartridges.
- 9—Audio filters, jack boxes, control heads, master control panel, microphones, headsets.

Space and weight are, of course, primary considerations in aircraft radio equipment—as are ruggedness and dependability. Units must be mounted to withstand severe jolts and be accessible in flight for minor adjustments. This condition is met in the DC-3 by mounting the first five items above in a rack directly behind the cockpit forward of the passenger cabin. Jack boxes and control heads and the master control panel are mounted in the cockpit within easy reach of the pilots, providing 100 per cent remote control of all equipment. Units are individually fused, with the fuse panel readily accessible in flight. Dual frequency coverage is provided for all but the 75-mc. band, item -3- above covering both range and company communication frequencies and considered a stand-by receiver for these bands.

The range receiver is an eight-tube superheterodyne covering the band of frequencies from 200 to 400 kc. Remote tuning is accomplished by the use of "tach" shaft and control head; "coffee grinder," the pilots call it. The coffee grinder can be seen in the center of the accompanying photograph, mounted just above the windshield to the right of the center column. The range receiver is used for reception of radio ranges, "M" type marker stations and control towers. To provide quick change to tower frequency without disturbing the range tuning, a set of condensers within the receiver are pre-tuned to 278 kc. A toggle switch on the master control panel actuates a relay to select this frequency at will. Volume control, a.v.c. switch, beat oscilla-

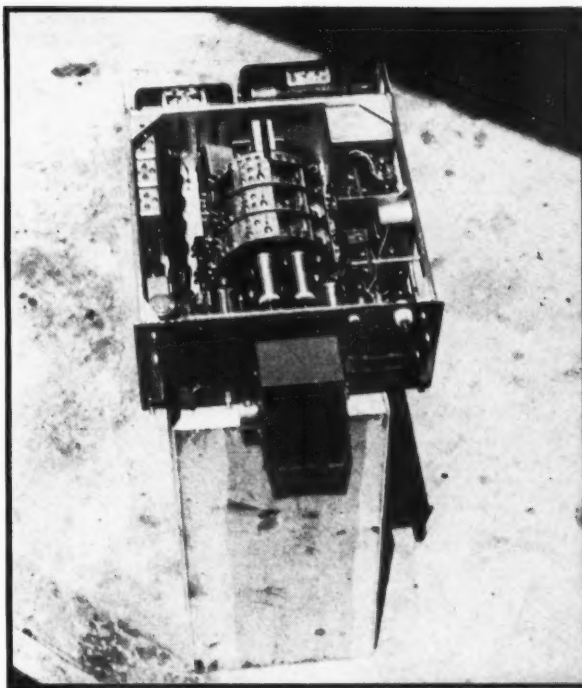

Open view of the 50-watt 10-channel aircraft transmitter-receiver. Frequency selection is by a motor-driven turret controlled from cockpit. Both transmitter and receiver channels are fixed-tuned and crystal-controlled.

tor switch and antenna selector switch are also located on the master panel. The antenna normally used is a balanced "T" located beneath the aircraft, but during static conditions a fixed one-turn loop may be switched in.

Band Filters

The switches to select range or voice broadcasts from the range station are incorporated in the pilot's individual jack boxes. The filter circuit is shown in Fig. 4. It consists of band-elimination and band-pass networks. For voice reception the band-elimination network is cut in, its components designed for maximum attenuation at 1,020 cycles. Cutoff frequencies are at approximately 830 and 1,250 cycles, sacrificing very little in speech quality. The band-pass filter for reception of range signals is designed for minimum attenuation at 1,020 cycles with cut off at approximately 900 and 1,100 cycles. Its use permits reception of range signals without the disturbing interference of the voice modulation.

The ultra-high-frequency marker receiver is used for reception of "FM" and "Z" type marker stations. Crystal control of frequency is obtained by utilizing a 6N7 tube as crystal oscillator and harmonic generator. The ninth harmonic is selected and beats with the incoming signal in a 6J7 modulator tube in the usual manner. Antenna used is a dipole mounted below the belly of the aircraft and coupled to the receiver by a low-impedance cable. Visual indication for the pilots is provided by rectifying a por-


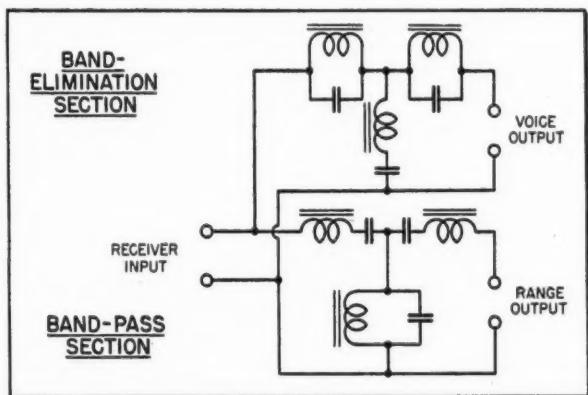


Fig. 4. Audio filter for selection of voice or range signals.

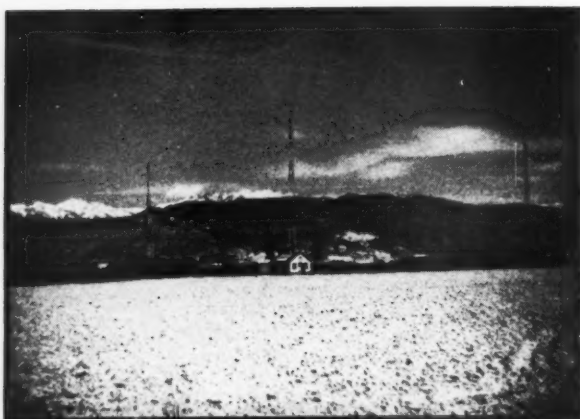

Far view of a typical five-tower radio range station, with 120-foot vertical towers.

tion of the a.f. signal output and applying this voltage to the d.c. winding of a reactor of the saturable-core type. When the impedance is lowered by saturation, sufficient current flows in the a.c. winding of the reactor to operate an indicating lamp on the instrument panel. At the same time the pilots hear in their headphones the characteristic 3,000-cycle note of the u.h.f. marker stations.

Automatic Direction Finder

The automatic direction finder covers range and broadcast frequencies as well as the aircraft communication frequencies from 2,800 to 6,600 kc. In the space allotted, a technical description of the operation of the ADF's complicated circuits is hardly possible. Briefly, the phase relationship between current and voltage of an incoming signal as received simultaneously on a sense and a loop antenna is utilized to keep the loop automatically turned to the null position for the received signal. The loop is coupled by an autosyn system to an azimuth indicator in the cockpit whose needle then points directly to the station being received. The ADF azimuth indicator can be seen in the photograph just forward of the throttles on the control column. The ADF tuning head is in the extreme top center of the picture above the windshield. The meter fastened to the side of the head provides fine adjustments in tuning.

The importance of the aircraft communication equipment can be measured only by the importance of the complete CAA system of traffic control. Frequent position reports must be made by each aircraft in flight, that its course may be plotted on the flight progress boards in the airway traffic control centers. Traffic information and clearances must be received and acknowledged for. Frequent information on current and forecasted weather conditions must be made available to the pilots. These and other requirements denote the communications unit as perhaps the most valuable piece of radio equipment carried by the airliner. Constant development over

a period of years has evolved the present truly remarkable piece of apparatus.

A transmitter and receiver on one frequency was all that was once required for aircraft communication purposes. Heavier schedules and longer runs brought about the boosting of power in ground-station transmitters and consequent frequency congestion. It was found that a single frequency was not suitable for both day and night use. The aircraft band is now split at 4,000 kc., frequencies above that being used during the day and the lower end utilized after sunset. A coast-to-coast airline now splits radio communications into four sections, each using separate day and night frequencies. In addition to these eight channels required for company operations, 3,117.5 and 6,210 kc. are used by aircraft to communicate with CAA stations and airport control towers. The aircraft transmitter, then, must be able to select at will any one of ten operating frequencies.

Aircraft Transmitter-Receiver

The modern ten-channel aircraft transmitter-receiver shown in the accompanying photograph weighs 74.5 lbs. complete. It occupies a space in the radio rack slightly less than 23 by 16 by 8 inches. It provides 50 watts output, 100 percent modulated, on ten selected crystal-controlled frequencies between 2,500 and 13,000 kc. The ten receiving channels are also crystal controlled and utilize the transmitter tank inductances as r.f. coils in the "receive" position. Frequency selection is accomplished by a motor-driven turret remotely controlled from the cockpit.

In the transmit position a 6L6 tube acts as a Miller crystal oscillator on the lower frequencies and becomes a Pierce oscillator on the higher channels. The 6L6 drives two 807 tubes in parallel to an output of 50 watts. A zero-level carbon mike feeds a 6V6 speech amplifier tube which drives a pair of 807 modulator tubes in Class AB₂. The audio response from 500 to 3,000 cycles is flat to within plus or minus 3 db, and 100 percent modulation of the 50 watt carrier is easily accomplished. Power consumption in the transmit position during full modulation is 37 amps at 12.3 volts, plate power being furnished by the larger of the two dynamotors mounted at the rear of the chassis. The small box protruding from the front panel contains the motor which drives the band-switching turret. In the cockpit photograph the frequency change switch may be seen just above the windshield on the extreme right, while other control switches are incorporated in the master control panel. The antenna is stretched horizontally above the fuselage from just behind the cockpit to the rear fin. It is approximately 45 feet long and is tuned by rotating the tank coils at the front of the turret.

In the receive position the 6L6 tube is again utilized as crystal oscillator. In receiving, the Pierce circuit is used on all frequencies. Two r.f. stages

precede the first detector and give excellent image rejection. Two i.f. stages, combination second detector-a.v.c.-first audio and push-pull 12A6 audio tubes complete the tube complement. Sensitivity is better than 2 microvolts-per-meter at all frequencies. Plate power is supplied by the smaller dynamotor. Power consumption in receive position with transmitter tube filaments on is 7.2 amps at 14 volts.

The output of all receivers is fed through a master dual output interphone amplifier. This provides separate output for each pilot's jack box and permits interphone communication. The jack box selector switches are so arranged that one pilot may receive range signals while the other conducts two-way radio communication with ground stations. During an instrument letdown one pilot may listen to the range receiver while the other double-checks him by tuning in the range signals on the ADF receiver.

Anti-Static Cartridge

Not the least novel piece of radio equipment aboard the airliner is the anti-static cartridge. Flying through snow or dust storms the entire aircraft may become heavily charged with static electricity. The charge is often so heavy that sparks leap across windshields and radio antenna insulators. At such times radio reception even on the loop antennas is knocked out completely. Aeronautical radio engineers went to work on this knotty problem and devised the anti-static cartridge as a means of bleeding off this static charge. The DC-3 carries two of these cartridges in the extreme tail just below the rudder and stabilizers. Each consists of a dural tube about three inches in diameter and twelve inches long. About four feet of flexible steel wire connected to a similar length of rubber-covered resistance cord is coiled inside. By throwing a switch in the cockpit the pilot can release a spring gun mechanism in the cartridge which shoots the wire out into the slipstream. The static charge then discharges from the tip of the trailing wire, while the resistance cord damps the oscillation in the same manner as the resistance type automobile spark-plug suppressor.

Future in U.H.F.

The trend in aviation radio is toward the ultra-highs. The success of recent tests on u.h.f. radio ranges operating in the band of 123 to 127 mc. foretells abandonment of the low-frequency range stations. CAA airport towers are already installing u.h.f. transmitters which will operate in the frequency range of 129 to 132 mc. A blind landing system in use at Indianapolis, Ind., utilizes three u.h.f. transmitters in performance of its various functions. Thousands of successful experimental blind landings have been made using this system. There is no question but what this type equipment

will soon replace the inadequate low-frequency runway localizers in use at some fields.

Radio altimeter equipment has been undergoing extensive service testing by the airlines and military and naval services. This device consists of a frequency-modulated transmitter operating in the neighborhood of 420 mc., a receiver at the same frequency and a cycle-counting device. In use the transmitted signal is radiated downward from the aircraft while a small portion of the signal is permitted to reach the receiving antenna. The signal reflected from the ground is then compared in the receiver with the direct signal received, the difference in frequency being directly proportional to the distance of the aircraft above the ground. The cycle-counting circuit applies this reading to a meter with its scale calibrated in "feet above ground." The advantage of this type of indication over that of the pressure-type altimeter, which indicates height above sea level, is immediately apparent.

The principal advantages expected to be gained from the swing to ultra-highs are: freedom from atmospheric interference; freedom from fading and skip effects; reduction in power and weight of equipment; smaller, but more efficient antenna systems; more frequencies available. Today the ultra-highs have the 200-to 400-kc. band on the run. Tomorrow they may assail the ramparts of the medium-wave communication band. And all towards the one objective: that aviation may continue its phenomenal rate of progress—ad finem. . . .

NEW CIRCULAR ANTENNA

Radio engineers inspecting a new General Electric circular type radio antenna exhibited at the recent convention of the Institute of Radio Engineers at Cleveland. An outstanding feature of the antenna, simple in structure, and resembling a donut, is its ability to radiate substantially uniform energy in all directions without resorting to the complex and comparatively costly structures previously designed with phasing networks to secure this uniform pattern.



LOW-FREQUENCY R-F OSCILLATORS

Design of 10- to 500-kc. Generators for Carrier-Current and Remote-Control Applications

RUFUS P. TURNER

Frequencies between 10 and 500 kc., which formerly were of no interest except for the appearance of superhet intermediate frequencies at four or five points in this range, are important now as channels for carrier-current and induction field communication, and remote control.

The generation of low radio frequencies is accomplished with oscillator or amplifier circuits basically identical with high-frequency units, except for the difference in tank circuit values. Inductances and capacitances for this work are larger in magnitude; while, generally speaking, stray capacitances (including tube interelectrode capacitances) are of less moment than in short-wave circuits.

Low power is employed in carrier current and induction field systems in order to keep down interference. Tank coils for such power levels need not be bulky, but may consist of the high-inductance choke coils, i.f. oscillator "transformers," old-time honeycomb coils, etc., from the spare parts shelf.

Most of us have some of these inductors lying around unused, and these may be pressed into service as low-frequency tank coils. If the inductance of a readily available coil is insufficient to resonate at the desired low frequency, the difference may be made up by padding the circuit with a silver mica fixed condenser of suitable capacitance. And while the presence of fixed capacitance in the circuit will limit the tuning range of the variable condenser, the circuit may still be peaked to the desired frequency by the latter.

Determining L and C

Fig. 1 gives a chart for finding either the inductance or capacitance which will resonate at any desired frequency between 10 and 500 kc. When either one of these quantities is known, one may readily find the other by lining up the known points with a straight edge. If both inductance and capacitance values are known, the frequency to which they will tune may be determined from the chart.

An example of the use of the chart is the determination of required condenser size: To find the total capacitance required to tune a 1-millihenry coil to 50 kc., lay a straight edge across the chart so that one end intersects the inductance scale at the 1-mh.

point and the other end rests upon the 50-kc. point on the frequency scale. The required capacitance—0.01 μ fd.—is then read at the point of intersection of the straight edge with the capacitance scale. Another example: To what frequency will a 2.5-mh. air-core choke coil and a 100- μ fd. condenser resonate? The 2.5-mh. point on the inductance scale is lined up by means of the straight edge with the 100- μ fd. point on the capacitance scale. The line established by the straight edge then intersects the frequency 320 kc. on the frequency scale.

Low-Frequency Coils

Air-core coils for low-frequency oscillators and amplifiers may take any one of several shapes. The principal configurations are (1) single-layer solenoid, (2) multi-layer solenoid, and (3) universal-wound type.

For frequencies between 400 and 500 kc., the single-layer solenoid type of construction may be employed without running into ungainly sizes for a given inductance, provided, of course, that the current-carrying requirement of the coil is low enough to allow small-sized wire to be used. The inductance of a single-layer coil may be determined by means of the equation:

$$L = \frac{200 A^2 N^2}{3A + 9B} \quad (1)$$

Where L is the inductance in millihenries;

A , diameter of coil in inches;

B , length of winding in inches;

N , number of turns.

If a large value of current is to flow through the coil, the wire size must be increased proportionately and a single-layer type of inductor might become too bulky. In order to preserve the same coil length, it then becomes necessary to wind the inductor in more than one layer.

The second pattern—the multi-layer coil—is wound by placing one complete layer of winding upon another until the required number of turns have been wound. Spools or bobbins may be used as forms for this type of winding. While this type of construction materially reduces the girth of a high-current coil, it increases the distributed capacitance and attendant losses.

Equation (1) is altered slightly to give the inductance of a multi-layer coil:

$$L = \frac{200 A^2 N^2}{3A + 9B + 10C} \quad (2)$$

Where the additional term, C , is the radial depth of the winding, in inches, and all other terms are the same as in Equation (1).

The third pattern—the universal winding—is difficult of duplication unless a coil-winding machine is available. Most i-f. transformers and r-f. chokes are of this type of construction, and may be readily employed. For low-power, low-frequency generation, receiver-type r-f. chokes are available in inductance values between 1 and 250 millihenries and with current-carrying capacities from 50 to 125

milliamperes. Superhet beat oscillator coils are likewise convenient for low-power work and are available for 175, 456, 465, and 500 kc. These operating frequencies may be still further lowered, when desired, by loading the circuit with fixed condensers. For higher-powered oscillators and amplifiers, transmitter-type r-f. chokes (also universal wound) are available in inductance values between 225 microhenries and 25 millihenries, and rated to carry from 250 to 500 milliamperes.

Circuits

Figs. 2 to 4 show well-known circuits which are finding use in low-power systems for low-frequency

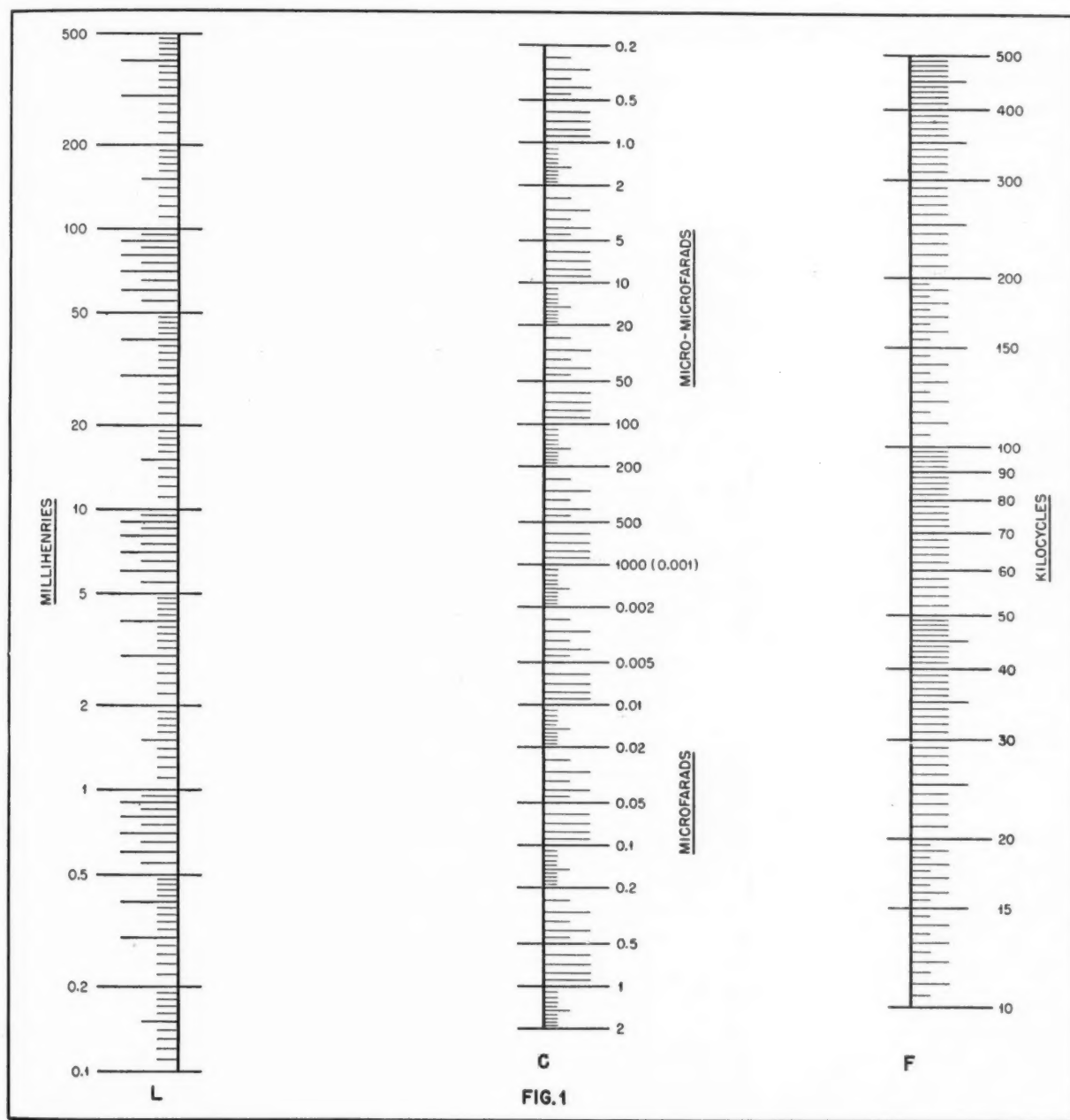


Chart for finding either the inductance or capacitance which will resonate at any desired frequency between 10 and 500 kc.

emergency communications and for remote control.

Fig. 2 is an electron-coupled arrangement with constants shown for 100-kc. operation. The coil, L , is a 2.5-mh. pi-wound, receiver-type r-f. choke. The cathode tap is connected between the first and second pi's from the grounded end. $C1$ is a 0.001- μ fd. silver mica fixed condenser for tank-circuit loading, while $C2$, the variable section, is a 100- μ fd. midget tuning condenser.

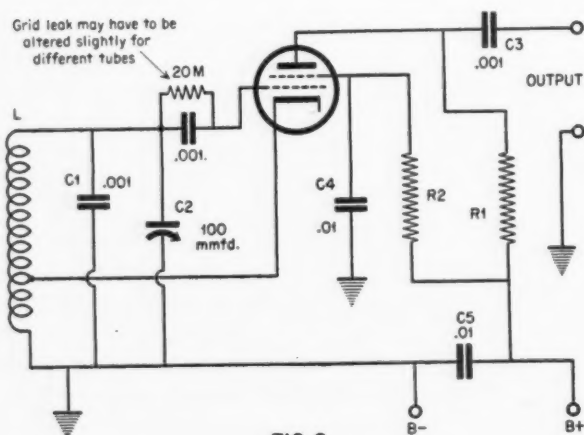


FIG. 2

Electron-coupled oscillator circuit with given constants for 100-kc. operation. Tube may be pentode or beam-power receiving type.

The tube may be any convenient receiving type pentode or beam-power tetrode of suitable power output. If a pentode is used, the suppressor must be connected to the cathode at the socket. The plate and screen resistors, $R1$ and $R2$, will be those values specified in the characteristics for the tube used. The r-f. output is delivered through a fixed mica condenser, $C3$. $C4$ and $C5$ are respectively screen and plate bypass condensers of high capacitance.

The inductor for this oscillator might likewise be an internally-tuned superhet-type of beat oscillator coil.

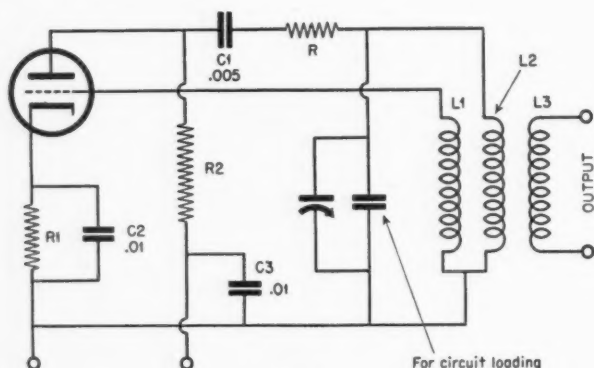


FIG. 3

Resistance-stabilized low-frequency oscillator circuit suitable for low-power carrier-current work.

Fig. 3 shows a resistance-stabilized low-frequency oscillator circuit which has been in use for some time in signal generators. This is a stable circuit well suited to low-power work where large drains are not to be made upon the oscillator, such as in driving a low-frequency output amplifier.

Peculiar to this circuit is the stabilizing resistor, R , which is connected in series with the plate coil, $L2$. The value of this resistor, which must not be less than 5 times the tube plate resistance, may be determined approximately from the equation:

$$R = R_L (\mu - 1) - R_p \quad (3)$$

Where R is the value of the stabilizing resistor;

R_L , recommended load resistance for the tube;

μ , amplification factor of the tube;

R_p , plate resistance of tube.

(See tube characteristics sheet for R_L , μ , and R_p .)

With this approximate value in the circuit, the exact value may be arrived at experimentally by increasing the resistance to the point where oscillations are stopped, then decreasing the resistance to the point where the circuit goes into oscillation quickly as the plate voltage is rapidly switched on.

The resistance-stabilized circuit operates best with triodes with amplification factors between 5 and 10. The following tubes gave good performance in tests carried out by the writer: 1G4-G, 1H4-G, 2A3, 6A3, 6AD7-G, 6AE5, 6F6 (triode-connected), 6L6 (triode-connected), and 45.

The cathode resistor $R1$ is of such value as to give slightly less bias than would be required for Class A

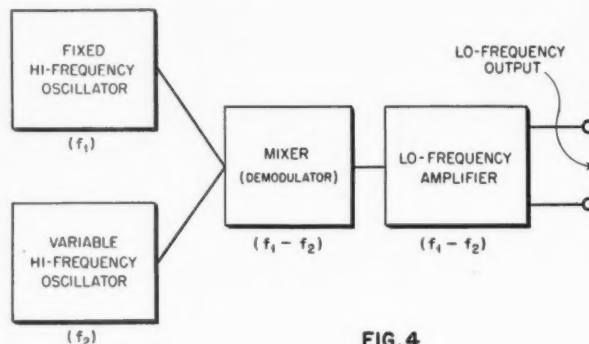


FIG. 4

Functional block diagram of beat-frequency oscillator.

amplifier service with the same tube, and the plate load resistor is of approximately the same value required for Class A. The coupling condenser, $C1$, and the bypass condensers, $C2$ and $C3$, should be of mica construction for best results.

The grid, plate, and coupling coils— $L1$, $L2$ and $L3$ —are close-coupled, generally being wound upon the same form in such a manner that the grid coil is split, half of it lying on each end of the plate coil. The plate and grid coils are usually of the same inductance, and the size of the close-coupled coupling coil is adjusted to give the desired voltage output.


Fig. 4 shows a functional block diagram of a beat-

[Continued on page 44]

PORTABLE BOMB DETECTOR

FRANK A. BRAMLEY

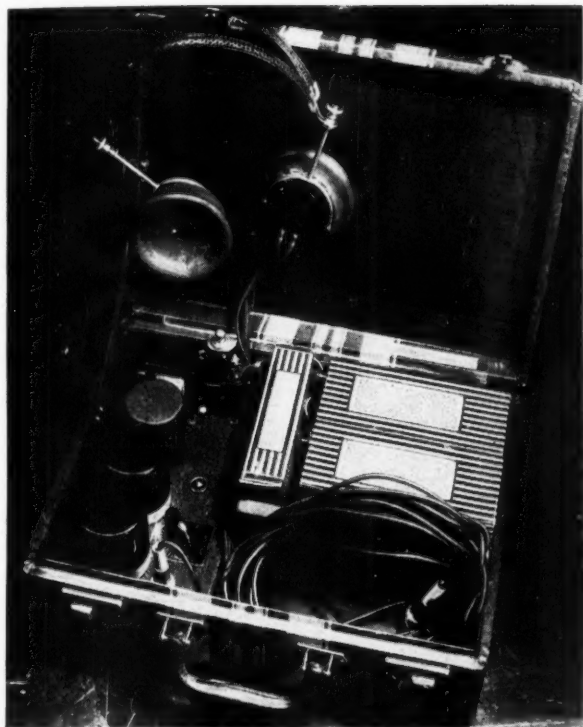Radio Technician, Connecticut State Police



The portable, battery-operated bomb detector. It is housed in a lady's overnight case with inside dimensions of $12\frac{1}{2}$ " x $9\frac{1}{4}$ " x 4" deep. Any similar case will do.

As preparations for National Defense increase in scope and intensity, local and state police departments are perfecting plans to safeguard life and property with every known scientific device. With this in mind the radio technicians of the Connecticut State Police Department were directed to design a device to minimize the danger to officers assigned to investigate suspicious packages, supposed bombs, etc. Recalling the death of several New York State detectives who tried to remove a bomb at the 1940 New York World's Fair, and the recent FBI round-up of Axis saboteurs, makes any device which would decrease the danger of investigating suspicious packages a welcome object to police officers.

The device described herewith has actually been used to test a supposed bomb. The officer who used the amplifying device was able to do so successfully although he had never been instructed in its use.

Most bombs of the homemade type, such as are

likely to be found in public places or defense factories, use a timing mechanism which will usually consist of some simple clockwork to set off the bomb after the saboteur has made his getaway. Such a mechanism would make a ticking or clicking sound which could be heard if one were close enough. But getting close is the thing most unwise to do.

Essentials of Outfit

The complete outfit consists of three units, only one of which will be completely described here. They are:

1. A high-gain, battery-operated amplifier
2. A jointed boom with attached microphone
3. A metal shield to hold in front of the operator's body.

The so-called "Bomb Detector" is essentially a high-gain, battery-operated speech amplifier. The pickup device is a Shure "Stethophone" which is a special type of crystal microphone. The reproducer is a pair of crystal headphones fitted with earmuffs.

Since the purpose of the device is to pick up faint sounds originating within a box or package at any spot, the device must be small and easily portable—thus battery-operated. And also, since the persons operating it are almost certain to be excited or very nervous, it must be as nearly foolproof as possible.

For these reasons the device is completely shielded and the tubes are mechanically protected; an automatic switch is provided so that the batteries will be turned off when the cover is closed. The batteries are selected for their quality of long shelf life. The earphones have earmuffs attached permanently to them with Duco cement; thus extraneous noise will tend to be reduced and the operator may concentrate on the sounds picked up by the microphone. Likewise, the microphone is selected because of its characteristic of eliminating most of the incidental noises in or on the surface of the object with which it is in contact.


The Amplifier

The amplifier itself is a straightforward speech amplifier essentially flat in characteristic. It uses standard 1.5-volt tubes. The first two stages are self-biased by virtue of the 10-megohm grid leaks, while

No correction of frequency response is necessary, and the amplifier appears to be reasonably flat nearly up to 15,000 cycles, but cuts off rapidly below 150 cycles.

In practice the operator stands behind an iron shield or a heap of sandbags and manipulates the boom until the microphone comes into contact with the object to be examined. The microphone must be in contact because the design of the Stethophone is such that it does not respond efficiently to air-borne sounds but is very sensitive to contact sounds. For instance, a very quiet wrist watch lying on a table several feet from the microphone will produce loud sounds in the earphones, if the mike is also on the table, but the same watch would not be heard if held only a few inches from the mike suspended in air. The use of a contact type mike and of headphones is necessary to reduce extraneous noise and feed-back. With a standard mike, a typewriter 50 feet away or an auto horn two blocks away produce deafening sounds if the gain is up high.

[Continued on page 43]

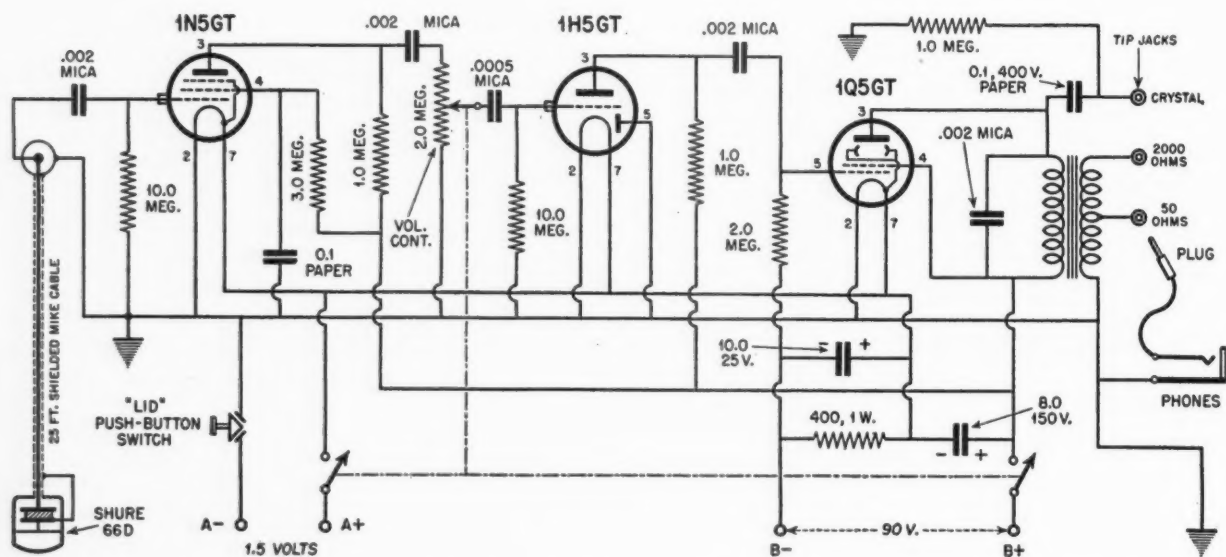

Schematic of high-gain, battery-operated a-f. bomb detector amplifier, designed for use with Shure Stethophone.



THE COMPLETED CONSOLE. THE 78 TURNTABLES ARE IN FRONT, THE 33 TABLE AT LEFT REAR.

A Versatile

SPEECH CONSOLE

CORTLANDT VAN RENSSELAER

◀ The Speech Console herein described was constructed to make possible a maximum number of relaying, sound reproduction and recording functions.

The primary objectives in working out the design were economy, reliability, fidelity, and completeness. Since the first of these was a major factor, care was taken in the selection of the apparatus to secure types which would give a maximum of quality for a minimum of cost. That this aim was realized is amply demonstrated by the fact that the frequency and distortion characteristics compare most favorably with those of commercial equipment designed for broadcast applications. Besides the recording turntable, two others were added for dubbing; a 78 r.p.m. and a 33-1/3 r.p.m. table. In order that the space be used with the utmost efficiency, a speaker resonant chamber and a record file were included in the construction of the desk.

Mechanical Design

A study of the various possible schemes for de-

signing the desk revealed that a speech amplifier console on a table, of which the turntables were an integral part, would be the most logical arrangement. The recess in the front of the desk top makes all apparatus more accessible to the operator. The top shelf of the record files on the side of the desk accommodates 250 ten-inch commercial pressings. The lower shelf holds 200 twelve-inch records or a number of the now popular albums. The speaker cavity on the right hand side is of the base-reflex type and will give, with a reasonably good speaker, excellent listening quality. The dimensions for placing the rear baffle are such that the area of the enclosure causes it to resonate at approximately 100 cycles, but to obtain the best possible response certain measurements should be made.

Baffle Adjustment

It might be well to theorize on the design principles of speaker cavities in order that this procedure may be better understood. All loudspeakers have such

frequency characteristics that their lower register drops off at some specific frequency. The lowest note which most reasonably-priced speakers will reproduce with normal volume is about 150 cycles. The ideal frequency response curve of such a speaker would be similar to that in *Fig. 1-A*. To make this

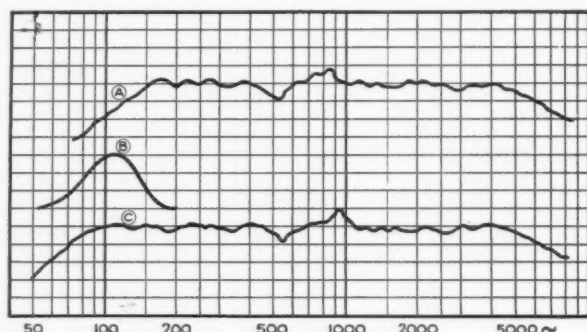


FIG. 1

A—Ideal response curve; B—peak provided by baffle; C—curve of combined speaker and bass-boost baffle.

speaker reproduce lower notes with normal volume, it is necessary to build its baffle in such a fashion that it will resonate about 50 cycles lower than the lowest frequency of the speaker. The resonance curve for such a baffle is shown in *Fig. 1-B*. Adjusting the baffle so that it matches the speaker requires some patience, but it can be done with normal laboratory equipment. The curve of the combination of the speaker and baffle is shown in *Fig. 1-C*.

The suggested procedure is as follows: Connect an audio oscillator to the input of the amplifier to which the speaker is connected. Put a volume-indicator meter across the output of this amplifier and maintain the output over the tested range of frequencies at a constant level. To measure the characteristics of the speaker, a microphone with its calibration curve must be used. This calibration curve is usually supplied with a microphone and can be considered a good enough criterion of the microphone's characteristics to be used for this purpose. It is suggested that the microphone be connected to an amplifier, the output of which is read on a db. meter. Then a curve should be drawn of the decibel indications over speaker frequencies of from 50 to 200 or 300 cycles. In order that there be as little error as possible from side radiation of the speaker cone, the microphone should be placed directly in front of the speaker and some distance from it. At any specific frequency, the microphone output will be a certain number of db. below a reference level. This number of db. must be added to the speaker frequency response curve at various points in order to correct it for the error caused by the microphone.

From observation the speaker cutoff point and the baffle resonant frequency can be determined. The rear board of the speaker cavity in the desk should

be moved back and forth, and the characteristics should be measured for various positions. When the response curve appears similar to that of *Fig. 1-C*, the baffle can be considered properly placed.

Construction of Desk

The desk is constructed of three-quarter inch five-ply and is held together with wood screws. The lumber was purchased in the exact sizes needed, and sanding and assembling the pieces required only a few hours. The irregular shapes were cut out by the lumber company. The desk is mounted on two-by-three bases which leave foot room around the edges and add a touch of smartness to the appearance. Eight flat steel casters are placed on the bottoms of the two-by-three's to prevent marring of the floor. It is finished with clear shellac.

The speech amplifier case originally contained a Philco radio, which was transferred to another cabinet. An interesting feature is the tilt back chassis which makes the sub-deck wiring, the tubes, and the panel connections instantly available for servicing. As can be seen in *Fig. 2*, the chassis is in a vertical position with the underdeck wiring facing outward and the transformers and tubes in a horizontal plane inside. It is mounted on small hinges which are attached to the rear of the cabinet with wood screws.

Electrical Considerations

For a clearer understanding of the possible operations which can be performed with the amplifier, a


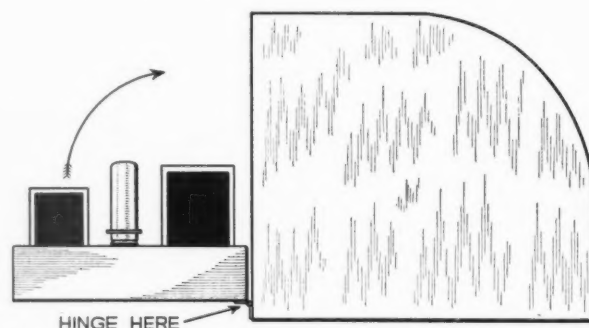


FIG. 2

Details of tilt-back chassis, for easy servicing.

self-explanatory block diagram is shown in *Fig. 3*. The mixing circuit of the amplifier consists of eight channels which are connected through four two-position key switches and four potentiometers to the four grids of two 6N7's. As the block diagram indicates, the respective connections are as follows: 1) Microphone, 2) Remote line, 3) Microphone, 4) 33-1/3 r.p.m. turntable, 5) Recording turntable, 6) 33-1/3 r.p.m. turntable, 7) 78 r.p.m. turntable, 8) Receiver.

The reason for having two separate inputs for

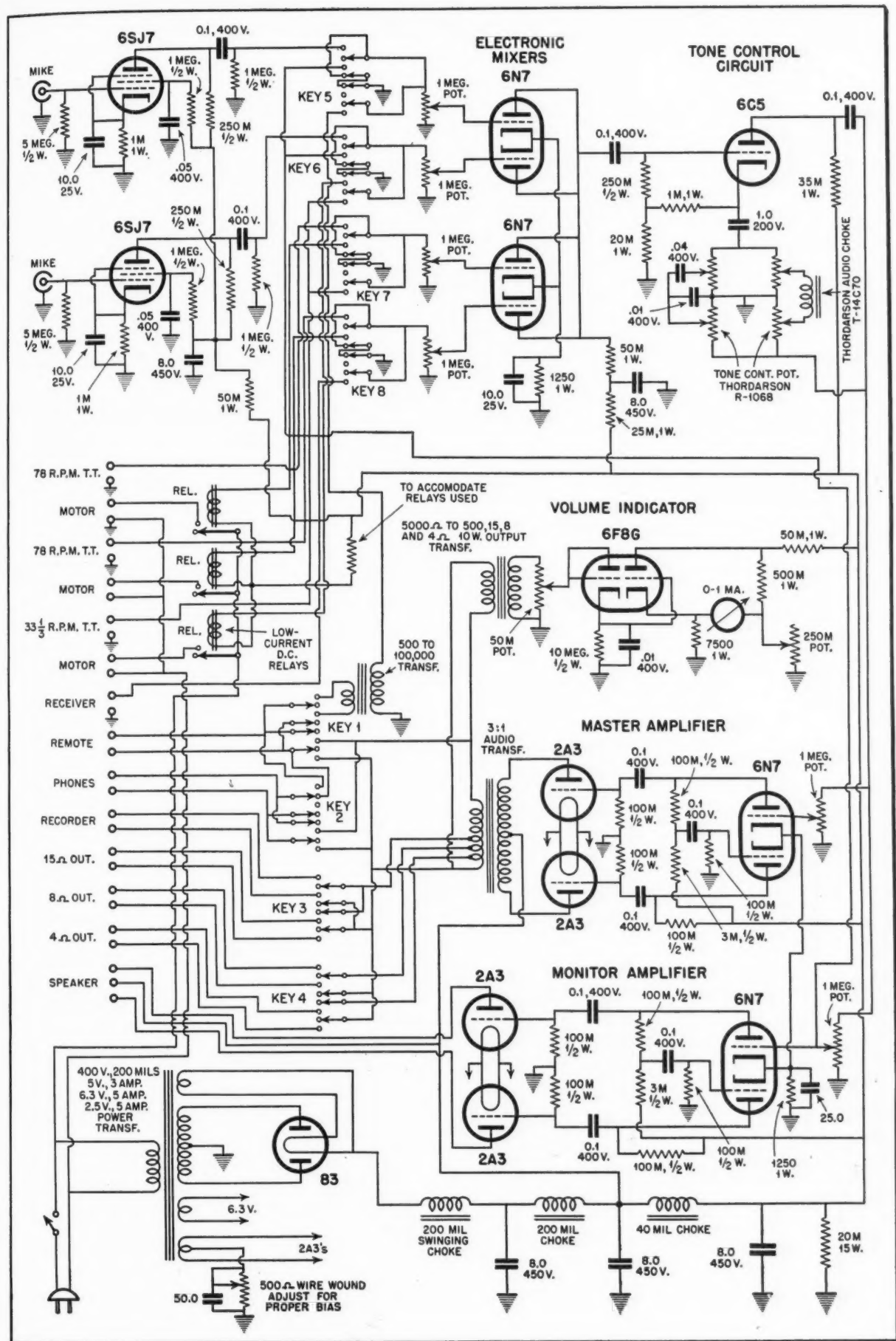


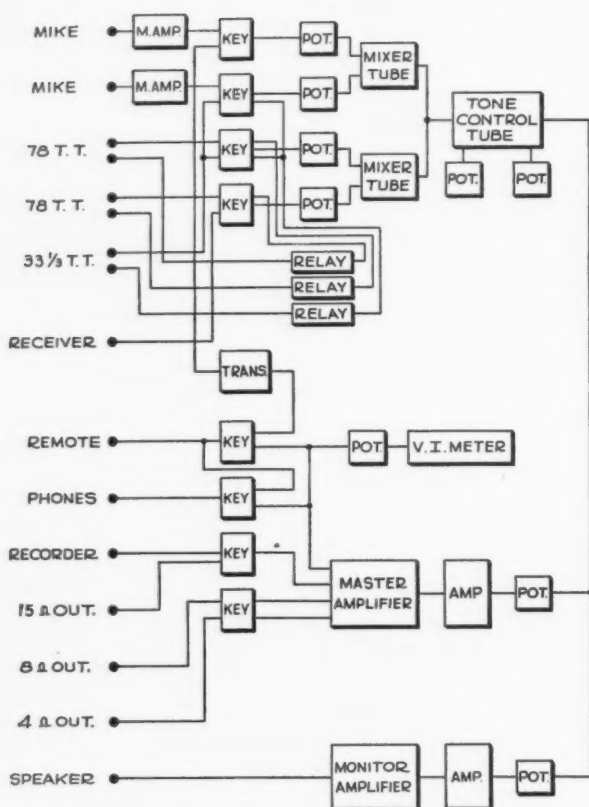


FIG. 3

A block diagram of the complete speech console, showing operations that may be performed with the equipment.

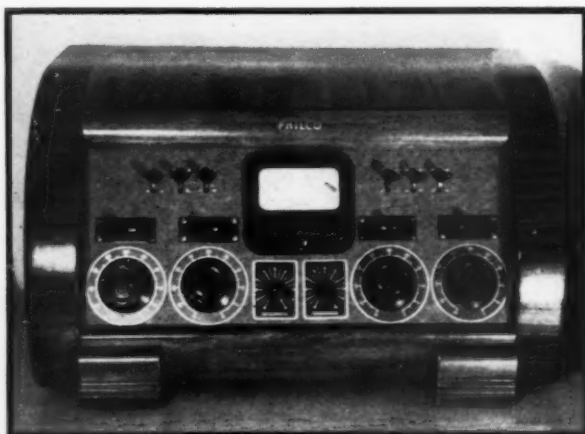the 33-1/3 r.p.m. turntable is that the simultaneous use of either two microphones or both 78 r.p.m. tables would make impossible the use of the slower speed one. The receiver in use here is a Hallicrafters communication type, the headphone high-impedance output of which has excellent quality on broadcast



The amplifier console. The Thordarson tone control potentiometers, which were added later, were placed in the upper left corner. One of the key switches was moved to the right side to provide the necessary room. Note convenient position of volume-indicator meter and gain controls.

reception. Aside from switching the inputs, the four main keys also perform other important functions. The first two are so connected that switching on the microphones automatically turns off the monitor speaker, thereby preventing feedback. Each turntable switch is connected to a relay which automatically sets the motor running when it is closed.

Electronic mixing with 6N7's is particularly well suited to this type of amplifier, since constant output characteristics are maintained over long periods of time, and the advantages of cross-mixing are obtained without appreciable power loss. The over-all voltage gain from any of the inputs to the output of either 6N7 mixing stage is 19. Conventional 6SJ7 microphone amplifiers are used. Their voltage gain is approximately 100.

Tone Control Stage

A standard Thordarson tone control with a 6C5 tube is used. Its advantage in recording is enormous. The characteristics of the amplifier can be adjusted to suit those of the recording head so that the resultant recording will have any desired characteristics. With the Thordarson tone control it is possible to increase or decrease the response of an amplifier at 10,000 or 100 cycles about 15 db.

The tone control potentiometers are mounted on the upper left hand corner of the speech console face.

Power Amplifiers

Both the master amplifier and monitor amplifier consist of 6N7 phase inverters driving push-pull 2A3's. The specific advantages of this arrangement are: 1) There are no coupling transformers; therefore, the frequency characteristics are limited only by the output transformers. 2) Low plate resistance tubes such as 2A3's are preferable for high-quality

The record files at left end of desk. The upper shelf holds 10-inch discs; the lower 12-inch ones.



reproduction through low-impedance speakers and recorders. 3) The lack of coupling transformers reduces the cost of the console considerably.

Through the use of an especially designed phase-inverter circuit, it has been possible to reduce distortion at full output to practically an unmeasurable degree, and, at the same time, to obtain the essential 60-volt grid drive necessary for the 2A3's.

Needless to say, it is exceedingly important that the phase-inverter circuits be balanced by actual voltage measurements, for a poorly balanced phase inverter can cause very serious distortion. One thing to remember is that the plate emission of no two 2A3's is exactly alike; therefore, once these calibrations have been made, the tubes must not be changed unless the amplifier is rebalanced.

Connections between the potentiometers and keys on the front panel and the sub-deck wiring are made with shielded wires. The key switches are Western Electric built. The chassis lacks about one inch of being as wide as the opening in the back of the cabinet. Along the side of the cabinet in this opening are placed a series of terminals to which the low-impedance inputs and outputs of the amplifier are connected. Since the amplifier is permanently placed on the desk, the high-impedance lines are connected directly from the pickups and the receiver to the keys.

Outputs

The plates of the monitor amplifier 2A3's are connected directly to the speaker which is, in this case, an electro-dynamic type with a self-contained output transformer. The plates of the master ampli-



The speaker end of desk, made of $\frac{3}{4}$ " plywood. Note heavy 2 by 3 base which leaves foot room around edges.



Cueing in a record. This view shows details of the bass reflex speaker inclosure, with lower port. Speaker cavity adjustment is covered in text.

fier 2A3's are connected to a tapped impedance output transformer which is connected to several key switches. These output switches are mounted in the upper right hand corner of the speech console face. The first of them operates the remote line input, mentioned briefly before in regard to the input circuits. This line has an impedance of 500 ohms. It enters a two-position key in such a fashion that it may either go through a step-up ratio transformer and to the input circuit, or be switched directly to the 500-ohm termination of the master amplifier. This circuit makes possible the recording of programs originating at a remote point or the playing of programs at a remote point which are originating at the console.

The purpose of the second key is to switch a pair of monitoring earphones from the output of the master amplifier to the remote line input. In this fashion, a program which is being recorded can be heard without the use of the monitoring speaker, and the remote pickup can be monitored without the use of the amplifier. The 15-ohm output of the master amplifier is connected to the third key. This key makes connections with the recorder which has a 15-ohm impedance, or with a lug termination, included for convenience in case such an output should be needed. The fourth key similarly connects the 4- and 8-ohm outputs of the master amplifier to lug connections.

[Continued on page 44]

The Cathode-Ray OSCILLOSCOPE

JAY BOYD

PART IV—SEEING PATTERNS ON THE SCREEN

◀ Having covered the theory and design of cathode-ray oscilloscopes in preceding issues, we can hook up that instrument to some of our pet apparatus, and watch it work. But first, let's make a few checks on the oscilloscope, itself.

Checking 'Scope Operation

Turn on the heaters, but allow them to warm up a minute with the brilliance control turned low. Then set the focus control near its middle position and turn up the brilliance control until a spot appears on the screen. Turn the focus control to the right or left until this spot becomes as small and sharp as possible, and at the same time keeping the brilliance fairly low. Place the spot in the center of the screen by adjustment of the beam centering controls.

The spot should never be allowed to remain in one position any longer than necessary, as this may soon burn a dead spot in the fluorescent material coating the screen. So be careful to always keep the beam in motion or reduce the brilliance below that required for visibility.

Having learned the operation of the four knobs controlling the beam; that is, brilliance, focus, vertical and horizontal centering, we are now ready to try the saw-tooth oscillator.

Switch the free horizontal deflection plate to the horizontal amplifier and its grid to the saw-tooth oscillator—its normal position. Advance the horizontal gain control and the spot should become a horizontal line as the beam is swept back and forth across the screen. The synchronization control should be turned to the left.

Since the electron stream must now cover a much greater screen area than when not deflected, it will be necessary to advance the brilliance control to maintain a visible line. The rough and fine frequency controls may be manipulated, but won't show much effect on the horizontal line until the frequency is reduced to 15 cycles per second or less, or until a signal is applied to the vertical plates.

Before placing an a.c. signal on the vertical plates,

we may check vertical deflection of the beam by application of any convenient d. c. voltage of 20 to 70 volts. Connect the positive to the unamplified vertical binding post and negative to ground. Switch the free vertical plate to this binding post and the beam should shift upward. If the d.c. voltage is known, we can ascertain the deflection sensitivity of the instrument, which will be useful in future testing.

And while about it, we might also test the vertical amplifier. Switch the free vertical plate to this amplifier and apply a small signal to the vertical amplifier binding post. A positive d.c. signal will cause the beam to flick *downward* momentarily, after which it returns to the center of the screen. An a.c. voltage shifts the beam both upwards and downwards.

The reason a positive voltage causes a downward flick when using the amplifier is that the amplifier's output voltage is always opposite in sign (or 180° out of phase) to the signal applied on its grid. Also, a d.c. signal displaces the beam only momentarily because the amplifier is capacity coupled, being intended for amplification of d.c. signals. If it were intended to amplify a d.c. signal, or a.c. of very low frequencies, a direct-coupled amplifier would be necessary, and that's another headache.

Formation of Patterns

After having ascertained that the oscilloscope is functioning properly, we are ready to put it to work. When the instrument is properly connected to any type of electrical apparatus various types of patterns will be formed on the fluorescent screen. The shapes of these patterns show just how the apparatus is functioning.

The great variety of patterns produced are without number. We can show and explain only a limited number of the more frequent ones in this limited space. Every user will discover patterns that are "not in the book." So if he is to benefit most he must carefully study the way in which these patterns are formed, so the interpretation of unfamiliar patterns will be easy.

Tracing a Sine Wave

Let's begin by playing around with a common 60-cycle sine wave. Connect the vertical deflection plates to any convenient 60-cycle supply, either direct or through the vertical amplifier. If the particular 'scope is equipped with a "60-cycle test" binding post, wire this over to the vertical amplifier post and work through that amplifier.

With this signal on the vertical plates, and with the horizontal amplifier gain turned to zero, a thin, vertical line will be formed, extending an equal distance above and below the center of the screen.

With the horizontal plates connected to the saw-tooth oscillator (through the horizontal amplifier, of course) we may get any number of patterns, depending upon the frequency of the saw-tooth oscillator. But to make it easy, first adjust this oscillator to a frequency of nearly 60 cycles per second.

A pattern like that in Fig. 1 will appear, but it will wriggle like a worm as it changes its shape upon the screen. With the synchronous selector switch turned to the "internal" position, advance the synchronization potentiometer slowly until this wriggling suddenly stops.

Now the saw-tooth oscillator frequency is locked to the 60-cycle signal being observed. And if the frequency of the test signal should vary several cycles per second, the saw-tooth oscillator will follow it and remain locked to the frequency under test.

But let's study this simple pattern more closely and see how it is formed. Remember, the beam is being acted upon by *two* voltages; that from the signal and that of the saw-tooth oscillator.

The latter is frequently called the "timing" oscillator because it furnishes the "time" bases of the "graphs" we make on the c.r. screen. In the case given, its frequency is 60 cycles per second. Therefore, the time required for one cycle is 1-60th of a second.

Being saw-tooth in form, the voltage increases at a uniform time rate in one direction, drawing the electron beam across the screen. Then this voltage collapses instantly, returning the beam to the opposite side of screen and the cycle begins anew.

The beam, then, will move uniformly from one side of the screen to the other, this direction being from left to right in most oscilloscopes.

But at the same time, the beam is also shifted *up* and *down* by the signal voltage applied to the vertical plates. It is the combination of these two forces upon the beam, and their timing relationship, which causes the formation of patterns upon the screen.

At this point the reader may wonder why we see only *one* sine curve, knowing that 60 of these cycles occur each second. Yes, 60 traces really are made on the screen each second but the saw-tooth oscillator begins its cycle in synchronism with the signal on the vertical plates, so each trace lies exactly on top of the preceding one. Due to the persistence time of the screen and also our own eyes (the latter re-

taining an image for about a twelfth of a second), we see the pattern as a single trace.

Other Patterns from Same Signal


Now change the sweep frequency to 30 c.p.s. and you will find two cycles on the screen, as shown in Fig. 2. The sweep time is slower and the signal goes through two complete cycles for every one of the saw-tooth oscillator.

Set the s.t.o. at 120 c.p.s. and the pattern may look like Fig. 3 or Fig. 4, depending on just what part of the signal cycle the trace begins. Since the time is just one-half that required for a complete cycle, *two* horizontal sweeps are necessary to record a single cycle.

Next, set the s.t.o. for 180 c.p.s. and make the "pattern" shown in Fig. 5. If the foregoing pattern formation is not quite clear, repeat all the experiments until they are thoroughly understood, before going to more complex patterns.

As the s.t.o. frequency is varied, a number of other patterns are produced, many of these being pretty but having little practical value.

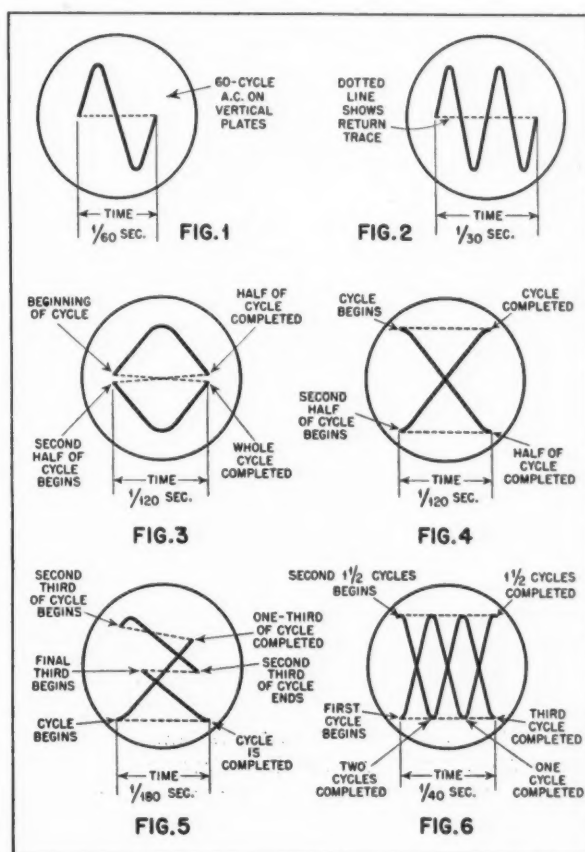One of these, where the s.t.o. frequency is neither an exact multiple nor sub-multiple of the signal frequency, is shown in Fig. 6. Here the sweep time is one-and-a-half times that of the signal (or two-thirds



Six sketches, explained in text, showing how various patterns are developed on the 'scope screen. Fig. 1 is a 60-cycle sine wave.

signal frequency—40 c.p.s. in this case), so we get three cycles on the screen for every two horizontal sweeps.

Patterns Not Requiring S.T.O.

In all foregoing examples, the graphs were drawn by plotting the test signal against a linear time base, the latter furnished by the saw-tooth oscillator. While the s.t.o. is necessary for about ninety percent of the work you will do, there are a number of applications which make its use unnecessary.

Trapezoidal patterns, so useful in transmitter checking, and Lissajous figures, from which frequency comparisons may be made, are produced by applying a.c. signals to both vertical and horizontal plates simultaneously. Receiver alignment is another special case, wherein the horizontal deflection is controlled by a frequency wobblator. But since we have just shown how a.c. wave forms are plotted against a linear time base, it is perhaps most logical to next consider audio amplifier checking by this method.

Checking Audio Amplifiers

Audio amplifiers may be checked on the oscilloscope by several methods but the set-up sketched in Fig. 7 allows us to see most easily what we wish to know. The audio oscillator may be simple or elaborate, so long as it will produce sine waves of good form. Its output does not have to be "flat" in respect to frequency.

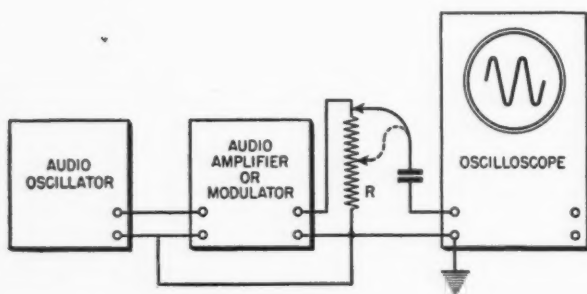


FIG. 7

Simple set-up, with audio oscillator, for checking the frequency response of audio amplifiers.

The amplifier feeds into a load having an impedance similar to that for which it was designed. The output may be fed either to the vertical plates or through the vertical amplifier. A coupling condenser of .25 μ fd. should be used when not working through the vertical amplifier. If a modulator is being checked it will be necessary to reduce the voltage to 50 or 75 volts by tapping the 'scope down on the load resistor R .

Horizontal deflection is obtained by using the s.t.o. for the "time" base, its frequency being adjusted to that of the audio amplifier. Using "internal" syn-

chronization, the pattern produced should be a perfect sine wave similar to that shown in Fig. 1. Halving the s.t.o. frequency will place two waves upon the screen. It is somewhat optional whether we see one, two, or three cycles, although the former is better when really going after "bugs."

Overloading an amplifier stage can be expected to produce flattened peaks, which may look like Fig. 8. But this overloading usually produces harmonics in the amplifier's output which may alter its waveform to appear something like Fig. 9.



FIG. 8



FIG. 9



FIG. 10

Fig. 8—Flattened peaks due to overloading. Fig. 9—Distortion due to presence of harmonics. Fig. 10—Distortion caused by harmonics and phase shift.

The exact appearance depends on several factors such as degree of overloading, percentage and relative amplitudes of all major harmonics, presence of regeneration, amplifier phase shift, adjustment of grid operating point, grid drawing current, saturation of audio transformers or other undesirables.

If the waveform is composed of fairly straight lines bending at well-defined angles like that of Fig. 10, use larger coupling condensers and check up plate and grid resistor networks; phase shift is occurring somewhere.

Correct analysis of distorted waves unquestionably requires a great deal of skill. But this does not detract from the oscilloscope's usefulness. If any distortion is found, the observer should next check the amplifier stage by stage until the fault is localized. It should then be easy to remedy the fault by substitution of any parts suspected, rechecking each change for improvement of pattern.

Balancing Phase Inverters

Whenever phase-inverter circuits are used it is essential that both sides of the circuit be perfectly balanced. To check circuits similar to Fig. 11, connect oscilloscope ground post at A and run B or C into the vertical amplifier. If resistor R is of correct value the signals taken from B and C will be of equal amplitude. Swinging the vertical amplifier to D and E should also show equal signals.

Similar signals will be found at F and G but this is misleading, since the voltage at one end of the transformer primary will be found at the opposite end of the winding, whether the tubes feeding this winding balance or not. Therefore, the overall output should be checked between H and I .

Single-ended Stages

Single-ended Class A stages produce very little distortion if operated with correct bias and are not over-driven. If correctly biased but overloaded, both peaks will be flattened as in *Fig. 8*. If improperly biased, flattening will occur on either the top or bottom peak, depending on whether the bias is too little or too much, and will produce patterns similar to *Fig. 13*.

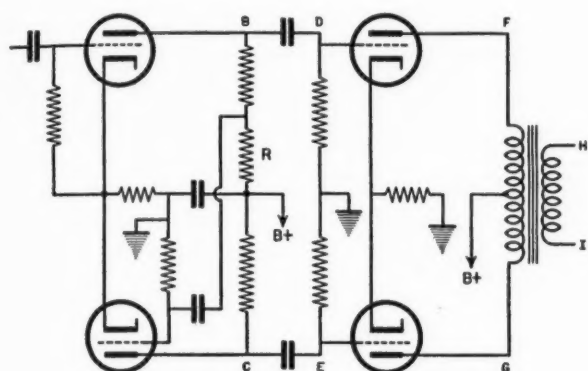


FIG. 11

Typical phase-inverter circuit, easily balanced by means of the oscilloscope. See text.

Another excellent test of linearity may be obtained from the set-up sketched in *Fig. 12*. A signal from the audio oscillator feeds the vertical plates through the oscilloscope's vertical amplifier, while the same signal deflects the beam horizontally, working through the audio amplifier under test, and not using the scope's horizontal amplifier.

If the amplifier being tested is operating linearly the pattern will appear as a straight diagonal line like *Fig. 14*. A pattern such as *Fig. 15* indicates slight overloading at the bottom, while the upper bend shows very bad overloading on the upper peak.

This test presupposes, of course, that the oscilloscope's amplifier is linear. Incidentally, the two amplifiers within the oscilloscope may be checked in a similar manner, which should be done before making the above test.

Checking for Hum Pickup

The oscilloscope is also useful for checking hum in amplifiers or other apparatus, where it is frequently difficult to distinguish between a.c. field pickup and power-supply ripple. With the equipment set up as in *Fig. 7*, but with the oscillator output turned down, an a.c. ripple may appear on the screen.

Remember that inductive field pickup will show up as a 60-cycle wave, while power-supply ripple will have a frequency twice that of the power line, or 120 c.p.s. So with the s.t.o. set for 60 c.p.s., if this ripple shows up as a single cycle the trouble is hum pickup in

an input transformer or wiring pickup in one of the first stages. But if two cycles are found, a need for more power supply filtering is indicated.

Another method is to run a 60-cycle a.c. signal on the horizontal plates with the audio amplifier running into the vertical amplifier. Sixty-cycle hum pickup produces a narrow oval, while power supply ripple shows a "figure 8" lying on its side.

Transmitter Testing

For checking the performance of radiophone transmitters the cathode-ray oscilloscope has no equal. Besides checking the speech and modulator stages as described, the overall output can be conveniently observed. *Fig. 16* shows a typical set-up which allows observation of either the r.f. envelope or formation of trapezoidal patterns, simply by flipping the usual horizontal selector switch, *SW1*, to either position.

Unless the transmitter is a broadcast job running after hours, a suitable dummy antenna should be substituted for the usual sky-wire. A two- or three-turn pickup loop placed near the final amplifier tank feeds the r.f. signal directly to the vertical plates *without* the amplifier.

A non-inductive voltage divider¹ from the modula-

¹A total resistance of around one megohm seems best in practice. Larger values produce phase shift, making meaningless patterns. If the voltage on the final amplifier runs around 1,000 volts, *R1* may be made up of two half-megohm, one-watt resistors, with about 50,000 ohms for *R2*. *R1* should consist of eight or ten 100,000-ohm, one-watt resistors for 2000-volt rigs. And keep those resistors off the operating table; they carry dangerous voltages!

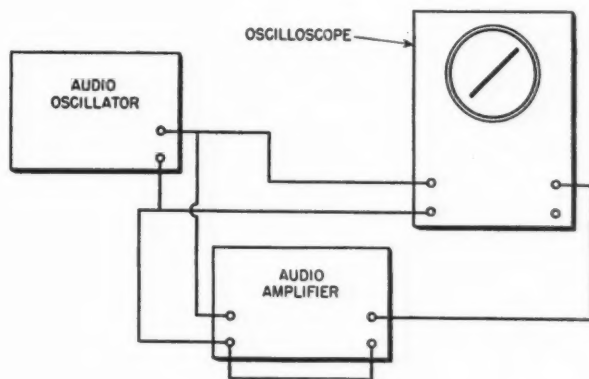


FIG. 12

Test set-up for checking linearity of audio amplifier.



FIG. 13



FIG. 14



FIG. 15

First pattern indicates improper biasing; second, perfect linearity; third, overloading at both ends.

tion transformer to ground and a tenth- or quarter-mike coupling condenser taps off the audio signal, furnishing horizontal deflection for trapezoidal patterns.

Throw the horizontal selector switch to the s.t.o. and turn on the transmitter. With no audio signal adjust the pickup loop until a ribbon of color shows across the screen. This pattern should look like *Fig. 17*, except in practice the individual r.f. cycles are so close together as to be indistinguishable. These individual cycles are shown in all sketches to make pattern formation more easily understood.

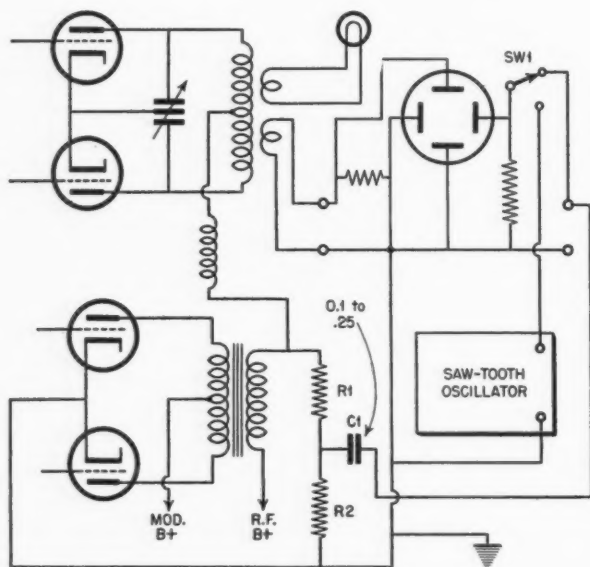


FIG. 16

Set-up for observing r.f. envelope at output of transmitter.

If the ribbon is bulged in spots like *Fig. 18*, there is hum on the carrier. This may be in either the speech or r.f., but if the former it should have been removed before testing the whole rig.

Now turn on the audio oscillator and watch the pattern change to the shape of *Fig. 19*, which shows a good, 100% modulated envelope. Use internal synchronization to make the "bumps" stand still.

Crank up the gain and notice narrowing of these individual "bumps," (*Fig. 20*) which seem tied to-

gether like link sausage. Those bright horizontal lines have no vertical deflection, telling us quite definitely that no carrier is being transmitted at these points. If the modulator is working beyond its capability, the peaks will also be found flattened.

Fig. 21 shows flattening of the peaks only, although the carrier is not over-modulated. This may indicate lack of sufficient grid excitation or incorrect grid bias on the final amplifier. Or it may mean that the modulator or one of the speech stages is being overtaxed.

Trapezoids and Triangles

The r.f. performance of 'phone rigs should also be checked by trapezoidal patterns which, generally speaking, indicate their performance more clearly than the envelope method. Their formation is brought about by deflecting the beam vertically by the r.f. and horizontally by the audio signal. This latter must be taken from the modulation transformer; if taken from a low-level stage, phase shift will be present and the patterns meaningless.

The way in which these patterns are formed should be apparent from a study of *Fig. 22*. A minute fraction of the audio power which modulates the carrier is used to swing the beam horizontally. Positive audio peaks increase the carrier amplitude to twice its unmodulated value, while negative audio peaks reduce the carrier to zero.

Positive audio peaks swing the beam to the left, negative to the right in most 'scopes. The opposite occurs in certain makes, reversing the pattern, but this is of no importance. If modulation is 100% the left side of the pattern will be twice the unmodulated value, while the vertical deflection is reduced to zero at the right. The increased brightness on this side of the triangle is due to the beam covering less area and does not indicate faulty adjustment.

When modulation is linear the sides of this triangle will be perfectly straight, although the height of the left (perpendicular) side does not have to be equal to the length of the other two.

Fig. 23 shows linear modulation of less than 100%, the pattern being a trapezoid rather than a triangle. This pattern is very useful for measuring modulation percentage. Carefully measure the maximum and

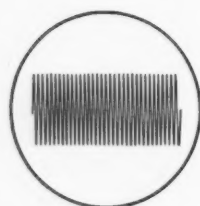


FIG. 17

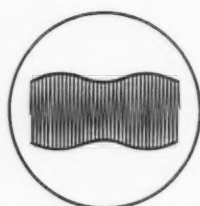


FIG. 18

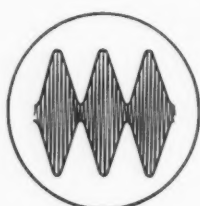


FIG. 19

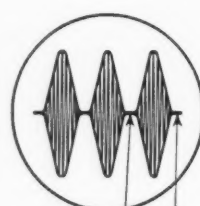


FIG. 20

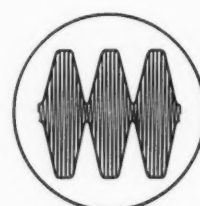


FIG. 21

From left to right: Pattern of carrier; hum on r.f. carrier; carrier 100% modulated; overmodulated carrier. In *Fig. 21*, the carrier is not overmodulated, but the flattened peaks indicate insufficient excitation.



FIG. 23



FIG. 24

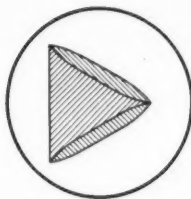


FIG. 25

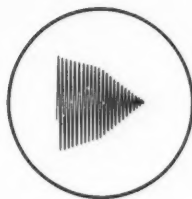


FIG. 26



FIG. 27

Trapezoidal patterns provide an easy means of checking the r.f. performance of phone rigs.

minimum height of the trapezoid and apply the following formula:

$$\text{Percentage modulation} = \frac{E_{\text{max.}} - E_{\text{min.}}}{E_{\text{max.}} + E_{\text{min.}}} \times 100$$

Fig. 24 shows a familiar pattern. The modulation is very good—but there's entirely too much of it! The bright "handle" shows the beam being dragged along by the audio signal but no vertical deflection, the carrier being completely cut off. Turning the audio gain knob to the left cures this sort of trouble.

Patterns such as Fig. 25 show improper phase relations between the audio and r.f. signals on the deflection plates; not a transmitter fault. If such occurs, increase C1 and reduce R1 and R2 in Fig. 16 and check ground connections.

Incorrect R.F. Amplifier Adjustment

In all foregoing examples there was no fault with the final r.f. amplifier; the trouble was over-modulation, overloaded speech or modulator stage, or faulty oscilloscope connection. But now let's take a look at some r.f. amplifiers that are ailing.

One common fault, lack of final grid driving power, shows up as Fig. 26. Note that modulation is linear

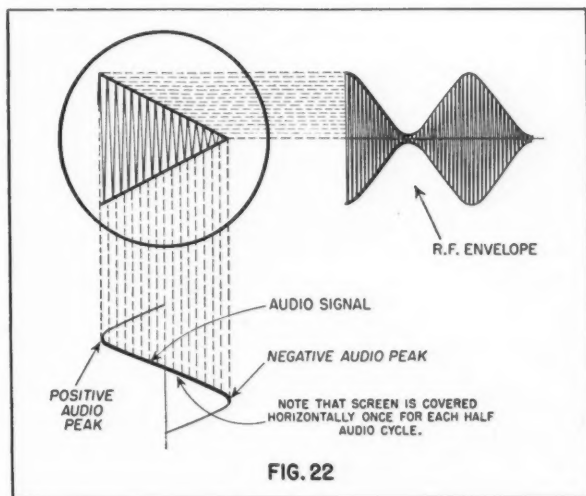


FIG. 22

Illustrating the manner in which a trapezoidal pattern is formed on the screen of an oscilloscope. See text.

up to about 60%, after which the r.f. peaks do not continue to rise in proportion to the audio voltage increase.

Sometimes we find a pattern like Fig. 27, in which
[Continued on page 44]

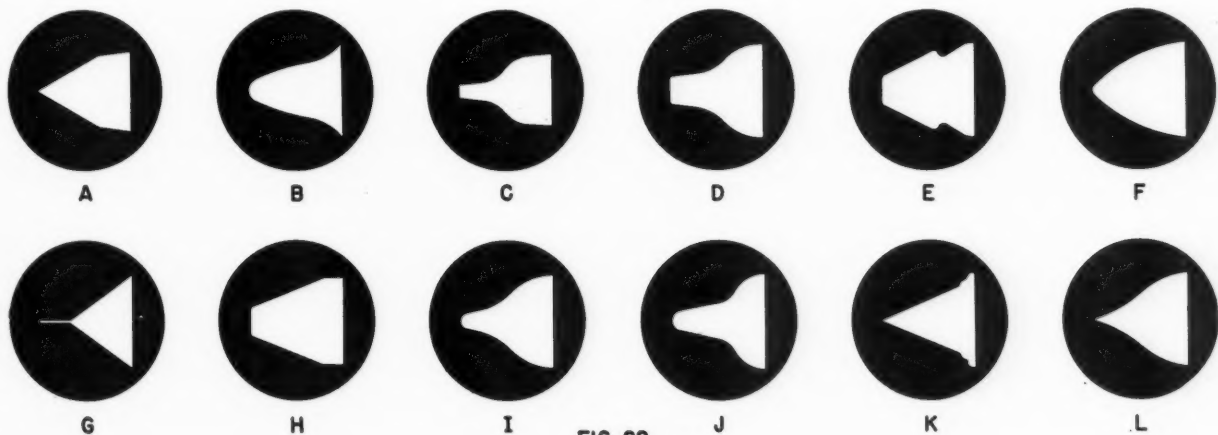


FIG. 28

Trapezoidal patterns. A: Insufficient Class C excitation. B: Improper neutralization. C: Distortion of negative peaks. D: Mismatched modulator. E: Regeneration in modulated stage. F: Insufficient excitation and bias. G: Overmodulation, with clipping of negative peaks. H: Plate modulation of s-g tube. I: Approximately 100% suppressor modulated. J: Suppressor modulated, with xtal in grid circuit. K: Whiskers (parasitics) on positive peaks. L: Well-adjusted grid or cathode modulation.

ELECTRONIC VOLTMETERS

Design and Application

JOHN H. POTTS

Within the past few years the electronic voltmeter has become widely accepted as one of the most simple, accurate and convenient instruments for measuring d-c. voltages in high-impedance circuits. Because of their wide use in the war effort, it is felt that a discussion of their design and applications will be of particular interest at this time.

Essentially, the electronic voltmeter differs from other vacuum-tube voltmeters in that it is designed to measure d-c. voltages only, rather than a.c., or both a.c. and d-c. By limiting its application to d-c. measurements, greater stability, accuracy and simplicity are readily obtained. These advantages are extended to a-c. measurements when the electronic voltmeter is employed in conjunction with a suitable rectifier. In addition, such instruments may be designed to serve as ohmmeters, as well as voltmeters, and in such applications enable measurement of extremely high resistances.

Fundamental Circuit

The fundamental circuit of one of the simplest types of electronic voltmeters is shown in Fig. 1. The meter in the cathode circuit of the triode indicates the cathode current. When a negative d-c. voltage is applied to the grid, the current decreases; when the grid terminal connects to the positive pole of the voltage source, the cathode current increases. Thus the meter may be calibrated to indicate both the *polarity* and the *magnitude* of the d-c. voltage under measurement.

Now let us see what design considerations are involved in this simple circuit. First, to complete the grid circuit when the voltmeter is disconnected from the circuit under test, the resistor R must be used. A high resistance, of the order of 10 megohms, is desirable, since the amount of circuit loading and the ohms-per-volt rating depend upon the value of resistance chosen. Thus, if R is 10 megohms and the meter is calibrated to read up to 5 volts, negative or positive, the sensitivity is equal to 2,000,000 ohms-per-volt. To duplicate this sensitivity using a microammeter and series multiplier, without the vacuum tube, would require a center-zero meter designed to deflect to full scale in either direction for a current of 2.5 microamperes. While such meters are available, they are costly and require considerable care in handling. By

using the electronic voltmeter circuit, a relatively insensitive meter—full scale deflection for 1 ma.—may be employed to provide equal sensitivity.

Damage due to accidental overload of the meter may be guarded against in the design. R_2 serves as a limiting resistor which prevents the plate current—and cathode current—from rising to extreme values should the applied positive grid voltage exceed the range of the meter. When the applied grid voltage is negative, the cathode current decreases, so the only effect of excessive voltage of negative polarity is to reduce the meter current to zero, so no damage can possibly result.

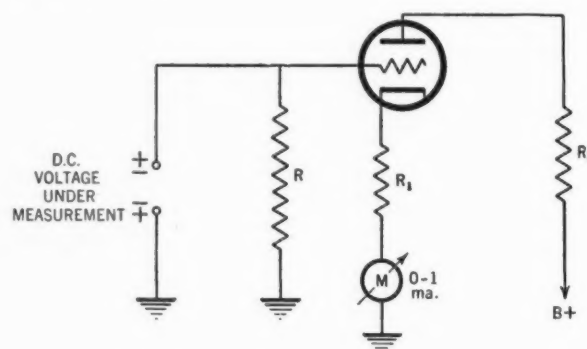


Fig. 1. Fundamental circuit of electronic voltmeter. Meter in cathode circuit indicates cathode current.

The use of the cathode resistor R_1 provides degeneration so that greater stability is secured. Minor variations in tube characteristics then have negligible effect upon the calibration of the meter. However, R_1 must not be too high in value, otherwise the tube will function as a detector and alternating voltages in the circuit under test will produce a rectified voltage which will register on the meter. To avoid this, the cathode resistor is so chosen that the bias applied enables the tube to operate as a Class A amplifier; and the plate voltage is selected to meet the range of the meter chosen.

Operating Point

A grid-voltage, plate-current characteristic of a typical triode is shown in Fig. 2. Note that the operating point is chosen at a grid bias which produces

a plate current of 0.5 ma. The voltages and resistances in the circuit are so chosen that this value of plate current occurs in approximately the middle of the straight portion of the E_g - I_p curve. Thus a 1-ma.

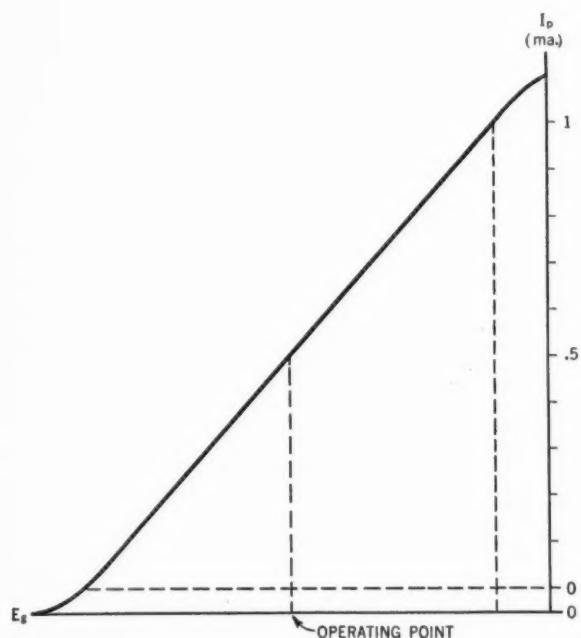


Fig. 2. Grid-voltage, plate-current characteristic of typical triode. Point is chosen which produces a plate current of 0.5 ma.

meter will read half scale when the electronic voltmeter is operating, but with no test voltage applied. If this point on the voltmeter scale is calibrated as zero, then a 5-volt change in a positive direction will cause the meter pointer to deflect full scale to the right, while a 5-volt change in a negative direction will cause a similar deflection in the opposite direction. Since operation is chosen over a straight portion of the curve, the scale is substantially linear. Further, it should be noted that, though changes in tube-operating voltages will cause an increase or decrease in the meter current, they will not affect the calibration, provided means are employed to readjust the plate current to 0.5 ma.

Preventing Rectification

Since the operating point chosen is such that the deflection in a positive direction is substantially the same as that in a negative direction for equal applied voltages of opposite polarity, it follows that a-c. voltages within the operating range of the voltmeter will not be rectified provided they are of pure waveform. If, however, the alternating voltage applied is unsymmetrical in form, or of sufficient magnitude to drive the bias beyond cutoff, rectification will result unless special precautions are taken. This is done by employing a simple resistance-capacity filter in the grid circuit, as shown in Fig. 3. In some commercial

instruments, the resistance is placed in the probe end of a shielded cable which plugs into the input terminals of the electronic voltmeter, as shown in Fig. 4. A small capacitance, of the order of .001 μ fd. is placed across the input circuit. The grounded shield forms the balance of the capacitive section of the filter circuit. Sufficient attenuation is thus secured to render negligible the effect of a strong a-c. component in the d-c. reading of the circuit under test. It is, of course, not entirely essential that the cable be shielded, but this is an advantage in guarding against stray pickup, due to the high impedance of the input circuit. By placing the resistor $R1$ in the probe, the shielded cable capacitance is effectively isolated from the circuit under test and it becomes possible to measure d-c. voltages in tuned circuits without introducing any more loading than would result if the isolating resistor alone were shunted across the circuit under test. Since it is possible to make $R1$ 1 megohm or more, measurements of d.c. in radio-frequency circuits are thus made possible without appreciable detuning effect.

Commercial Design

The complete circuit of a typical commercial design of electronic voltmeter, as employed in signal-tracing instruments of various types, is shown in Fig. 5. This circuit represents the design originally used in the RCA Rider Chanalyst. When used with the special cable and probe shown in Fig. 4, the ranges covered are as shown on the diagram. The filter condenser $C1$ is limited to a capacity of .001 μ fd. While a larger capacitance would provide greater attenuation of a-c. voltages arriving at the grid, it would also increase the time constant of the input circuit to the

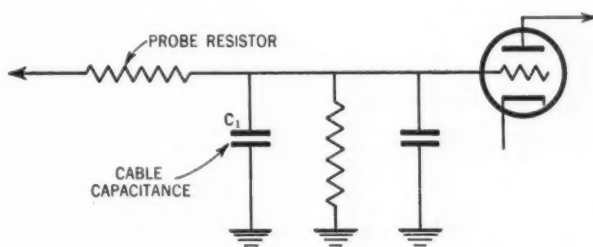


Fig. 3. Grid-circuit resistance-capacitance filter used to prevent rectification of a-c. voltages.

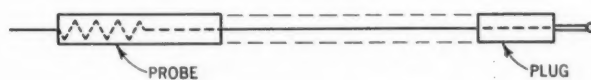


Fig. 4. In some designs the filter resistor is placed in the probe end of the shielded cable.

extent that the interval required for the charge accumulated on the condenser to leak off would become appreciable. During the period over which this charge is held, the voltage applied to the grid remains effective, so the meter pointer does not return to zero

until this charge is dissipated. This results in sluggish action which interferes with the utility of the device. There is no appreciable time lag of this sort when the values shown in the diagram are maintained.

The 5000-ohm rheostat shown in the cathode circuit is adjusted to give the required sensitivity for the particular tube chosen. When properly adjusted, the meter pointer will rise to half-scale deflection as soon as the tube has reached operating temperature, and will deflect to full scale for an input voltage of 5 volts (applied through the 1-megohm probe) in either a positive or negative direction. In the latter direction, the deflection is not quite full scale, since the tube bias does not reach cutoff. Once adjusted, this rheostat seldom requires change when replacement tubes are substituted, except when the replacement differs widely in characteristics from that for which the original calibration was made. Changes in power-supply voltage will affect the zero setting; compensation for these changes is made by readjusting the 10,000-ohm zero adjustment. The normal applied plate voltage (at the tube plate) is 70 volts.

This design of electronic voltmeter has outstanding advantages in that it permits measurements of either positive or negative voltages without regard to the polarity of connection of the voltmeter. The ground connection of the electronic voltmeter is simply connected to the corresponding ground connection of the apparatus under test and the probe may be moved from circuit to circuit, without the operator needing to know the polarity of the voltage under test. Further, the magnitude of the voltage is likewise of small concern. For, if the voltmeter is switched to the 5-volt scale and the voltage across the circuit under test is as much as 500, no damage to the meter will result. The maximum current which will be produced in the cathode circuit of the tube, and which passes through the meter, is approximately 8 ma., which does not overload a 1-mil. meter enough to bend the pointer. And, when overvoltage of any magnitude in a negative direction is applied, the result is simply to reduce the meter current to zero.

Laboratory Design

These advantages are obtained at a sacrifice of

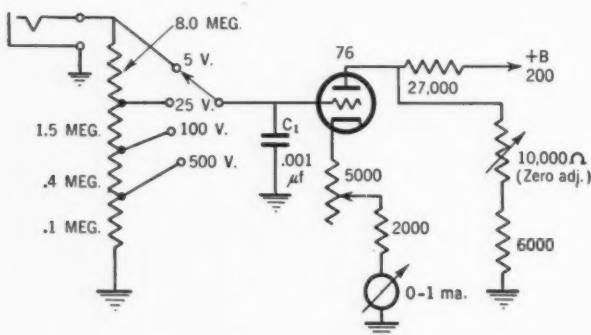


Fig. 5. Circuit of typical commercial design of electronic voltmeter, as used in signal tracing.

the accuracy and readability which would result were the full scale of the meter to be used, and means were employed for reversing the polarity. While the advantages greatly outweigh the disadvantages when an electronic voltmeter of this design is employed for trouble-shooting in maintenance work, for laboratory applications a design utilizing the full range of the meter is undoubtedly preferable. Although the polarity of the voltage must be known, a reversing switch enables such adjustment with minimum effort.

A fundamental circuit of a laboratory type electronic voltmeter is shown in Fig. 6. This is a bridge arrangement in which V_1 and V_2 form two arms of a bridge and the sections of the potentiometer R_3 supply the other two arms. When R_3 is properly adjusted, the current flowing in the plate circuit of

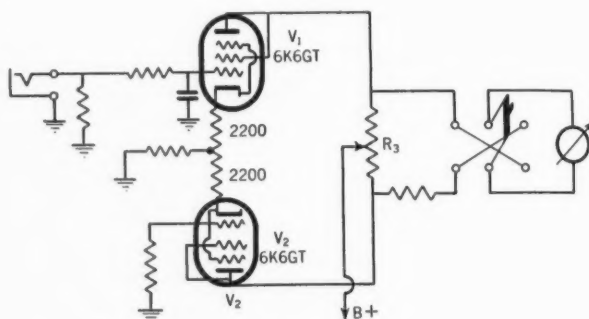


Fig. 6. Fundamental circuit of laboratory type electronic voltmeter of the bridge type, with V_1 and V_2 the two arms.

V_1 is balanced out by that flowing in the plate circuit of V_2 . Thus no current flows through the meter circuit and the meter reads zero. If the plate voltage increases due to a change in line voltage, the plate current of each tube should increase in like degree (provided their characteristics are identical) and therefore the bridge remains balanced and the meter indication is unaffected. For the same reason, changes in heater voltage should likewise produce no unbalance in the circuit. Practically, however, it is impossible to obtain conveniently tubes which match precisely, so some slight degree of unbalance due to changes in operating voltages must be expected. It is customary, in the more elaborate designs, to use some form of voltage regulator in the power-supply circuit, such as an Amperite or a special voltage-regulating transformer. An exceptional degree of stability is then secured.

It will be noted that V_2 serves solely as a means of balancing out the normal quiescent plate current in the measuring tube, V_1 , when no external voltage is applied to the grid of V_1 . However, when the test probe of V_1 is connected to a d-c. voltage source and a positive voltage is applied to its grid, the current in the plate circuit of V_1 is increased and consequently the cathode voltage is likewise increased. The increase in plate current upsets the balanced state due to the bridge arrangement, causing a meter indication. This reading is further increased because the unbal-

ance due to the increase in the plate current of $V1$ is further augmented by a decrease in the plate current of $V2$ (due to an increase in cathode voltage). Thus the action is somewhat regenerative and greater sensitivity is thus obtained.

It might be pointed out that the need for the reversing switch to change the meter polarity might be avoided by interchanging the input leads and re-adjusting the meter to read full scale and deflect in reverse direction for negative voltages. While this could be done, it would be necessary to isolate all circuits from grounds, otherwise in measuring high negative potentials the case of the instrument would be "up in the air" and a severe shock might be thus obtained. Such contingencies are avoided when the case is grounded and the reversing switch is employed in the manner shown.

Resistance Measurement

The application of this device to the measurement of resistances is obtained in the manner illustrated in Fig. 7. A voltage E , sufficient to produce full-scale deflection of the electronic voltmeter, is applied through the calibrating resistor R to the input circuit of the electronic voltmeter. Since the input circuit resistance is extremely high in comparison with that of the calibrating resistor R , no appreciable voltage drop occurs. But when an unknown resistor, R_x , is shunted across the input circuit, as shown, the voltage applied to the electronic voltmeter input is reduced so that the input voltage E_i , resulting, is determined by the formula

$$E_i = E \left(\frac{R_x}{R_x + R} \right)$$

whence the value of unknown resistance producing any measured input voltage may be readily calculated.

It has been stated that the input resistance of the electronic voltmeter is extremely high in comparison with the calibrating resistor R of Fig. 7. In order to obtain such a condition, it is necessary to operate $V1$ and $V2$ far below their rated voltages. When the heater voltage is reduced to approximately 5 volts and the plate voltage is limited to 60 volts, and is further reduced by the cathode bias, lowering of input resistance due to ionization of gas particles is reduced to such degree that an input resistance of the order of thousands of megohms is readily realized. Thus it becomes possible to measure resistances of the order of hundreds of megohms in the manner shown in Fig. 7.

In multi-range ohmmeters, one annoying characteristic of most conventional designs has been the need to readjust the zero setting when switching from a high range to a low range, and vice versa. This is due to the change in current drain on the test battery, causing a varying voltage drop across the internal resistance of the battery. By using an electronic voltmeter in the resistance-measuring circuit diagrammed in Fig. 7, the zero setting does not require readjustment when switching from range to range.

This is due to the fact that the drain on the battery is practically nil, except when the unknown resistor is under test, because the input circuit of the voltmeter presents a constant high impedance termination

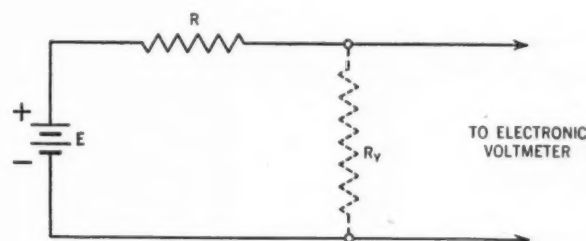


Fig. 7. Additional circuit employed with electronic voltmeter for making resistance measurements.

to the measuring circuit. However, it must be pointed out that some inaccuracy will result if a run-down battery is used in the circuit. Though the open-circuit voltage remains substantially unaffected by the increase in the internal resistance of the battery, this resistance is added to that of the resistor under test and may cause serious errors when very low values of resistance are measured. For higher resistance ranges, of course, no trouble results. It is convenient to avoid this trouble by checking the condition of the battery by noting the reading obtained from a low value resistor of known resistance, say 10 ohms or less, and to replace the battery when the reading obtained deviates appreciably from the known value.

VoltOhmyst Jr.

One of the most widely known types of electronic volt-ohmmeters, incorporating most of the features described above, is the RCA VoltOhmyst Jr., the schematic of which is given in Fig. 8. This instrument measures d-c. voltages in six ranges, from 3 to 1000 volts, full scale, with a constant input resistance of 10 megohms (this becomes 11 megohms when the 1-megohm resistance in the probe is added); a-c. volts (at 1000 ohms-per-volt) in 5 ranges from 10 to 1000 volts, full scale; and ohms in 6 ranges, from 10 ohms to 10 megohms, center scale. This means that the effective range as an ohmmeter covers from 0.1 to 1000 megohms.

The meter used has a 200-microampere movement. This sensitivity is required because of the low operating voltages employed. Note that the heater voltage for the 6K6GT's is only 5.7 volts and the total output voltage of the high-voltage section of the power supply is only 60 volts. The effective plate voltage is less than this value, since the cathodes are "up in the air" 30 volts. These low operating potentials make for the high input resistance required in the ohmmeter circuit.

A polarity reversing switch, $S2B$ and $S2C$, enables the input circuit to remain grounded regardless of the polarity of the voltage in the circuit under test.

Radio-Frequency Measurements

It should be particularly emphasized that the input resistor of the electronic voltmeter must be open-circuited when this rectifier is employed, otherwise the sensitivity of the instrument will be appreciably reduced. The "contact" potential of the rectifier will

ment for a.c., which must be done in any event. The scale will be fairly linear and the readings will be proportional to the positive peak of the voltage being tested. This will cause no error in measuring sine waves, but inaccuracies will result if complex waves are being measured. For higher voltage ranges, where the sensitivity must be reduced, the input circuit of the electronic voltmeter may be used in the normal manner, using the range switch and voltage divider resistors just as for measuring d.c. voltages. For the higher voltages, the increase in output voltage of the rectifier will be essentially proportional to the magnitude of the voltage being measured, so the readings will follow a linear scale.

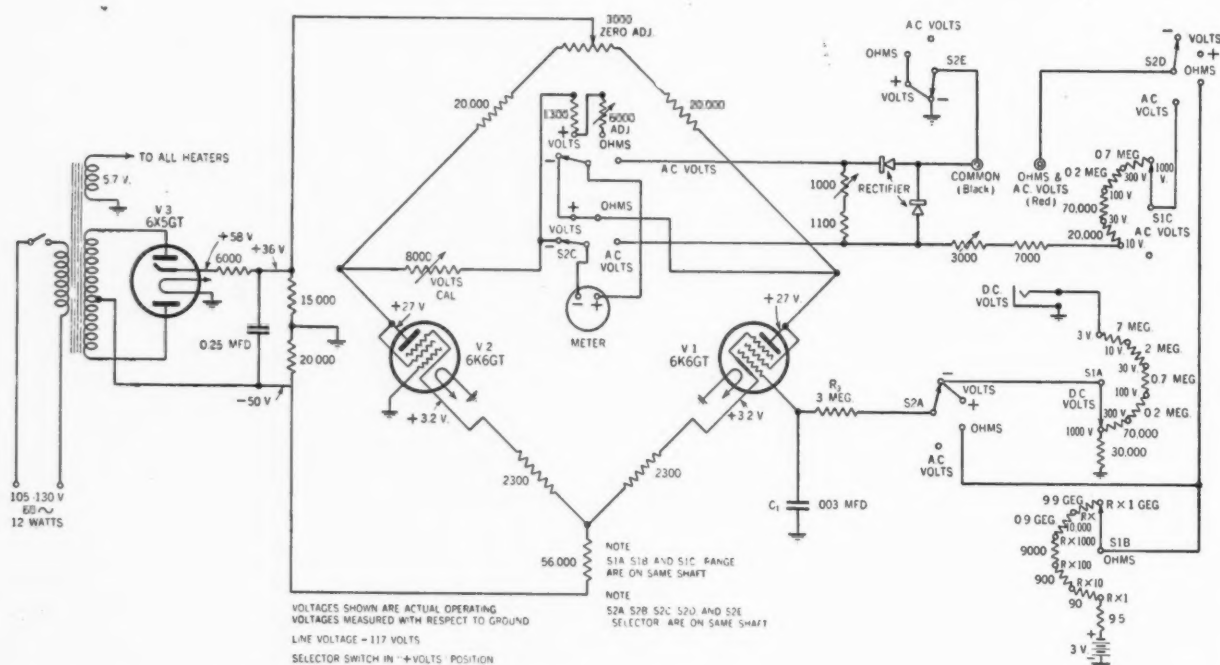



Fig. 8. Schematic of the RCA VoltOhmyst Jr. electronic volt-ohmmeter. It measures d-c. voltages in six ranges, a-c. volts in five ranges, and ohms in six ranges, as indicated in the diagram. Its effective range as an ohmmeter is from 0.1 to 1000 megohms. Note that the cathodes of V1 and V2 are up in the air to the extent of 30 volts.

RADIO DESIGN WORKSHEET

No. 3—TUNED R-F CIRCUITS

SIMPLE TUNED CIRCUIT

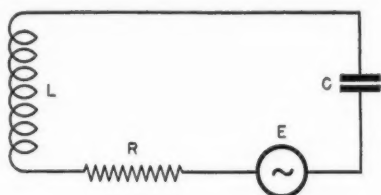Problem 1:—To explore some of the characteristics of a simple tuned circuit. The accompanying figure illustrates a simple series tuned circuit.



Solution:—The reactance of the circuit is:

$$X = 2\pi fL - \frac{1}{2\pi fC}$$

And the impedance is: $Z = \sqrt{R^2 + X^2}$

At resonance $2\pi fL = \frac{1}{2\pi fC}$ and $X = 0$

Hence $Z = R$

In television and other applications the phase of the current flowing in the circuit is of considerable interest. To determine the relation between phase and current amplitude for a constant applied or induced voltage, let I_0 be current at resonance and I the current at any other frequency. Then:

$$I_0 = \frac{E}{R}$$

At any other frequency, f , $I = \frac{E}{\sqrt{R^2 + X^2}}$

$$\text{Let } K = \frac{I}{I_0} = \frac{R}{\sqrt{R^2 + X^2}} = \frac{1}{\sqrt{1 + \tan^2 \theta}}$$

where θ = phase angle between I and I_0

$$\text{Then } \theta = \pm \tan^{-1} \frac{\sqrt{1 - K^2}}{K} \quad (1)$$


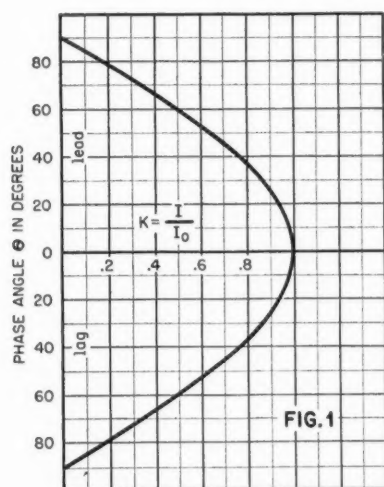


Fig. 1 illustrates the relation between phase and amplitude of current I as percent of I_0 as found from equation (1)

PASSBAND TUNED CIRCUIT

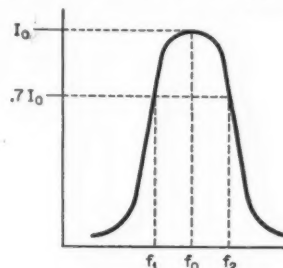Problem 2:—To determine conditions for constant passband of tuned circuit as frequency is varied.

Solution:—Define passband as frequency difference between points of 0.7 maximum response (i.e., 3-db.



loss). From Fig. 1, referred to in Problem 1, it will be noticed that at 70% of maximum response the phase angle is 45° and the resistance and reactance components of the tuned circuit impedance are equal.

$$\Delta f = f_2 - f_1$$

Now the shape of the resonance curve is due to the ratio $\frac{R}{2f_0L}$ instead of R alone. This quantity is often called the *decrement* of the circuit. To derive this relation, we know that at $.7 I_0$:

$$2\pi f_1L - \frac{1}{2\pi f_1C} = -R$$

$$2\pi f_2L - \frac{1}{2\pi f_2C} = R$$

Multiply these equations by $2\pi f_1C$ and $2\pi f_2C$ to obtain:

$$4\pi^2 f_1^2 LC - 1 = -2\pi f_1CR \text{ or } C(4\pi^2 f_1^2 L + 2\pi f_1R) = 1$$

$$4\pi^2 f_2^2 LC - 1 = 2\pi f_2CR \text{ or } C(4\pi^2 f_2^2 L - 2\pi f_2R) = 1$$

$$\text{Whence } 4\pi^2 f_1^2 L + 2\pi f_1R = 4\pi^2 f_2^2 L - 2\pi f_2R$$

$$R(2\pi f_2 + 2\pi f_1) = 2L(2\pi^2 f_2^2 - 2\pi^2 f_1^2)$$

$$\frac{R}{2L} = \frac{2\pi^2 f_2^2 - 2\pi^2 f_1^2}{2\pi f_2 + 2\pi f_1} = \pi \frac{(f_2^2 - f_1^2)}{(f_2 + f_1)} = \pi(f_2 - f_1)$$

$$\frac{R}{2f_0L} = \pi \frac{(f_2 - f_1)}{f_0}$$

$$\therefore \text{Decrement } \delta = \frac{R}{2f_0L} = \frac{\pi \Delta f}{f_0} = \pi R \sqrt{\frac{C}{L}}$$

$$\frac{R}{2L} = \pi \Delta f$$

$$\Delta f = \frac{Rf}{2\pi fL} = \frac{f}{Q} \text{ where } Q = \frac{2\pi fL}{R}$$

If $Q = Kf$ where K is a constant, then Δf is constant with varying frequency.

$$\text{Now: } Q = \frac{2\pi fL}{R} \frac{K'f}{R}$$

If R is constant for all frequencies involved, and L likewise, then $Q = K''f$ and $\Delta f = K'''$.

Therefore, for a capacitatively tuned circuit, the passband will remain constant if R is constant.

One means of approximating this condition is to add to a high Q circuit additional resistance, the value of which is large compared to the variation of resistance with frequency.

Q. & A. STUDY GUIDE

—Theory and Practice

CONTINUED FROM MARCH ISSUE

181. Under what load conditions will a vacuum tube have the highest ratio of power output to plate circuit d.c. input?

The voltage and current must be in phase. Maximum instantaneous power is delivered when the product of the maximum values of E and I is maximum; maximum average power is equal to one-half the value of the maximum product of E and I .

182. Under what load conditions will a vacuum tube produce its greatest output?

When the external load resistance is equal to the internal resistance of the tube.

183. What is the chemical composition of the active material composing the negative plate of a lead-acid type storage cell?

A lead oxide paste pressed in a lead-antimony alloy frame or grid; when the battery is charged with direct current the oxide is changed to pure lead, of a spongy consistency.

184. What is the chemical composition of the active material composing the negative plate of an Edison type storage cell?

Finely divided iron powder placed in thin rectangular pockets of steel frames or grids.

185. What is the chemical composition of the active material composing the positive plate of a lead-acid type storage cell?

A lead oxide paste which is changed, on charging the battery with direct current, to lead peroxide assuming the oxygen freed from the negative plates on charging.

186. How does a primary cell differ from a secondary cell?

A primary cell (i.e. dry cell) cannot be recharged once it becomes exhausted (unless provided with new electrodes and new electrolyte) whereas in a secondary cell (i.e. storage battery) the process of changing chemical energy into electrical energy with a resultant flow of current is reversible. The storage cell, when exhausted may be charged by an external current in reverse polarity to the current delivered from the cell.

187. What is the chemical composition of the active material composing the positive plate of an Edison type storage cell?

Nickel oxide in the form of round tubes.

188. What is the chemical composition of the electrolyte used in an Edison type storage cell?

A solution of potassium hydroxide.

189. What is the chemical composition of the electrolyte of a lead-acid storage cell?

A dilute solution of sulphuric acid.

190. Why is a 45 volt, dry cell "B" battery generally considered unsatisfactory for use when the terminal voltage has fallen to approximately 36 volts?

When the terminal voltage of a 45-volt dry cell "B" battery has fallen to approximately 36 volts, normal "local action" or deterioration, together with polarization will have taken place and increased the internal resistance of the battery, reducing the current available to an unsatisfactory value for general purposes.

191. What is "polarization" as applied to a primary cell and how may its effect be counteracted?

Polarization is the formation of hydrogen gas bubbles around the positive electrode of the primary cell. These bubbles decrease the electrode's surface in contact with the electrolyte, increasing the cell's resistance. In addition, a minute voltage is set up between the hydrogen gas and the electrode opposite to the useful voltage of the cell, thereby reducing the output voltage. Polarization cannot be permanently overcome, but may be temporarily remedied by placing chemicals in the cell to supply oxygen (i.e. manganese dioxide) which react with the hydrogen to form water. Also, idleness will diffuse the gas somewhat.

192. Describe three causes of a decrease in capacity of an Edison type storage cell.

(1). Local deterioration upon standing idle for any length of time. (2). Temperature: a nickel-iron cell has a critical temperature which varies with the discharge rate. At a normal rate of discharge this is slightly above the freezing point of water. Lower temperatures reduce the capacity. (3). Gradual reduction of the density of the electrolyte with use.

193. What is the cause of the heat developed within a storage cell under charge or discharge condition?

The flow of electric current through the electrolyte generates heat.

194. How should sulphuric acid and water be mixed, if it becomes necessary to do so in order to replace lost electrolyte?

The acid should be poured slowly into the water and stirred constantly. *Never pour water into acid.*

[Continued on page 44]

F. X. RETTENMEYER

RCA Manufacturing Co., Inc.

Third of a series of bibliographies for design engineers, research workers and students allied with the war effort.

3—CRYSTALLOGRAPHY

IN PREVIOUS ISSUES:

Aviation Radio, May, 1942

Frequency Modulation, June, 1942

Dynamical Determination of the Elastic Constants and Their Temperature Coefficients for Quartz—J. V. Atanasoff and P. J. Hart—*Physical Review*, Vol. 59, January 1, 1941, Page 85.

Contour-Mode Vibrations in Y-Cut Quartz Crystal Plates—G. Builder and J. E. Benson—*AWA Technical Review*, Vol. 5, No. 5, 1941, Page 181.

The Pierce Piezo-Electric Oscillator—H. Jefferson—*Wireless Engineer*, Vol. XVIII, No. 213, June, 1941, Page 232.

Oscilloscope Patterns of Damped Vibrations of Quartz Plates and Q-Measurements with Damped Vibrations—H. A. Brown—*Proceedings IRE*, April, 1941, Page 195.

A Quartz Crystal Cutting and Lapping Machine—B. Butler—*Electronics & Television & Short Wave Radio*, May, 1941, Page 204.

A Determination of the Elastic Modulus S-13 of Beta-Quartz—A. W. Lawson—*Physical Review*, Vol. 59, April 1, 1941.

The Elastic, Dielectric and Piezo-Electric Constants of Heavy-Water Rochelle Salt—A. N. Holden & W. P. Mason—*Physical Review*, Vol. 57, January 1, 1940, Page 54.

Quartz Crystals—C. F. Baldwin—*G. E. Review*, Vol. 43, No. 5, May, 1940, Page 188.

Low Temperature Coefficient Quartz Crystals—W. P. Mason—*Bell System Technical Journal*, January, 1940.

The Generation for Television of Horizontal Synchronizing Pulses from Vertical Pulses by Means of Impulse Excitation—J. B. Sherman—*Proceedings IRE*, September, 1940, Page 406.

A General Reciprocity Theorem for Transmission Lines at Ultra-High Frequencies—R. King—*Proceedings IRE*, May, 1940, Page 223.

A Note on the Determination of the Equivalent Electrical Constants of a Quartz-Crystal Resonator—G. Builder—*AWA Technical Review*, Vol. 5, No. 1, 1940.

The Development and Application of Quartz Crystal Technique, *Electronics & Television & Short-Wave Radio*, September, 1940, Page 403.

Quartz Crystals—Their Piezo-Electric Properties and Use in Control of High Frequency—C. F. Baldwin—

General Electric Review, Vol. 43, No. 6, June, 1940, Page 237.

Electro-Acoustic Reactions with Special Reference to Quartz Crystal Vibrators—A. T. Starr—*Wireless Engineer*, June, 1940, Page 247.

Electro-Acoustic Reactions—A. T. Starr—*Wireless Engineer*, July, 1940, Page 303.

The Location of Hysteresis Phenomena in Rochelle Salt Crystals—W. P. Mason—*Physical Review*, Vol. 58, October 15, 1940, Page 744.

Properties of Rochelle Salts, III—H. Mueller—*Physical Review*, Vol. 58, September 15, 1940, Page 565.

Finite Complexes in Crystals: A Classification and Review—A. F. Wells—*Philosophical Magazine* (Cambridge) and *Journal of Science*, August, 1940.

A New Quartz Crystal Plate, Designated G. T., which Produces a Very Constant Frequency Over a Wide Temp. Range—W. P. Mason—*Proceedings IRE*, Vol. 28, No. 5, May, 1940, Page 220.

On the Right- and Left-Handedness of Quartz and Its Relation to Elastic and Other Properties—K. S. Van Dyke—*Proceedings IRE*, Vol. 28, No. 9, September, 1940, Page 399.

Equivalence of Two Piezo-Electric Oscillating Quartz Crystals of Symmetrical Outlines with Respect to a Plane Perpendicular to an Electrical Axis—I. Koga—*ETJ*, Vol. 3, No. 8, August, 1939, Page 185.

Research Items, *ETJ*, Vol. 3, No. 6, June, 1939, Page 142.

Quick Building-up of the Electron-Coupled Quartz Oscillator—T. Hayasi and S. Akasi—*ETJ*, Vol. 3, No. 10, October, 1939, Page 219.

Crystal Control for Portable and Semi-Portable Broadcast Pick-up Transmitters—S. T. Carter—*Communications*, Vol. 19, No. 1, January, 1939, Page 14.

The Production of Quartz Resonators for the London-Birmingham Coaxial Cable System—C. F. Booth and C. V. Sayers—*The Post Office Electrical Engineer Journal*, Vol. XXXI, Part 4, January, 1939, Page 245.

Small Temperature Coefficient of Frequency of Quartz Plates—P. Modrah—*Wireless Engineer*, January, 1939, Page 6.

The Increase of X-Ray Reflection from Quartz Due to a Strong Electric Field—Y. Kakiuchi—*Physical Review*, Vol. 54, 1938, Page 772.

Transient Frequency Variation of Crystal Oscillator—I. Koga and M. Shoyama—*Electrotechnical Journal* (Inst.

RADIO-ELECTRONIC BIBLIOGRAPHY

- of Elec. Eng., Japan), Vol. 2, No. 9, September, 1938, Page 199.
- Comments on "The National Physical Laboratory's Notation for Piezo-Electric Quartz"—I. Koga—*Electrotechnical Journal* (Inst. of Elec. Eng., Japan), Vol. 2, No. 12, December, 1938, Page 287.
- Notation for Piezo-Electric Quartz, *The National Physical Laboratory*, 1938, Page 3.
- The Production of Rochelle Salt Piezo-Electric Resonators Having a Pure Longitudinal Mode of Vibration—N. C. Stamford—*Proceedings IRE*, Vol. 25, No. 4, April, 1937, Page 465.
- A Simplified Circuit for Frequency Substandards Employing a New Type of Low Frequency Zero-Temperature-Coefficient Quartz Crystal—S. C. Hight and G. W. Willard—*Proceedings IRE*, Vol. 25, No. 5, May, 1937, Page 549.
- The Harmonic Mode of Oscillation in Barkhausen-Kurz Tubes—W. D. Hershberger—*Proceedings IRE*, Vol. 25, No. 5, May, 1937, Page 564.
- A Voltage Stabilized High Frequency Crystal Oscillator Circuit—S. Sabaroff—*Proceedings IRE*, Vol. 25, No. 5, May, 1937, Page 623.
- Frequency Multiplication and Division—H. Sterky—*Proceedings IRE*, Vol. 25, No. 9, September, 1937, Page 1153.
- X-Ray Studies of Crystals Vibrating Piezo-Electrically—C. V. Bertsch—*Physical Review*, Vol. 49, 1936, Page 128.
- Phenomena in High-Frequency Systems*—A. Hund—McGraw Hill Book Co., New York, Chapter VIII, 1936.
- The Piezo-Electric Resonator and the Effect of Electrode Spacing Upon Frequency—W. G. Cady—*Physics*, Vol. 7, No. 7, July, 1936, Page 237.
- A Treatise on Piezo-Electric Quartz Crystals—W. F. Diehl—*Broadcast News*, October, 1936 and December, 1936.
- A New Piezo-Electric Quartz Crystal Holder with Thermal Compensator—W. F. Diehl—*RCA Review*, Vol. 1, October, 1936, Page 86.
- Elastic Vibration of Quartz—G. W. Willard—*Bell Lab. Record*, April, 1936, Page 250.
- Multi-Frequency Radio Transmitter—J. B. Bishop—*Bell Lab. Record*, April, 1936, Page 350.
- A Broadcast Frequency Measuring Set—W. M. Kellogg—*Bell Lab. Record*, 1936, Page 307.
- Radio on Germany's Latest Floating Island (Transatlantic Aircraft Depot Ship [Ostmark]), *Wireless World*, Vol. 39, July 31, 1936, Page 99.
- Notes on Piezo-Electric Quartz Crystals—I. Koga—*Proceedings IRE*, March, 1936, Page 510.
- Young's Modulus of a Crystal in Any Direction—I. Koga—*Proceedings IRE*, March, 1936, Page 532.
- A Determination of Some of the Properties of Piezo-Electric Quartz Resonators—K. S. Van Dyke—*Proceedings IRE*, April, 1935, Page 386.
- An Electromechanical Representation of a Piezo-Electric Crystal Used as a Transducer—W. P. Mason—*Proceedings IRE*, April, 1935, Page 1252.
- Quartz Crystal Filters—W. P. Mason—*Bell Lab. Record*, June, 1935, Page 305.
- Proper Frequencies of Piezo-Electric Quartz Crystals Excited in the Direction of Thickness—L. Bergman—*Annalen der Physik*, January, 1935, Page 553.
- Anomalous Dispersion of the Dielectric Constant of Rochelle Salt—G. Busch—*Helv. Phys. Acta.*, May, 1935, Page 31.
- Method of Testing Crystals for Piezo-Electricity—L. Bergman—*Phys. Zeits*, January, 1935, Page 31.
- Motion of a Bar Vibrating in Flexure—W. P. Mason—*Acoustical Soc. of Am. Journal*, April, 1935, Page 246.
- The National Primary Standard of Radio Frequency—E. L. Hall, V. E. Heaton, and E. G. Lapham—*U. S. Bureau of Standards Journal*, February, 1935, Page 85.
- 19A Transmitter for Private Airplanes—B. S. Blair—*Bell Lab. Record*, December, 1935, Page 136.
- Wind from Quartz Crystals—S. C. Hight—*Bell Lab. Record*, December, 1935, Page 121.
- Temperature Coefficients of Piezo-Electric Quartz Plates and Rods—R. Bechmann—*Hochfrequenztechn. U. Elektrotechnik*, November, 1934, Page 145.
- Optical Proof of Super Harmonics and of Oscillating Characteristics of Piezo-Quartz According to Debye and Sears Method and its Application for the Determination of Electric Wave Lengths—L. Bergmann—*Hochfrequenztechn. U. Elektrotechnik*, March, 1934, Page 83.
- Practical Operating Advantages of Low Temperature Frequency Coefficient Crystals—Baldwin and Bokovoy—*QST*, January, 1935.
- A Crystal Superheterodyne—G. F. Lampkin—*Communication & Broadcast Engineering*, Vol. 2, No. 9, September, 1935, Page 21.
- X-Ray Extension in Piezo-Electrically Oscillating Crystals—G. W. Fox and W. A. Fraser—*Physical Review*, Vol. 47, 1935, Page 899.
- Diffuse Scattering of X-Rays from Piezo-Electrically Oscillating Quartz—G. E. M. Jauncey and J. H. Deming—*Physical Review*, Vol. 48, 1935, Page 462.
- Multiple Laue Spots—C. C. Murdock—*Physical Review*, Vol. 45, 1934, Page 117.
- Multiple Laue-Spots from Aluminum Crystals—A. Komar and W. Obukhoff—*Physical Review*, Vol. 45, 1934, Page 646.
- The Perfection of Quartz and Other Crystals and Its Relation to Surface Treatment—R. M. Bozorth and F. E. Haworth—*Physical Review*, Vol. 45, 1934, Page 821.
- An X-Ray Study of Long-X-Cut Crystal (Quartz) Vibrating under the Transverse Piezo-Electric Effect—M. Y. Colby and S. Harris—*Physical Review*, Vol. 46, 1934, Page 445.
- Thermal Characteristics of Piezo-Electric Oscillating Quartz Plates—I. Koga—*Reports of Radio Research in Japan*, Vol. IV, No. 2, 1934, Page 1.
- Refracting Interferometer for Examining Modes of Vibration of Quartz Plates—H. Osterberg—*Review of Scientific Instruments*, May, 1934, Page 183.
- Circle Diagrams of Quartz Crystals (with English Abstract)—R. Usul—*Institute Electrical Engineers Journal*, Japan, March, 1934, Page 201.
- A 200 Kilocycle Piezo-Oscillator (Abstract)—E. G. Lapham—*Proceedings IRE*, January, 1934, Page 83.
- Development of Standard Frequency Transmitting Sets (Abstract)—L. Mickey and A. D. Martin—*Proceedings IRE*, February, 1934, Page 265.
- Quartz Crystal Controlled Oscillator Circuits—H. R. Meahl—*Proceedings IRE*, June, 1934, Page 732.
- Thermal Characteristics of Piezo-Electric Quartz Plates—I. Koga—*Radio Research*, July, 1934, Page 61.
- Measurement of a Strain Ratio in an X-Cut Quartz Crystal—M. Y. Colby and S. Harris—*Optical Soc. of America Journal*, August, 1934, Page 217.
- Interferometer Method of Measuring the Amplitude of Vibration of Quartz Bar Crystals—S. H. Cortez—*Optical Soc. of America Journal*, May, 1934, (Erratum [July])

RADIO-ELECTRONIC BIBLIOGRAPHY

- Electrical Filters Employing Quartz Crystals as Elements—W. P. Mason—*Bell System Technical Journal*, July, 1934, Page 405.
- Some Improvements in Quartz Crystal Circuit Elements—F. R. Lack, G. W. Willard, and I. E. Fair—*Bell System Technical Journal*, July, 1934, Page 543.
- Modes of Vibration of Piezo-Electric Quartz Plates—Y. Sakisaka and I. Sumato—*Inst. Phys. and Chem. Research*, October, 1934, Page 20.
- Temperature Coefficient of Quartz Oscillators—H. Straubel—*Zeits F. Techn. Physik*, December, 1934, Page 607.
- Piezo-Electric Microphone—A. L. Williams—*Journal of Society of Motion Picture Engineers*, 1934.
- Quartz Crystal Fundamentals—J. J. Wolfskill—*QST*, December, 1934, Page 37.
- Triple Interferometer for Distinguishing Flexural and Longitudinal Vibrations in Quartz—H. Osterberg—*Optical Society of America Journal*, January, 1933, Page 30.
- A 200 Kilocycle Piezo-Oscillator—E. G. Lapham—*U. S. Bureau of Standards Journal*, July, 1933, Page 59.
- Converse Piezo-Electric Effect in Mixed Crystals Iso-morphous with Rochelle Salt—S. Bloomenthal—*Physics*, May, 1933, Page 172.
- Piezo-Electric Properties of Tourmaline—W. Fox and M. Underwood—*Physics*, January, 1933, Page 10.
- The Interdependence of Frequency Variation and Harmonic Content, and the Problem of Constant-Frequency Oscillators—J. Groszkowski—*Proceedings IRE*, July, 1933, Page 958.
- Modes of Vibration of Piezo-Electric Crystals—W. H. Williams—*Proceedings IRE*, July, 1933, Page 990.
- A Piezo-Electric Loudspeaker for the Higher Audio Frequencies—S. Ballentine—*Proceedings IRE*, October, 1933, Page 1939.
- Vibrating Quartz Crystals and Their Sound Emission—K. Bucks and H. Muller—*Zeit Fur Hochfrequenztechnik*, July, 1933, Page 75.
- Notes on Crystals—E. H. Reitzke—*Radio Engineering*, September, 1933, Page 23.
- The Application of Methods of Geometrical Inversion to the Solution of Certain Problems in Electrical Resonance—W. G. Cady—*Proc. of the American Academy of Arts & Sciences*, Vol. 68, No. 10, September, 1933.
- Pierce Crystal Oscillations—K. Heegner—*Electrische Nachrichten-Technik*, September, 1933, Page 357.
- New Temperature Control Quartz Oscillators—R. Bechman—*Electrische Nachrichten-Technik*, September, 1933, Page 371.
- Tourmaline Oscillators—S. Matsumuar and S. Ishikawa—*Radio Research*, June, 1933, Page 1.
- Effect of Etching on the Relative Intensities on the Components of Double Laue Spots Obtained from a Quartz Crystal—M. Y. Colby and S. Harris—*Physical Review*, Vol. 43, 1933, Page 562.
- Laue Patterns from Thick Crystals at Rest and Oscillating Piezo-Electrically—J. M. Cork—*Physical Review*, Vol. 42, 1932, Page 749.
- X-Ray Reflections from a Quartz Piezo-Electric Oscillator in a Bragg Spectrograph—M. Y. Colby and S. Harris—*Physical Review*, Vol. 42, 1932, Page 733.
- Silvering Electrodes on Quartz Crystals (Brashear Process)—G. S. Parsons—*QST*, Vol. 16, March, 1932, Page 20.
- X-Ray Reflection from Inhomogeneously Strained Quartz—C. S. Barrett and C. E. Howe—*Physical Review*, Vol. 39, 1932, Page 889.
- Experimental Study of Parallel-Cut Piezo-Electric Quartz Plates—G. W. Fox and W. G. Hutton—*Physics*, Vol. 2, 1932, Page 443.
- Temperature Variations of the Frequency of Piezo-Electric Oscillations of Quartz—R. E. Gibbs and V. N. Thatte—*Philosophical Magazine*, October, 1932, Page 682.
- Modes of Vibration of Quartz Piezo-Electric Plates as Revealed by an Interferometer—W. D. Dye—*Royal Soc. Proc.*, October, 1932, Page 1.
- Experimental Determination of the First Piezo-Electric Modulus of Quartz—B. Nussbaumer—*Zeit fur Hochfrequenztechnik*, October, 1932, Page 781.
- First Piezo-Electric Modulus of Quartz from Determinations with a Quartz Resonator—A. Szekely—*Zeit fur Hochfrequenztechnik*, October, 1932, Page 560.
- Fundamental Crystal Control for Ultra High Frequencies—H. Strubel—*QST*, April, 1932, Page 10.
- Piezo-Electric Loudspeakers and Microphones—A. L. Williams—*Electronics*, 1932, Page 166.
- Interferometer Method of Studying Vibrations of Oscillating Quartz Plate—H. Osterberg—*Optical Society of America Journal*, January, 1932, Page 19.
- Quartz Crystal Resonators—W. A. Marrison—*Bell Lab. Record*, February, 1932, Page 194.
- Discussion on "Quartz Plate Mountings and Temperature Control for Piezo Oscillators"—V. E. Heaton and E. G. Lapham—*Proceedings IRE*, February, 1932, Page 1064.
- Crystal Control Applied to the Dynatron Oscillator—K. A. MacKinnon—*Proceedings IRE*, November, 1932, Page 1689.
- Thickness Vibrations of Piezo-Electric Oscillating Crystals—I. Koga—*Physics*, August, 1932, Page 70.
- Piezo-Electric and Di-electric Characteristics of Rochelle Salt—Von Erich Schwartz—*Electrische Nachrichten-Technik*, December, 1932, Page 481.
- Notes on Frequency Stability of Quartz Plates—L. B. Hallman, Jr.—*Radio Engineering*, February, 1932, Page 15.
- Some Experimental Studies of the Vibrations of Quartz Plates—(Abstract)—R. B. Wright and D. M. Stuart—*Proceedings IRE*, February, 1932, Page 182.
- Quartz Plate Mountings and Temperature Control for Piezo-Oscillators—V. E. Heaton and E. G. Lapham—*Proceedings IRE*, February, 1932, Page 261.
- Application of Quartz Plates to Radio Transmitters—O. M. Hovgaard—*Proceedings IRE*, May, 1932, Page 767.
- The Vibrations of Quartz Plates—R. C. Colwell—*Proceedings IRE*, May, 1932, Page 808.
- The Precision Frequency Measuring System of RCA Communications, Inc.—H. O. Peterson and A. M. Braaten—*Proceedings IRE*, June, 1932, Page 941.
- Thickness Vibration of Piezo-Electric Oscillating Crystals—I. Koga—*Radio Research*, September, 1932, Page 157.
- Recent Developments in Precision Frequency Control—D. E. Replogle—*Radio Engineering*, April, 1932, Page 29.
- Quartz Oscillator Wave Constants—E. G. Watts—*Radio Engineering*, September, 1931, Page 23.
- Oscillating Characteristics and Temperature Coefficient of Quartz Oscillators—H. Strubel—*Zeit fur Hochfrequenztechnik*, July, 1931, Page 14.
- Accurate Method of Measuring Transmitted Wave Frequencies at 5000 and 20,000 Kc.—E. L. Hall—*Proceedings IRE*, January, 1931, Page 35.

RADIO-ELECTRONIC BIBLIOGRAPHY

- Application of Piezo-Electric Crystals to Receivers—R. R. Batcher—*Electronics*, August, 1931, Page 57.
- Measurement of Temperature Coefficient and Pressure Coefficient of Quartz Crystal Oscillators—S. L. Brown and S. Harris—*Review of Scientific Instruments*, March, 1931, Page 180.
- A New Oscillator for Broadcast Frequencies—O. M. Hovgaard—*Bell Lab. Record*, December, 1931, Page 106.
- An Analysis of a Piezo-Electric Oscillator Circuit—L. P. Wheeler—*Proceedings IRE*, Vol. 19, No. 4, April, 1931, Page 627.
- Note on the Piezo-Electric Quartz Oscillating Crystals Regarded from the Principle of Similitude—I. Koga—*Proceedings IRE*, Vol. 19, No. 6, June, 1931, Page 1022.
- Performance of Piezo-Oscillators and the Influence of Decrement of Quartz on the Frequency Oscillation—M. Boella—*Proceedings IRE*, Vol. 19, No. 11, November, 1931, Page 1911.
- The Adjustment of the Multivibrator for Frequency Division—V. J. Andrew—*Proceedings IRE*, Vol. 19, No. 11, November, 1931, Page 1911.
- New Methods of Frequency Control Employing Long Lines—J. W. Conklin, J. L. Finch, and C. W. Hansell—*Proceedings IRE*, Vol. 16, No. 11, November, 1931, Page 1918.
- Some Experimental Studies of the Vibrations of Quartz Plates—R. B. Wright and D. M. Stuart—*Bureau of Standards Journal of Research*, Vol. 7, 1931, Page 519.
- Quartz Resonators and Oscillators—P. Vigoureux—His Majesty's Stationery Office, London, 1931 (A very complete review and bibliography).
- Effect of Piezo-Electric Oscillation on the Intensity of X-Ray Reflections from Quartz—G. W. Fox and P. H. Carr—*Physical Review*, Vol. 37, 1931, Page 1622.
- An Interpretation of the Effect of Piezo-Electric Oscillations on the Intensity of X-Ray Reflections from Quartz—B. E. Warren—*Physical Review*, Vol. 38, 1931, Page 572.
- X-Ray Reflection from Oscillating Crystals—R. M. Langer—*Physical Review*, Vol. 38, 1931, Page 573.
- Laue Spots from Perfect, Imperfect and Oscillating Crystals—C. S. Barrett—*Physical Review*, Vol. 38, 1931, Page 832.
- Regular Reflection of X-Rays from Quartz Crystals Oscillating Piezo-Electrically—C. S. Barrett and C. E. Howe—*Physical Review*, Vol. 38, 1931, Page 2290.
- The Effects of the Thermal Strain on the Intensity of Reflection of X-Rays by Some Crystals—Y. Sakisaka and I. Sumoto—*Proc. Phys., Math. Soc. of Japan*, Vol. 13, 1931, Page 211.
- Note on the Effect of Piezo-Electric Oscillation on the Intensity of X-Ray Reflections from Quartz—S. Nishikawa, Y. Sakisaka, and I. Sumoto—*Physical Review*, Vol. 38, Page 1078, 1931.
- X-Ray Reflections from Oscillating Crystals—F. M. Langer—*Physical Review*, Vol. 38, 1931, Page 573.
- Reflection of Monochromatic X-Rays from Some Crystals—Y. Sakisaka—*Jap. Journal Phys.*, Vol. 4, 1927, Page 171. *Proc. Phys., Math. Soc. of Japan*, Vol. 13, 1931, Page 211.
- Beugungs und Transversalschwingungen Piezo-elektrisch Angeregter Quarzplatten (Flexural and Transverse Vibrations of Piezo-Electrically Excited Quartz Plates)—H. Doerffler—*Zeitschrift fur Physik*, Vol. 63, 1930, Page 30.
- Die Schwingungen der Quarzlamelle (The Vibrations of Quartz Plates)—A. Lissutin—*Zeitschrift fur Physik*, Vol. 59, 1930, Page 265.
- Sur les Vibrations du Quartz Piezo-Electrique Auiant L'axe Optique (Vibrations of Piezo-Electric Quartz along the Optic Axis)—P. T. Kao—*Comptes Rendus*, Vol. 191, 1930, Page 768.
- Piezo-elektrische Versuche nach dem Princip der Methode von Giebe and Scheibe (Piezo-Electric Experiments on the Principle of the Method of Giebe and Scheibe)—A. Hettich—*Zeitschrift fur Physik*, Vol. 65, 1930, Page 506.
- An International Comparison of Frequency by Means of a Luminous Quartz Resonator—S. Jimbo—*Proceedings IRE*, Vol. 18, 1930, Page 1930.
- Modes of Vibration of a Round Plate cut from a Quartz Crystal—A. M. Skellet—*Journal Opt. Soc. Amer.*, Vol. 20, 1930, Page 293.
- Transversalschwingende Leuchtresonatoren als Frequenznormale in Bereich von 1000-20,000 Hertz (Luminous Resonators in Transverse Vibration as Frequency Standards in the Range of 1000 to 20,000 Cycles per Second)—E. Giebe and A. Scheibe—*Zeitschrift fur Hochfrequenztechnik*, Vol. 35, 1930, Page 165.
- New Piezo-Oscillations with Quartz Cylinders Cut Along the Optical Axis—A. Hund and R. B. Wright—*Bureau of Standards Journal of Research*, Vol. 4, 1930, Page 383. *Proceedings IRE*, Vol. 18, 1930, Page 741.
- Strukturbestimmung durch Akustische Eigenschwingungen (The Internal Structure Determined by the Natural Frequencies of Vibration)—A. Meissner—*Zeitschrift fur Physik*, Vol. 65, 1930, Page 145.
- The Excitation of Overtones of Shear Vibrations in Y-cut Quartz Plates—J. R. Harrison—*Physical Review*, Vol. 35, 1930, Page 1417.
- The Crystal Clock—W. A. Marrison—*Nat. Acad.*, July, 1930, Page 496.
- Quartz Control for Frequency Stabilization in Short-wave Receivers—P. Van Handel, K. Kruger, and H. Plendl—*Proceedings IRE*, February, 1930, Page 307.
- Some Remarks on the Multivibrator—Y. Watanabe—*Proceedings IRE*, February, 1930, Page 327.
- Method and Apparatus Used at the Bureau of Standards in Testing Piezo Oscillators for Broadcast Stations—E. L. Hall—*Proceedings IRE*, March, 1930, Page 490.
- The Piezo-Electric Resonator in High Frequency Oscillation Circuits—Y. Watanabe—*Proceedings IRE*, April, 1930, Page 695. Parts II, III and IV, May, Page 682.
- New Piezo Oscillations with Quartz Cylinders Cut Along the Optical Axis—August Hund and R. B. Wright—*Proceedings IRE*, May, 1930, Page 741.
- Design of a Portable Temperature Controlled Piezo Oscillator—V. E. Heaton and W. S. Brattain—*U. S. Bureau of Standards Journal*, March, 1930, Page 345.
- The Establishment of the Japanese Radio-Frequency Standard—Y. Namba—*Proceedings IRE*, June, 1930, Page 1017.
- Design of a Portable Temperature Controlled Piezo Oscillator—V. E. Heaton and W. H. Brattain—*Proceedings IRE*, July, 1930, Page 1447.
- Electroelastic and Pyro-Electric Phenomena—W. G. Cady—*Proceedings IRE*, July, 1930, Page 1247.
- Interpolation Methods for Use with Harmonic Frequency Standards—J. K. Clapp—*Proceedings IRE*, September, 1930, Page 1575.
- A Precise and Rapid Method of Measuring Frequencies from Five to Two Hundred Cycles per Second—N. P. Case—*Proceedings IRE*, September, 1930, Page 1586.
- An International Comparison of Frequency by Means

RADIO-ELECTRONIC BIBLIOGRAPHY

- of a Luminous Quartz Resonator—S. Jimbo—*Proceedings IRE*, November, 1930, Page 1930.
- Characteristics of Piezo-Electric Quartz Oscillators—I. Koga—*Proceedings IRE*, November, 1930, Page 1935.
- Temperature Control for Frequency Standards—J. K. Clapp—*Proceedings IRE*, December, 1930, Page 2003.
- Summary of Piezo-Electric Crystal Conference Held by U. S. Navy Department, December 3-4, 1929, *Proceedings IRE*, December, 1930, Page 2128.
- Piezo-Electric Terminology—W. G. Cady—*Proceedings IRE*, December, 1940, Page 2136.
- Push-Pull Piezo-Electric Oscillator Circuits—J. R. Harrison—*Proceedings IRE*, January, 1930, Page 95.
- Investigation of Quartz Controlled Oscillation Processes—P. von Handel—*Elektrische Nachrichten-Technik*, January, 1930, Page 34.
- Transversal Oscillating Light Resonators as a Frequency Standard in Range from 1,000 to 20,000 Hertz—E. Geibe and A. Scheibe—*Zeit fur Hochfrequenztechnik*, May, 1930, Page 166.
- Uses of Oscillating Piezo-Electric Quartz Plates—R. C. Hitchcock—*M. A. Foote Prints*, Volume 3, No. 1, 1930, Page 3.
- The Dimensions of Low Frequency Quartz Oscillators—R. C. Hitchcock—*Review of Scientific Instruments*, January, 1930, Page 13.
- Design and Manufacture of Oscillating Quartz Plates—S. Matsumura and K. Takahashi—*Electrotech. Lab. Circular*, July, 1930.
- New Piezo Oscillations with Quartz Cylinders Cut Along the Optical Axis—A. Hund and R. B. Wright—*U. S. Bureau of Standards Journal*, March, 1930, Page 384.
- Method and Apparatus Used in Testing Piezo Oscillators for Broadcasting Stations—E. L. Hall—*U. S. Bureau of Standards Journal*, January, 1930, Page 115.
- General Properties of Piezo-Electric Quartz and the Value of a Quartz Oscillator as a Frequency Standard—S. Namba and S. Matsumura—*Electrotech. L. Researches*, April, 1929.
- The Piezo-Electric Crystal Oscillator—J. Warren Wright—*Proceedings IRE*, January, 1929, Page 127.
- A Convenient Method for Referring Secondary Frequency Standards to a Standard Time Interval—L. M. Hull and J. K. Clapp—*Proceedings IRE*, February, 1929, Page 252.
- A System for Frequency Measurements Based on a Single Frequency—E. L. Hall—*Proceedings IRE*, February, 1929, Page 272.
- A High Precision Standard of Frequency—W. A. Harrison—*Proceedings IRE*, July, 1929, Page 1103.
- Observations on Modes of Vibration and Temperature Coefficients of Quartz Crystal Plates—F. R. Lack—*Proceedings IRE*, July, 1929, Page 1123.
- Some Principles of Broadcast Frequency Allocation—L. E. Whittlemore—*Proceedings IRE*, August, 1929, Page 1343.
- Measurement of Frequency—S. Jimbo—*Proceedings IRE*, November, 1929, Page 2011.
- High Frequency Quartz Crystal Oscillators—F. R. Lack—*Bell Lab. Record*, October, 1929, Page 54.
- Characteristics of Piezo-Electric Quartz Oscillations—I. Koga—*Institute Electrical Engineers Journal*, Japan, September, 1929, Page 1031.
- Observations on Modes of Vibration and Temperature Coefficients of Quartz Crystal Plates—F. R. Lack—*Bell System Technical Journal*, July, 1929, Page 515.
- Sur les Vibrations Suivant L'Axe Optique dans un Quartz Piezo-Electrique Oscillant (Vibrations along the Optic Axis in a Piezo-Electric Quartz Crystal)—E. P. Tawil—*Comptes Rendus*, Vol. 189, 1929, Page 163.
- Internationale Vergeichungen von Frequenznormalen für elektrische Schwingungen (International Comparisons of Frequency Standards for Electrical Oscillations)—E. Geibe and S. Scheibe—*Zeitschrift für Hochfrequenztechnik*, Vol. 33, 1929, Page 176.
- Untersuchung über Pyro- und Piezo-Elektrizität (Investigation on Pyro- and Piezo-Electricity)—A. Meissner—*Die Naturwissenschaften*, Vol. 17, 1929, Page 25.
- An Interferometer Method of Observing the Vibrations of an Oscillating Quartz Plate—H. Osterberg—*Proc. Nat. Acad. Sciences*, Vol. 15, 1929, Page 892.
- On the Modes of Vibration of a Quartz Crystal—J. W. Harding and F. W. G. White—*Phil. Mag.*, Vol. 8, 1929, Page 169.
- Mosaic Crystals—F. Zwicky—*Proc. Nat. Acad.*, Vol. 15, 1929, Page 816.
- Atomic Arrangements in Silicate—W. L. Bragg—*Trans. Faraday Society*, Vol. 25, 1929, Page 291.
- The Physics of Crystals*—A. F. Joffe—McGraw-Hill Book Co., Inc., New York City, 1928.
- Introduction to Crystal Analysis*—W. H. Bragg—G. Bell and Sons, London, 1928.
- A Visual Method for Studying Modes of Vibration of Quartz Plates—A. M. Skellet—*Journal Optical Soc. Amer.*, Vol. 17, 1928, Page 308.
- Etude Experimentale des Deformations et des Changements de Proprietes Optiques due Quartz sous L'Influence du Champ Electrique (Experimental Investigation of the Deformations and of the Alterations of the Optical Properties of Quartz Subjected to an Electric Field)—Ny Tsi Ze—*Journal de Phys.*, Vol. 9, 1928, Page 13.
- Mechanische Schwinungen Piezo-Elektrisch Angeregter Quarze (Mechanical Vibrations of Piezo-Electrically Excited Quartz Plates)—R. Wachsmuth and H. Auer—*Zeitschrift für Physik*, Vol. 47, 1928, Page 323.
- Der Piezo-Elektrische in Hochfrequenzschwingungskreisen (The Piezo-Electric Resonator in High Frequency Oscillatory Circuits)—Y. Watanabe—*Elektrische Nachrichtentechnik*, No. 5, 1928, Page 45.
- Piezo-Elektrische Erregung von Dehnungs, Biegungs und Drillungsschwingungen bei Quartzstäben (Piezo-Electric Excitation of Longitudinal, Transverse and Torsional Vibrations in Quartz Rods)—E. Geibe and A. Scheibe—*Zeitschrift für Physik*, Vol. 46, 1928, Page 607.
- Piezo-Elektrische Kristalle als Frequenznormale (Piezo-Electric Crystals as Frequency Standards)—A. Scheibe and E. Geibe—*Elektrische Nachrichtentechnik*, Vol. 5, 1928, Page 65.
- Nouveau Model de Developpement D'Electricite par Torsion dans les Cristaux de Quartz (New Method of Liberating Electrical Charges by Torsion in Quartz Crystals)—E. P. Tawil—*Comptes Rendus*, Vol. 187, 1928, Page 1042.
- Bibliography on Piezo-Electricity—W. G. Cady—*Proceedings IRE*, Vol. 16, 1928, Page 521.
- Frequency Control for Broadcasting—J. C. Barber—*Bell Lab. Record*, Vol. VII, No. 1, September, 1928, Page 24.
- Notes on Quartz Plates, and Gap Effect, and Audio-Frequency Generation—A. Hund—*Proceedings IRE*, August, 1928, Page 1072.

RADIO-ELECTRONIC BIBLIOGRAPHY

- Piezo-Electric Oscillator Circuits with Four-Electrode Tubes—J. R. Harrison—*Proceedings IRE*, November, 1928, Page 1455.
- The Dependence of the Frequency of Quartz Piezo-Electric Oscillation Upon Circuit Constants—E. H. Terry—*Proceedings IRE*, November, 1928, Page 1486.
- Bibliography on Piezo-Electricity—J. H. Dellinger—*Proceedings IRE*, April, 1928, Page 521.
- The Status of Frequency Standardization—H. J. Dellinger—*Proceedings IRE*, May, 1928, Page 579.
- The Piezo-Electric Resonator and Its Equivalent Network—K. S. Van Dyke—*Proceedings IRE*, June, 1928, Page 742.
- The Navy's Primary Frequency Standards—R. H. Worall & R. B. Owens—*Proceedings IRE*, June, 1928, Page 778.
- Thermostat Design for Frequency Standards—W. A. Marrison—*Proceedings IRE*, July, 1928, Page 976.
- A New Type of Standard Frequency Piezo-Electric Oscillator—L. P. Wheeler and W. E. Bower—*Proceedings IRE*, August, 1928, Page 1035.
- Quartz Crystals; How to Cut Them—H. C. Hitchcock—*Radio Broadcast*, December, 1928, Page 85.
- International Measurements of Frequency Standards for Electric Oscillations—E. Giebe and A. Scheibe—*Zeit fur Hochfrequenztechnik*, May, 1938, Page 176.
- A Crystal Grinder—H. F. Mason—*QST*, May, 1928, Page 37.
- Grinding of Quartz Plates—E. G. Watts—*QST*, January, 1928, Page 27.
- A Precision Method for the Measurement of High Frequencies—C. B. Aiken—*Proceedings IRE*, February, 1928, Page 125.
- Precision Determination of Frequency—J. W. Horton and W. A. Marrison—*Proceedings IRE*, February, 1928, Page 137.
- Modes of Vibration in Piezo-Electric Crystals—A. Crossley—*Proceedings IRE*, April, 1928, Page 416.
- Piezo-Electric Crystals at Radio Frequencies—A. Meissner—*Proceedings IRE*, April, 1927, Page 281.
- Piezo-Electric Crystal-Controlled Transmitters—A. Crossley—*Proceedings IRE*, January, 1927, Page 9.
- Note on Piezo-Electric Generators with Small Back Action—A. Hund—*Proceedings IRE*, August, 1927, Page 725.
- Mounting Quartz Oscillator Crystals—R. C. Hitchcock—*Proceeding IRE*, November, 1927, Page 902.
- Piezo-Electric Resonance and Oscillatory Phenomena with Flexural Vibrations in Quartz Plates—J. R. Harrison—*Proceedings IRE*, December, 1927, Page 1040.
- A Shear Mode of Crystal Vibration—W. G. Cady—*Physical Review*, Vol. 29, 1927, Page 617.
- Quelques Observations Faites sur Le Quartz Piezo-Electrique on Resonance (Observations on Piezo-Electric Quartz in Resonant Vibration)—E. P. Tawil—*Comptes Rendus*, Vol. 185, 1927, Page 114.
- Quartz Oscillators (Quartz)—A. Hinderlich—London, 1927.
- The Piezo-Electric Resonator—Y. Watanabe—*Journal Inst. Elec. Engrs.*, Japan, No. 466, 1927, Page 506.
- Characteristics of the Piezo-Electric Coupler—Y. Watanabe—*Journal Inst. Elec. Engrs.*, Japan, No. 466, 1927, Page 529.
- Piezo-Electric Oscillators and Piezo-Electric Frequency Stabilizers—Y. Watanabe—*Journal Inst. Elec. Engrs.*, Japan, No. 469, 1927, Page 835.
- Sub-Fundamental Piezo-Electric Vibrations in Quartz Plates—J. R. Harrison—*Physical Review*, Vol. 29, 1927, Page 366.
- Normalfrequenzen und Absolute Frequenzmessung (Frequency Standards and Absolute Measurements of Frequency)—A. Scheibe—*Zeitschrift fur Hochfrequenztechnik*, Vol. 29, 1927, Page 120.
- Untersuchungen am Quarz (Investigations on Quartz)—A. Meissner—*Physikalische Zeitschrift*, Vol. 28, 1927, Page 621.
- Circuit Electrique Equivalent a un Quartz Piezo-Electrique (The Equivalent Electrical Circuit of a Piezo-Electric Quartz Resonator)—F. Bedeau—*QST Francais et Radio Electricite Reunis*, Vol. 8, 1927, No. 37.
- The Properties of Silica—R. Sesman—Chemical Catalog Co., New York, 1927.
- Piezo-Electric Quartz Oscillators with Metallic Films—E. O. Hulbert—*Physical Review*, Abstract, Vol. 27, 1926, Page 814.
- Structure of Quartz—R. E. Gibbs—*Proc. Royal Soc.*, A-110, 1926, Page 443.
- Intensity of Reflection of X-Rays by Crystals—C. G. Darwin, W. L. Bragg and R. W. James—*Phil. Mag.*, Vol. 1, 1926, Page 897.
- The Dependence of the Frequency of Quartz Piezo-Electric Oscillators upon Circuit Constants—E. M. Terry—*Proceedings IRE*, Vol. 16, 1926, Page 1486.
- Piezo-Elektrische Resonanzerscheinungen (Piezo-Electric Resonance Phenomena)—A. Scheibe—*Zeitschrift fur Hochfrequenztechnik*, Vol. 28, 1926, Page 15.
- Uses and Possibilities of Piezo-Electric Oscillators—A. Hund—*Proceedings IRE*, Vol. 14, 1926, Page 447.
- Le Quartz Oscillant et ses Applications a la T.S.F. (Oscillating Quartz and its Application to Wireless)—J. Quinet—*Radio Revue*, Vol. 5, 1926, Page 114.
- Uber Piezo-Elektrische Kristalle bei Hochfrequenz (On the Piezo-Electric Crystals at High Frequency)—A. Meissner—*Elektrische Nachrichtentechnik*, Vol. 3, 1926, Page 401.
- The Piezo-Electric Quartz Resonator and its Equivalent Electrical Circuit—D. W. Dye—*Proceedings Phys. Soc. London*, Vol. 38, 1926, Page 399.
- Het Gebruik van Piezo-Elektrische Kwarts-Kristallen in de Draadloze Telegrafie en Telefonie (The Use of Piezo-Electric Quartz Crystals in Wireless Telegraphy and Telephony)—B. Van der Pol—*Godenboek Ned. Vereen. voor Radiotel*, 1926, Page 293.
- Leuchtende Piezo-Elektrische Resonatoren als Hochfrequenznormale (Luminous Piezo-Electric Resonators as High Frequency Standards)—E. Giebe and A. Scheibe—*Elektrotechnische Zeitschrift*, Vol. 47, 1926, Page 380.
- Sur Les Variations des Proprietes Optiques du Quartz Piezo-Electrique Soumis a des Courants de Haute Frequence (On the Variations of the Optical Properties of Piezo-Electric Quartz Subjected to High Frequency Currents)—E. P. Tawil—*Comptes Rendus*, Vol. 183, 1926, Page 1099.
- A New Method of Obtaining Frequency Stabilization of a Transmitter by means of an Oscillating Quartz Crystal—C. W. Goyder—*Experimental Wireless*, Vol. 3, 1926, Page 717.
- Piezo-Electric Standards of High Frequency—W. G. Cady—*Journal Optical Society of America*, Vol. 10, 1925, Page 475.
- The Quartz Oscillator—E. Mallet and V. J. Terry—*Wireless World*, Vol. 16, 1925, Page 630.
- Sichtbarmachung von Hochfrequenten Longitudinal-

RADIO-ELECTRONIC BIBLIOGRAPHY

schwingungen Piezo-Elektrischer Kristallstäbe (Visible Phenomena in Piezo-Electric Rods Vibrating Longitudinally at High Frequencies)—E. Giebe and A. Scheibe—*Elektrotechnische Zeitschrift* (Probably 1926). Piezo-Elektrisch Erzeugene Schwingungen von Quarzstäben (Piezo-Electrically Induced Vibrations in Quartz Rods)—V. M. Laue—*Zeitschrift für Physik*, Vol. 34, 1925, Page 347.

Crystals and the Fine Structure of Matter—F. Rinne—Translation by W. S. Stiles, Methuen, London, 1924. A Self-Contained Standard Harmonic Wavemeter—D. W. Dye—*Phil. Trans. Roy. Soc.*, Vol. A224, 1924, Page 259.

An International Comparison of Radio Wave Length Standards by Means of Piezo-Electric Resonators—W. G. Cady—*Proceedings IRE*, December, 1924, Page 805.

Piezo-Electrically Driven Tuning Forks and Rods—W. G. Cady—*Physical Review*, Abstract No. 13, Vol. 21, 1923, Page 371.

Piezo-Electric Crystal Resonators and Crystal Oscillators Applied to the Precision Calibration of Wave-meters—G. W. Pierce—*Proc. Amer. Acad. Arts & Science*, Vol. 59, 1923, Page 81.

Dictionary of Applied Physics—Sir R. Glazebrook—Macmillan and Co., London, Vol. 2, 1922, Page 598.

Theory of Longitudinal Vibrations of Viscous Rods—W. G. Cady—*Physical Review*, Vol. 19, 1922, Page 1.

The Piezo-Electric Resonator—W. G. Cady—*Proceedings IRE*, April, 1922, Page 83.

Intensity of Reflection of X-Rays by Rock-Salt—W. L. Bragg, R. W. James, and C. H. Bosanquet—*Phil. Mag.*, Vol. 41, 1921, Page 309.

Crystal Structures of Sodium Chlorate and Sodium Bromate—R. G. Dickenson and E. A. Goodhue—*Journal of American Chemical Society*, Vol. 43, 1921, Page 2045.

Studies of the Etched Figures of Japanese Quartz—S. Ichikawa—*Am. Journal Sci.*, Fourth Series, Vol. XXXIX, No. 232, April, 1915, Page 455.

The Influence of Alternating Currents on Certain Melted Metallic Salts—C. Tissot—*Proceedings IRE*, January, 1914, Page 59.

Electrically Maintained Vibrations—S. Butterworth—*Proc. Phys. Soc.*, Vol. 27, 1915, Page 410.

Oeuvres (Complete Works)—P. Curie—Gauthier-Villars, Paris, 1908.

Mineralogy—H. A. Miers—Macmillan, London, 1902.

Hypothese de Polarisation Dielectriques Spontanees et Quelques-unes de ses Consequences Experimentales (Hypotheses of Spontaneous Dielectric Polarization and some of its Experimental Consequences)—*Archives des Sciences Physiques et Naturelles*, Vol. 41, 1916, Page 493.

The Piezo-Electric Effect in the Composite Rochelle Salt Crystal—A. M. Nicolson—*Proceedings IRE*, Vol. 38, 1919, Page 1315.

Analysis of Crystals by the X-Ray Spectrometer—W. L. Bragg—*Proc. Roy. Soc.*, A-89, 1913, Page 468.

X-Rays and Crystal Structure—W. H. Bragg and W. L. Bragg—Bell and Sons, London, 1915.

La Silice et les Silicates (Silica and Silicates)—H. L. LeChatelier—Hermann et Fils, Paris, 1914.

On the Piezo-Electric Property of Quartz—Lord Kelvin—*Philosophical Magazine*, No. 36, 1893, Page 331.

Allgemeine Theorie der Piezo- und Pyro-Elektrischen Erscheinungen an Kristallen (General Theory of Piezo-

and Pyro-Electric Phenomena in Crystals)—W. Voigt—Dieterich, Göttingen, 1890.

Bestimmung der Elasticitätsconstanten von Beryll und Bergkristall—V. Voigt—*Annalen der Physik*, Vol. 31, No. 474, and 701, 1899.

Developpement par Pression de L'Electricite Polaire dans les Cristaux Hemiedres a Faces Inclinees (Liberation of Electrical Charges by Pressure in Hemihedral Crystals with Inclined Faces)—P. and J. Curie—*Comptes Rendus*, Vol. 91, 1880, Page 294.

Sur L'Electricite Polaire dans les Cristaux Hemiedres a Faces Inclinees (On Polar Electricity in Hemihedral Crystals with Inclined Faces)—P. and J. Curie—*Comptes Rendus*, Vol. 91, 1880, Page 383.

Sur les Phenomenes Electriques de la Tourmaline et des Cristaux Hemiedres a Faces Inclinees (On Electrical Phenomena in Tourmaline and in Hemihedral Crystals with Inclined Faces)—P. and J. Curie.

Contractions et Dilatations Produites par des Tensions Electriques dans les Cristaux Hemiedres a Faces Inclinees (Contractions and Dilatations Produced by Differences of Electric Potential in Hemihedral Crystals with Inclined Faces)—P. and J. Curie—*Comptes Rendus*, Vol. 93, 1881, Page 1137.

Dilatation Electrique du Quartz (Electric Dilatation on Quartz)—P. and J. Curie—*Journal de Physique*, Vol. 8, 2nd series, 1889, Page 149.

Principe de la Conservation de L'Electricite (The Principle of Conservation of Electricity)—G. Lippman—*Annales de Physique et de Chimie*, Vol. 24, 5th Series, 1811, Page 145.

Addenda

A grouping of principally foreign references on Crystallography from the German book *Piezoelektrizität des Quarzes*, by Adolf Scheibe, is published as a supplement to the foregoing Bibliography, and will be found on page 61.

PORTABLE BOMB DETECTOR

[Continued from Page 18]

This amplifier obviously has other uses. The one that is most obvious is eavesdropping on suspects with a hidden microphone. For this purpose a standard lapel microphone is good and the cartridge only out of a regular crystal microphone may also be used. The Stethophone mike is not satisfactory for picking up voices since it was not designed for such a purpose. If the amplifier is connected to a vibration pick-up type of mike, it may be used to listen to heartbeats, but if used for this purpose, it would be better to increase the size of the coupling condensers in the amplifier to increase the low-frequency response, because heartbeat sounds are mainly in the low-frequency region.

A 15-foot extension cord for the microphone may also be found convenient. The jack for the earphones should be wired to the proper tap for the type of earphones it is expected will be used.

The case in which the equipment is installed may be purchased at any department or luggage store which carries low priced luggage. Mirrors and pockets not desired are easily torn out.

Q. & A. STUDY GUIDE

[Continued from Page 36]

195. How may a dry cell be tested to determine its condition?

By placing an ammeter across the terminals of the cell to determine the current.

196. What will be the result of discharging a lead-acid storage cell at an excessively high current rate?

The battery may be damaged physically as well as greatly reducing its ampere-hour capacity.

(To Be Continued)

CATHODE-RAY OSCILLOSCOPE

[Continued from Page 29]

the r.f. voltage rises in greater proportion than the audio, causing the outward curvature of the triangle's sides. This comes from regeneration when the final amplifier is not properly neutralized.

Checking Other Modulation Methods

Grid, screen, suppressor or cathode-modulated rigs are checked by the same apparatus set-up, the only difference being the requirement of less resistance in *R1* (Fig. 16). Adjustment of all these methods of modulation are less tolerant than plate modulation and their frequent checking is especially recommended.

Space does not permit a detailed description of all patterns, so a number of sketches are grouped together and briefly explained in Fig. 28, most of these being shown in the new *Radio Handbook*. Other patterns may be found in various articles. A very unusual case was described in the June, 1939, issue of *RADIO*² but is too long to repeat here.

Bear in mind that the oscilloscope may be connected to any stage suspected of faulty operation, so don't be afraid to experiment. And when new patterns are found think out the cause before trying haphazard cures. The results will be very much worth while.

Visual alignment of receivers, frequency comparisons by Lissajous figures, and numerous other oscilloscope applications will be discussed in the next installment.—Editor.

²The Pursuit and Capture of Parasitic "X."

SPEECH CONSOLE

[Continued from Page 23]

One very important part of every satisfactory recording amplifier is a volume indicator. On the console face is a 0 to 1 millimeter of the quick acting type, in a three-inch square case. The circuit, as

shown in the master diagram, consists of a single 6F8G, the first section of which acts as a diode rectifier, while the second section serves as a current-varying tube for the meter. Since this circuit is resistance coupled, the meter has very good frequency characteristics. The input potentiometer makes possible the setting of the standard volume at any desired level. This potentiometer is mounted on the chassis of the amplifier and is adjusted with a screw-driver. It is suggested that a standardized volume-indicator meter be connected in parallel with this one to determine its range. Then a constant-amplitude signal can be run through the amplifier, and reference points of standard volume can be noted for positions of the potentiometer.

The two 78 r.p.m. turntables are General Industries models. The 33-1/3 r.p.m. unit is a General Electric dual-speed model with a twelve inch table. The recorder was built by Universal. The power supply, which is placed inside the speaker cabinet in the desk, is a standard swinging choke-input type employing an 83 rectifier. It supplies 360 volts at 200 milliamperes.

LOW FREQUENCY R-F. OSCILLATORS

[Continued from Page 16]

frequency l.f. oscillator circuit strongly recommended for the generation of frequencies between 10 and 300 kc.

In this arrangement, the low-frequency beat note between two higher-frequency oscillators, one fixed and the other variable, is utilized. The two oscillators are coupled into a suitable mixer (demodulator) stage, the difference frequency being fed from this stage into an amplifier whose output tank is resonated at the beat frequency. In some instances (notably when frequencies between 10 and 50 kc. are amplified) the output amplifier may have resistance coupling in its plate circuit in lieu of a coil and condenser.

Any two convenient oscillators may be employed in this arrangement as long as it is possible to separate their frequencies of operation by the amount of the desired low frequency. For example: A fixed-frequency 6SK7 oscillator might be operated at 1000 kc. and a variable 6SK7 oscillator of the same electrical and mechanical construction operated between 1010 and 1050 kc. The beat note between the two might thus be adjusted to any value between 10 and 50 kc. This difference frequency would then be delivered by the mixer (which might be built around a 6L7 tube) to the 10-50-kc. output amplifier.

Another possibility often overlooked in the search for a low-frequency r-f. source is the 100-kc. crystal frequency standard in many station inventories. These instruments deliver an unusually stable signal at 100 kc. which may be amplified with a simple low-powered, capacity-coupled amplifier stage. Modulation may be applied to the amplifier.

CATHODE-RAY OSCILLOSCOPE

JAY BOYD

At the request of many radio instructors, and for the benefit of students and technicians now or soon to be allied with the war effort, we are reprinting the first part of Mr. Boyd's excellent series of articles on the Cathode-Ray Oscilloscope.

Of all the apparatus at our disposal there is none so versatile as the cathode-ray oscilloscope. By its use we may observe, compare or record any instantaneous changes or conditions taking place in any of our radio, sound or other electrical circuits.

The oscilloscope is to the radio engineer what the X-ray or fluoroscope is to the medical profession. By its use we can look at its fluorescent screen and see just what electrical effects are occurring in any part of the circuit to which it is connected. (Figs. 1 & 2)



FIGURE 1
THE X-RAY SHOWS
PICTURE LIKE THIS



FIGURE 2
THE CATHODE-RAY OSCILLOSCOPE PRODUCES
GRAPHS OF ELECTRICAL PHENOMENA

What Is the Oscilloscope?

The heart of the instrument is the cathode-ray tube. This is a special type of high-vacuum tube, shaped like a funnel, containing an electron gun, usually two pairs of deflecting plates, and a coated screen at the front of the tube where the image or pattern is viewed.

In operation, the heated cathode releases a cloud of free electrons. These are drawn through the electron gun which accelerates their velocity and focuses them into a tiny stream. As these electrons strike the coated surface of the viewing screen, a fluorescent glow is produced, lasting for a fraction of a second.

It is a property of emitted electrons that they will be attracted or repelled by any positively or negatively charged bodies in their proximity. Located between the electron gun and viewing screen will be found two sets of flat deflecting plates, arranged so the electron stream must pass between them.

Placing an electrical charge on these plates will cause the beam to move up or down, or to either side, making visible a graph of whatever action is taking place within the circuit under inspection.

In addition to the cathode-ray tube there is a special type of "saw-tooth" timing oscillator for providing the horizontal deflection, as required by

the majority of applications. But this is quite simple! In most commercial oscilloscopes we will find two amplifiers, labeled "vertical" and "horizontal," along with their respective gain controls, and switches for cutting them in or out of the circuit as desired. And then there is a power supply—usually a dual sort of affair. And that's about all there is to the instrument.

Put these five units—cathode-ray tube, saw-tooth oscillator, horizontal and vertical amplifiers and power supply into a suitable cabinet and there you have a complete, self-contained cathode-ray oscilloscope. A block diagram of this assembly will be found in Fig. 3.

Applications Are Many

It would be impossible to list all the applications for which the cathode-ray oscilloscope may be used to advantage. Its users are always finding new roles for it to play.

But before telling some of its more popular uses, let's consider its workings in a little more detail. We mentioned that the "movable element" is the electron stream. The mass of these electrons is so infinitesimally small that, for all our practical purposes, their weight and mass may be entirely ignored. The diversion of this stream, or beam, from its normal course may be effected at the highest radio frequencies without the sluggishness which would be the case if a mechanical vibrating element were used, however small it might be. Therefore, the beam will faithfully follow excitation of any frequency and pro-

duce a true graph upon the viewing screen.

Now let's consider some of the cathode-ray oscilloscope's more popular uses.

Audio amplifier checking—We may observe and correct waveforms, tube overloads and consequent distortion, feedback, unwanted oscillations of audio or radio frequencies, power supply hum, inductive pickup, check and measure gain per stage, frequency response, match phase-inversion circuits or load impedances.

The effect of any changes may be observed when "cleaning up" or "flattening out" a newly-built amplifier which, to the critical ear, will sound only as good as it looks on the oscilloscope.

Transmitter checking—The oscilloscope is the most satisfactory instrument known for checking the performance of radiophone transmitters. Besides checking the entire audio system from microphone to modulation transformer, we can also adjust the transmitter for the much desired hundred per cent modulation, check neutralization, lack or excess of grid drive, over- or under-biasing of amplifier, linearity of modulation, overloaded speech or modulator tubes. Modulation transformers may be properly matched to the r.f. load. The source of hum modulation or r.f. feedback may be more easily found and corrected.

Or, in short, if the phone transmitter is "ailing," the 'scope will certainly show up its faults. These checks are made by observing either the modulation envelope, audio waveform, or trapezoidal patterns, and sometimes by the elliptic or cat's eye pattern.

Receiver checking and alignment—Besides being useful for stage by stage checking of receiver circuits, the cathode-ray oscilloscope offers the most accurate means known for correctly aligning tuned circuits, and particularly the intermediate frequency channels of superheterodynes. Performance of demodulator and audio systems of the receiver may also be easily checked.

Study of power circuits—Alternating current waveforms are shown as a "graph" upon the screen and their various relations may be studied, measured and analyzed. Transients and surges

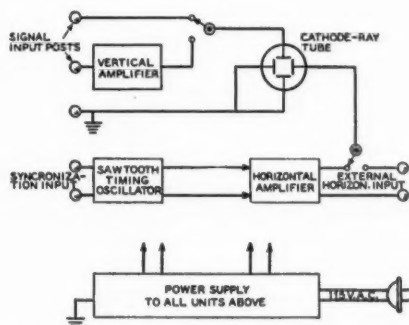


Fig. 3. Block diagram of a typical cathode-ray oscilloscope.

may be inspected, as well as operation of relays, circuit breakers, fuses, etc.

Large-screen oscilloscopes are ideal for class-room demonstrations of all sorts of electrical and radio phenomena.

The automotive and aviation industries have made frequent use of oscilloscopes in their studies of vibration, noise, combustion pressures, ignition systems, etc.

One special type of cathode-ray oscilloscope, the cardiograph (or 'scope) is used by doctors and hospitals for the study of heart conditions.

Another special type of instrument is used by orchestra directors for the exact tuning of musical instruments.

The Story of Cathode Rays

Now that we have covered a rough outline of the instrument and its many uses, let's turn back the pages of history for a brief look at its forbears. Not that it is necessary in order to understand the 'scope. But because its history is so interesting, and because we will more greatly appreciate the instrument when we remember the earlier apparatus.

The production of electron streams, which he named "cathode rays," was first discovered by Sir William Crookes about 1874, while experimenting with Geissler tubes (Fig. 4). These are simply vacuum tubes having electrodes in either end and containing small amounts of rarefied gases, which glow, something like our present-day neon tubes, when high voltages are applied to the electrodes.

He noticed that if these were pumped to a very high vacuum, the gaseous glow would disappear and then the inside walls of the glass tube would show brilliant fluorescent effects.

It was also found that these free electrons always left the cathode at right angles to its flat surface, and that if this cathode were made concave they could be focused into a highly concentrated beam, having enough energy to fuse platinum foil inserted at this focal point within the tube. There was much controversy over the question of whether the cathode ray was an ether wave, an invisible light, or a stream of material particles flowing between the cathode and anode.

Sir J. J. Thomson, about 1892, determined that these cathode rays were, in reality, a stream of free electrons and proved that they might be deflected by a magnetic or electrostatic field (Fig. 5). In his experiment he placed a strip of mica, coated with zinc sulphide, within the tube, parallel to the electron stream. Placing a magnet near the tube deflected the beam. As the electrons ricocheted along the screen, their path was made visible by the fluorescent glow thus produced. This experiment laid the foundation for our modern cathode-ray tubes.

Here we may diverge a moment to be reminded of another important discovery, for which the cathode ray was directly responsible. A German physicist,

Wilhelm Konrad Röntgen, in 1895, made the discovery that whenever cathode rays fell upon the walls of the tube or any obstacle within, and especially the platinum anode, a form of invisible radiation, capable of passing through many opaque objects, was produced. He had discovered the X-ray!

It should be noted here that the cathode ray differs from the X-ray in that the former is simply a stream of free electrons, while the latter is similar to our radio and light waves, only much, much shorter.

And now back to our story. About 1894 a Frenchman, Hess, suggested using the cathode ray as the writing stylus for tracing curves of electrical phenomena. Then K. F. Braun of Germany designed and applied a cathode-ray oscillograph for this purpose as early as 1897 (Fig. 6).

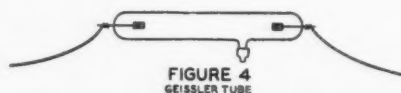


FIGURE 4
GEISSLER TUBE

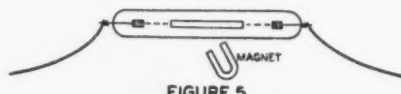


FIGURE 5
CROOKES' EXPERIMENT, PROVING
DEFLECTION OF CATHODE-RAYS



FIGURE 6
A SIMPLE BRAUN TUBE

This and all former tubes used a cold cathode, electron emission being effected by means of high vacuum and potentials of anywhere up to 100,000 volts. With such high potentials, the electrons attained velocities of about one-half the speed of light.

A few years later, Dufour in France and Sir J. J. Thomson and A. B. Wood in England built oscillographs of this pattern. They stood several feet in height, being made of iron and shaped like an upturned funnel, with the cathode at the top. They were equipped with a door for insertion of the six photographic plates and two fluorescent screens which were carried on a revolving drum. A glass window permitted viewing as well as photographing the phenomena under study.

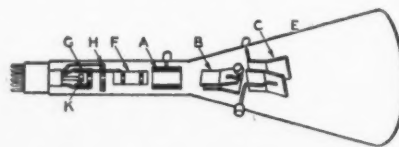


Fig. 7. A typical cathode-ray tube.

After loading the plate-holders and pumping the vacuum for awhile, these pioneer physicists were ready to photograph a few patterns, which usually consisted of a single trace across the screen. But in spite of this laborious method,

some very fine oscillograms were produced, particularly of radio wave trains.

So just remember that, the next time you think it is a little trouble to hook up your modern and highly developed oscilloscope!

Modern Cathode-Ray Tubes

In 1905 Wehnelt found that by using a hot cathode operation at very low voltages was practical but the filament life of the tube was a short one. Western Electric brought out their type 224, hot-cathode tube about 1921. This tube contained a small amount of argon gas, which, along with a critical adjustment of filament temperature, caused the electrons to gather into a concentrated stream. An improved cathode structure increased the filament life to several hundred hours.

In the earlier 1930's, Manfred von Ardenne in Europe and R.C.A., Dumont, Farnsworth and others in America began experimenting with cathode-ray tubes for television. This resulted in development of the excellent series of hot-cathode, high-vacuum tubes now available for either oscilloscopic or television use.

These tubes all focus by adjustment of voltages on certain elements of the electron gun, and, containing no gas, have a very long life.

Theory of the Tube

Having covered a rough outline of cathode-ray tubes and oscilloscopes, let us now examine the individual components in greater detail.

The "innards" of a typical cathode-ray tube are shown in Fig. 7. These comprise the cathode K which releases free electrons when heated by the filament within the cathode sleeve. This cathode is surrounded by a cylinder G, which has a small hole in its front for the passage of the electron stream. Although this element is not a wire screen as our usual grid, it is known by that name because its action is similar; that is, the purpose of controlling the cathode stream by a variation of its negative potential.

Next in line is found the first accelerating anode, H, being simply a disk having another small hole in its center. In some tubes this element is connected within the tube to a second cylindrical accelerating anode, A, both these elements operating at the full potential of the tube. In the tube sketched the first accelerating electrode connects to a base pin and operates at reduced voltage.

Between these elements is found a sleeve, F, containing two more small disks, these also having small holes in their centers. This is known as the focusing electrode.

The electrodes just described comprise the electron gun, which produces free electrons and focuses them into a slender, concentrated stream, for projection onto the viewing screen.

A comprehensive explanation of the electron action in this process of focusing involves a study of what is known

[Continued on page 48]



FOR QUICKER
Radio Defense Training
 USE **MEISSNER KITS**

One, two and three tube Student "Midget" kits will solve the problem of quicker radio training. They are especially designed for classroom use. The "add-on" feature permits the conversion of the one tube to a two tube and the two tube to a three tube receiver. Meissner Student "Midget" Kits are being widely used in schools for defense radio training.

EASY TO BUILD! . . . with the Meissner Pictorial Wiring Diagram furnished with each kit, construction is simplified so that even a beginner can quickly and easily assemble the kits.

The one, two and three tube kits are available for battery operation. The two and three tube can be obtained for AC-DC operation.

Write for complete catalog. Address Dept. RA8.

Meissner

MT. CARMEL, ILLINOIS

"PRECISION BUILT PRODUCTS"

as "electron optics," so called because the electron stream obeys many common optical laws.¹

We will simply state here that when the focusing electrode voltage is adjusted to approximately one-fifth that of the accelerating electrodes, a very fine beam of electrons will find a focal point on the viewing screen.

Since the tube manufacturers have designed their tubes so as to focus properly, all we have to worry about is the inclusion of a potentiometer in our circuit for making this adjustment, and another potentiometer for adjusting the grid voltage to the value necessary for producing the desired brilliance of pattern.

Deflecting the Beam

Up to this point we have covered only the production and focusing of the beam. This, of course, must be deflected from its normal course so as to strike any part of the viewing screen if a pattern is to be produced. As previously stated, either a magnetic or electrostatic field will attract or repel the beam from its normal course.

Some tubes, particularly a few of the larger ones meant for television use, are designed for magnetic deflection and do not contain the electrostatic deflection plates found in all the smaller tubes used in cathode-ray oscilloscopes. Beam deflection in tubes of the former type is accomplished by means of electromagnets, usually made in the form of a yoke, which slip over the neck of the tube.

The only point in mentioning electro-magnetic deflection here is to impress upon the reader that the beam is easily deflected by magnetic fields, since this may be the source of much annoyance if the tube is not kept clear of all power transformer and filter choke fields.

Electrostatic Deflection

Referring back to Fig. 7, we will find, between the electron gun and viewing screen, two pairs of flat electrodes which we know as deflector plates. An outside connection, similar to a grid cap on receiving tubes, is brought out from each plate in the tube sketched. However, in the case of smaller tubes for oscilloscopic use, these terminals are connected to pins in the tube's base. Also, it should be mentioned, one plate of each pair is tied together inside the tubes and then connected to the accelerating electrodes, A and H, making actually four electrodes tied to this common pin. These electrodes are operated at ground potential, which is the *positive* terminal of the high-voltage power supply in oscilloscope practice. The two remaining free plates, then, are used for application of the voltages under test.

It will be noted that each pair of plates is mounted at right angles to the other set. Placing a positive voltage on either free plate will divert the beam toward that plate and a negative charge will like-

wise repel the beam, as shown in Fig. 8.

If the top plate of the set nearest the electron gun is made alternately positive and negative, as by connection to an alternating current potential, the beam will move up and down. As the electrons strike the screen a momentary fluorescent glow is produced.

Cathode-Ray Tube Characteristics

As with other types of vacuum tubes, cathode-ray tubes are designed to operate with certain specified voltages, although they are quite tolerant in this respect. The 902, for instance, is rated for 400- to 600-volt anode potential, but will focus with good brilliance at considerably less voltage.

In changing the anode voltage, however, the deflection sensitivity, spot diameter or line width, and maximum brilliance will be affected.

The higher the anode voltage, the smaller is the spot diameter or line width, the greater is the brilliance of trace, and the *lower* is the tube sensitivity.

Deflection Sensitivity

The user of an oscilloscope should know the deflection sensitivity of his instrument, whether with or without use of any amplifiers. The potential required to move the beam from its center position to outer edge of the screen varies from about 100 to 150 volts, depending on the particular tube used and its anode potential.

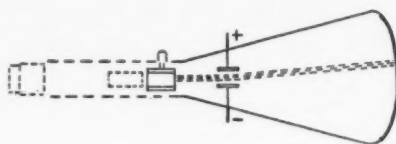


Fig. 8. A positive charge attracts the electron beam, deflecting it toward the charge.

In order to make the oscilloscope useful for testing voltages of such magnitude as encountered in receivers and amplifiers, a vertical amplifier is provided to boost the voltage under test to the value needed for beam deflection.

Changing the anode potential affects the sensitivity, this change being inversely proportional to the change in anode voltage. Or in other words, reduce the anode voltage to one-half and the tube is *twice* as sensitive. This is due to the simple fact that the velocity of electrons in their journey from the gun to the screen is in proportion to the anode voltage, and, therefore, a greater voltage charge is required on the deflector plates to divert a faster-moving stream.

The Fluorescent Screen

Cathode-ray tubes are made with several types of screen material, depending upon the purpose for which the particular type of tube is intended.

Their chief characteristic is known as "persistence," which refers to the period

of time the screen will glow after being bombarded by an electron shower.

Tubes intended for visual observation use screens of medium or long persistence; that is, the pattern remains on the screen for a fraction of a second, which eliminates any flickering at all but the very lowest frequencies. Screens of this type are well suited for "still" photography, whenever the pattern is of such character that it will remain stationary upon the screen.

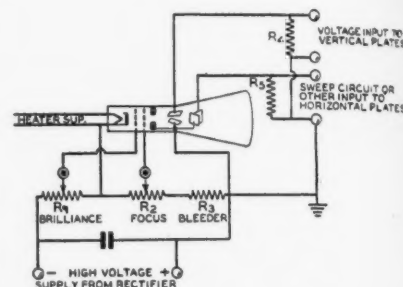


Fig. 9. Typical cathode-ray tube circuit.

There is also a short-persistence type of screen, which retains its glow for less than thirty microseconds, making it useful for oscillographic recording by means of moving-film photography. In this type of work the signal being recorded is connected to only one set of deflecting plates, the movement of the film furnishing the element of "time."

Medium or long-persistence screens glow with a greenish hue which is quite pleasant to the eye, especially when watching the screen for long periods of time. Short-persistence screens produce a blue line which is highly actinic, photographically.

In answer to the demands of television a screen giving a white line can be had in certain tube types. These make possible black-and-white pictures for the television audience.

Cathode-Ray Tube Circuits

Having covered the various elements inside the tube, as well as their functions, let us now consider a typical circuit in which they are used, as shown in Fig. 9.

The tube is shown schematically, with both the control grid and focusing electrodes shown by the usual grid symbols, as is customary in cathode-ray tube circuits. The potentiometers, R1 and R2, control the intensity (brilliance) and focusing of the beam, R3 simply completes the bleeder circuit.


Mention has been made of the two "free" deflector plates where test voltages are connected. Actually, they are connected to ground through resistors of from one to ten megohms. These resistors would not be needed if all circuits under test provided a ground return path. But with such high values, the input signals will not be affected. If allowed to "float" entirely free, these plates would soon accumulate enough electrons to give them a negative charge

[Continued on page 53]

DEATH *before* DISHONOR!



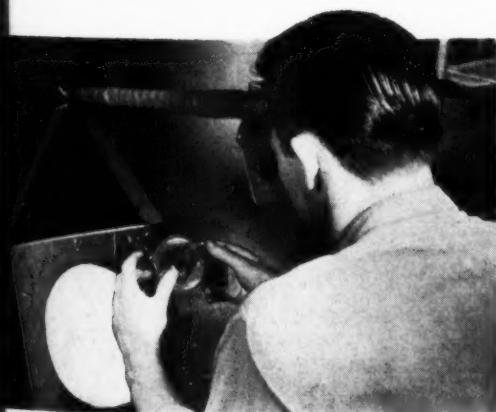Observation of the stress points on glass bead seals around vacuum tube leads is made with this device. Close-up photo above shows the actual view of a faulty lead. Note the change in polarized light creating distorted shadows which show up stress and strain in beads. Such strain sometimes occurs where metal and glass are sealed together.




Inspecting the entire glass bulb with the help of a polarized light. This device shows up stress and strain on the glass which might be created during the shaping operations.

Casual observation of a vacuum tube does not reveal its flaws. That's why Eimac engineers have developed many devices for the purpose of exposing even slight weaknesses in construction. The above is not a dungeon window, but a close-up photo of a faulty bead on a filament stem as viewed through a special bead testing device. Needless to say, this stem will never reach final assembly . . . better "death before dishonor" to the Eimac tradition of dependability.

Such care in production plus constant research into the phenomenon of the electron tube assures you of the utmost in performance from every Eimac tube . . . provides the answer to why Eimac tubes are first choice by most of the leading engineers throughout the world.

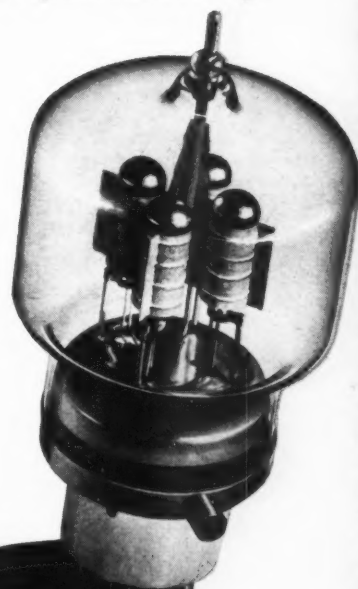Export Agents:
(**FRAZAR & CO., LTD., 301 Clay St.**)
San Francisco, California, U. S. A.



Follow the leaders to

Eimac
TUBES




Mfg. by Eitel-McCullough, Inc., San Bruno, California, U. S. A.

New Products

WORNER BLACKOUT WARDENS

Designed for the automatic blackout of signs, store windows, etc., these units have a range of 50 to 100 feet, depending on intensity of street light used as operating source.

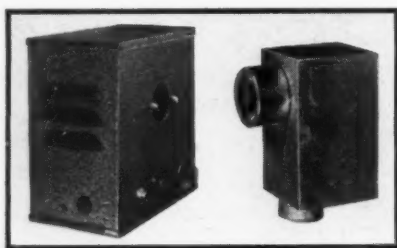Model 3001 is a single unit, with amplifier, relays, sensitivity regulators and photoelectric cell, all in one housing.



Model 3002 consists of two units; one being the Operating Unit and the other the Electric Eye Unit. No. 3002 is the same as No. 3001 in all other respects.

The Electric Eye Unit is weatherproof so that it may be located sufficiently close to a street light. Coaxial cable is used to connect the Electric Eye Unit to the Operating Unit. This may be up to 100 feet in length.


Relay contacts in both models are single pole, double throw, with capacity of 6 amps a.c. noninductive load and 2 amps inductive. Relay 3003 is provided for loads above 600 watts, and will handle up to 2000 watts.

Additional data may be obtained from the Worner Products Corp., 1019 West Lake St., Chicago.

★

A.A.I. ALARM SYSTEMS

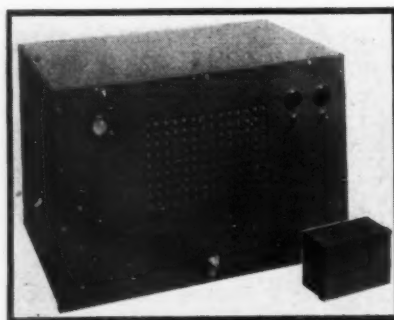Automatic Alarm Systems are designed for use in connection with steel wire fence. These alarm systems, although employing a new and improved method of protection, combine two tried and proven principles: the detection and



amplification of sound. The Detector is an inertia type, vibration instrument to be mounted on the guard fence at pre-determined intervals. The Indicator, located at a strategic point, is connected with the Detector unit and is designed to supply both an audible and visible warning of any attempt by saboteurs to scale, cut through or tunnel under the guard fence. The Indicator is built to operate on 110-120 volts, 60 cycles, and conforms with government requirements of uninterrupted operation at temperatures varying from 40 degrees below zero to 130 degrees above.


Illustrated is Model No. 11. This system is designed with a dual channel arrangement combined in a single unit, where the segregation of two sections of fence for separate alarms is advisable. It is supplied with six Detector units—three for each channel or section of fence—and will accommodate up to 12 Detector units.

A folder covering the complete details of the various models may be obtained from Automatic Alarms, Inc., Youngstown, Ohio.

★

"PLUG TYPE" SOLDERLESS TERMINAL

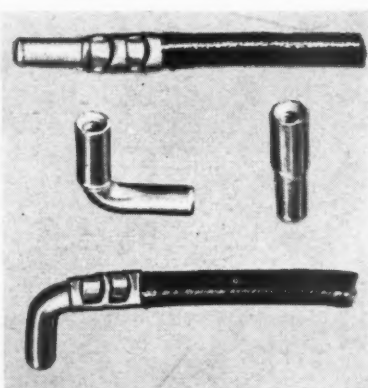A "plug type" terminal designed specifically for use on panel boards and rotary switches, on shipboard—or wherever plug-in wire connections are de-



manded—assures a durable, solderless connection. These terminals are available in straight and right angle shapes for wire sizes 16 and 14.


Easily installed—no special skill is required to crimp the terminal onto the wire end with the simple hand, bench or floor type crimping tools. The "plug type" solderless wire terminal is made of dead soft copper, annealed after fab-

rication to resist bending and breaking, and hot electro-tinned for corrosion resistance. For detailed information write for Bulletin No. 14 to Aircraft-Marine Products, Inc., 286 North Broad Street, Elizabeth, New Jersey.

★

SOLDERLESS TERMINAL WITH INSULATION SUPPORT

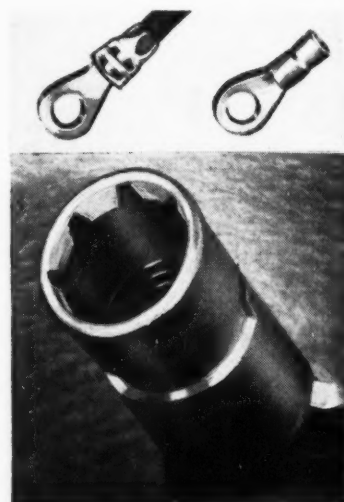A new terminal with insulation support, designed to meet demands for insulation protection in the lower wire gauges. Short and compact, the insulation support is designed to grip the insulation firmly without puncturing. This



new type terminal is available now for wire sizes 18, 20 and 22 and it will accommodate insulation diameters of A. N. specification.

The "Diamond Grip" insulation support sleeve is notched and folded in at the end to form a strong lip and a toothed grip, to prevent sliding. Only one operation is required with bench or floor type crimping tool for both wire and insulation crimp. Hand tools also are available. Eliminates taping, speeds up production.

Write for Bulletin No. 13 for full details to Aircraft-Marine Products, Inc., 286 North Broad Street, Elizabeth, New Jersey.

★

NEW R.C.P. INSTRUMENTS


New RCP instruments for laboratory and production use are described in the latest Radio City Products bulletin No. 126, slanted directly at America's wartime industry.

Typical of these new RCP models is
[Continued on page 51]

New Products

[Continued from Page 50]

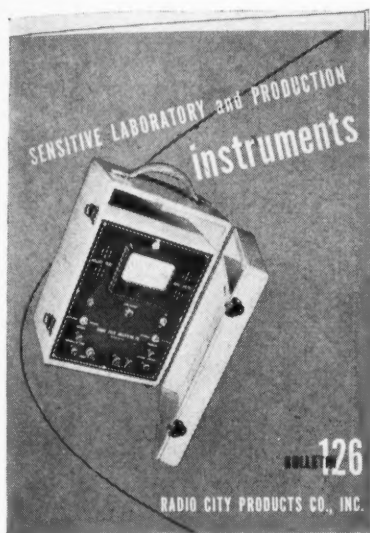a sensitive Electronic Limit Bridge for precision resistance testing, and a highly versatile multimeter for quick and accurate production line tests.



Copy of catalog will be sent on request. Inquiries should be addressed to the Engineering Department, Radio City Products Co., Inc., 127 West 26th St., New York City.



LIMIT SWITCH FOR AIRCRAFT SERVICE

A new lightweight limit switch designed especially for aircraft applications has been introduced by the General Electric Company.

The contact mechanism used is the G-E switchette. Snap action and double-break operation give the switch a high current rating. The switch is designed to meet all U.S. Army Air Force stipulations. The plunger operates with a 7/32 in. overtravel, which increases the number of applications for which the switch can be used.



The aluminum housing is made dust-proof by the use of a gasketed cover. There is adequate space inside the housing for easy wiring. The switch is available in three contact arrangements: single-circuit, normally open or normally closed; and single-pole, double-throw.

Each form can be furnished with a contact air gap of .010, .020, or .030 in. The switch weighs .13 lb.

• UTAH-CARTER PARTS •



DEPENDABILITY

is awake at the switch

● Here at the switch, where the human element and mechanical perfection must combine to assure top performance—Utah engineering and manufacture can be depended upon. Utah dependability is proving itself in hundreds of industrial electrical applications.

Utah Imp Push-Button Switches combine compact size, highest quality and economical price. Have finest nickel silver or phosphor bronze springs with integral contacts. Springs are fully insulated from the mounting, bushing and shaft—have high grade phenolic insulation. They are made in three circuit arrangements: “single make”—“single break”—one “break—make.”

Utah-Carter Rotary and Push-Button Jack Switches are made in long and short types. Small and compact they are designed to take minimum panel size. All electrical parts are fully insulated from the frame. Write today for full details.

UTAH RESISTORS have a minimum of two separately fired coats of vitreous enamel, forming a hard, glassy surface. Resistors 5-200 watts are available, either as Fixed, Tapped or Adjustable.



UTAH JACKS . . . The popularity of the “Imp” Jack is due to its compact size, highest quality and economical price. Its unique and patented design makes it the smallest jack to fit standard phone plugs. They are being used in connection with many war products.



UTAH PHONE PLUGS (2- and 3-Conductor Types)

They are designed to meet your needs—whether it's the application, size or shape.



WRITE FOR FULL DETAILS

UTAH RADIO PRODUCTS COMPANY

General Offices and Factory

846 ORLEANS STREET

CHICAGO, ILLINOIS

NEW METHOD OF PACKING RADIO TUBES

SAVES TIME, SPACE AND MATERIALS IN WAR EFFORT

A revolutionary new principle of packing radio tubes which, if utilized by the tube industry, will result in major contributions to the war effort in shipping space, material, handling and warehousing savings, has been developed by the manufacturers of RCA radio tubes.

By adopting the new method, RCA alone is saving some 120 tons of packing material a year, and is able to ship approximately twice as many tubes in a boxcar or truck, thus halving the need for critical shipping space. The new method supplants packing, handling, storing and shipping practices which have been common for many years.

To extend the value of the new packing principle more quickly, RCA has granted patent rights to the new type cartons to other tube manufacturers. In addition, other tube manufacturers have been shown factory routines that have been developed to make the most efficient use of the new process.

The American Standards Association is studying the possibilities of setting up an American War Standard covering the packaging of electronic tubes as a result of RCA's pioneering effort. Far reaching effects are expected of the new packaging principle in many fields.

The new packing ideas were developed by Charles I. Elliott, a 27-year-old packing engineer who was employed by the RCA tube division to study the Company's methods of handling tubes during the manufacturing process, and preparing them for warehousing and shipping.


Old Systems Scrapped

Mr. Elliott found that existing packing methods required the use of 210 separate pieces of packing material per 1000 tubes. Improvised handling methods were used in the factory where tubes travel from one assembly operation to another. A packing box of 22 parts, some of them no longer obtainable, was used to store and ship glass tubes.

When he had finished re-designing packing cases, Mr. Elliott found that he had reduced the 210 pieces of packing per 1000 tubes to 24 pieces. He discovered that a single one-piece, tray-like container, planned to hold the tubes safe within shipping cases, could also be used to save time in the manufacturing processes.

Standardization Important

Standardization of tube packages is

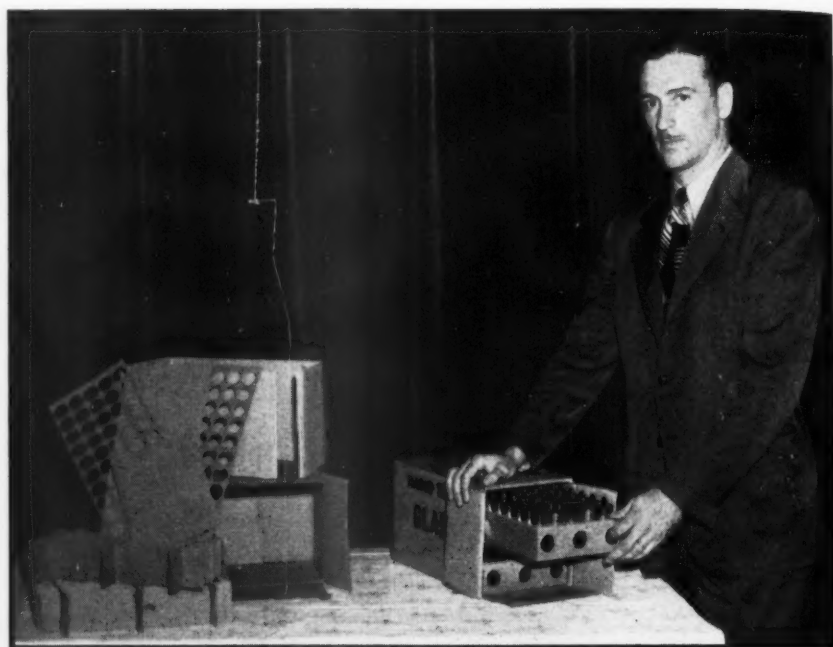

Charles I. Elliott, RCA packing engineer who developed the new method of packing radio tubes, demonstrates how 100 tubes may be packed in a sturdy carton for shipment while protected in two single piece heavy cardboard trays. To the left is shown the many pieces of packing material formerly required to pack the same number of tubes, indicating the savings in material made possible by the new method.

vitaly important in wartime for many reasons. Spare radio tubes can be made to fit into spaces designed for them by the builders of planes, tanks, mobile units, ships and other fighting equipment. And the tube packages will fit the spaces, no matter from which factory they originated. This is a vital consideration with U. S. fighting equipment in action in many parts of the world.

In handling receiving tubes alone, savings of 30 per cent in material were found to have been achieved by the new methods. Factory handling efficiency has been stepped up 20 per cent, loss by breakage has been materially reduced, as has the need for storage space. It is now possible to pack 647,500 tubes of a given type into a single boxcar, an increase of nearly 100 per cent in capacity.

A further improvement in the handling of the smaller types of receiving tubes has been made in the form of a "clip" of cardboard which holds 10 tubes. During testing, warehousing and branding operations, the "clip" of ten tubes is handled as a unit. However, when the time comes for the tubes to be packed into individual cartons for shipment, the "clip" is torn into 10 pieces along perforated

lines, to become the interior support for each tube in its individual carton. Further, the old 31-piece glass tube carton had resolved itself into a smaller, eleven-piece box.

Every Tube Type Aided

Tremendous advantages have been found in the new system in the handling of every type tube. In the case of a certain type power tube, a wooden box used to transfer small quantities about the factory and to the warehouse has given way to a more compact cardboard box in which the tubes are transported with greater protection from breakage.

One universal box has been designed for packing all types of power tubes of the same size, supplanting a large number of various sized special boxes. Ingeniously designed inner supports do away with the layers of wadding once used, while the application of simple laws of physics provides greater safety for the tubes when the box is subjected to unusual stress.

In the case of cathode ray tubes, the empty glass bulbs are now received at the RCA factory from the glass works in the same packing cases in which they are transported

[Continued on page 53]

throughout the manufacturing, testing, warehousing and shipping processes. So much has been saved in the cost of the packing cases that the glass company has agreed to furnish them to RCA without cost.

Mr. Elliott's work has been carried on under the direction of L. E. Mitchell, Manager of the Industrial Engineering Department devoted to the development of better methods through work simplification.

"Kit" Packing

Perhaps most ingenious of all the new packing methods is that designed for "kit" packing of tubes, used to provide in one package the several types of tubes required for factory assembly of radio equipment and the tubes needed as replacement parts. It was formerly necessary to keep a stock of all sizes of kit packages. Now one single size box is provided for all types of kits. It is changed in size and shape by being torn the proper way along carefully designed perforated lines. Larger packing cases in which the kits are shipped are made to telescope, so that they can be made larger or smaller as needed.

"All the new containers are fabricated so that they can be laid out flat," Mr. Mitchell explained. "None of them is stitched or glued. The result is that empty cartons can be stored in one tenth the space formerly required. Further, we are able to have the empty cartons returned from our customers time and time again at nominal expense, still further increasing savings in strategic materials, facilities and manpower."

Theory of 'Scope

[Continued from Page 48]

and shift the beam completely off the screen.

The heater supply is connected to a transformer which furnishes 2.5 or 6.3 volts to the filament, depending on tube type. In the smaller tubes the cathode is connected to one side of the filament, within the tube.

The high-voltage leads are connected to the rectifier output of the power supply. It should be noted, though, that the *positive* lead is grounded, which is contrary to receiver practice.

Sweep Circuits

What is the "sweep circuit" and how does it function? This is one of the first puzzling questions of those to whom the oscilloscope is new. We are all familiar with those graphs which engineers use to show the relation of one function to another. Take the old familiar sine wave, for example, a graph of which appears in Fig. 10.

To the left we find a vertical line representing instantaneous voltage values. At the bottom is found a notation of the time in which these changes

take place, being $1/60$ of a second in this case.

Now we will see how this same curve would be plotted on the cathode-ray screen. Facing the front of the tube

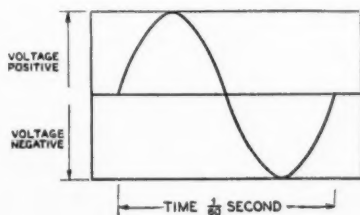


Fig. 10. Graph of a single sinusoidal wave.

would be seen the four deflecting plates if the screen were removed, and we would see the electron stream as a tiny dot if it were visible. (Fig. 11.)

The secondary of a transformer is here connected to the vertical plates so the beam will be moved up and down in accordance with the voltage. The voltmeter will read the r.m.s. voltage across the secondary, but the beam will follow the *instantaneous* potential. With no voltage on the horizontal plates, a fine vertical line will appear on the screen. Since this line represents the voltage changes from minimum to maximum, it is possible to measure the peak voltage directly with a ruler placed on the screen, provided the oscilloscope's sensi-



MICA CAPACITORS

"Quality Above All" mica capacitors add reliability to the communications equipment used by the Armed Service Branches of our Government. This self-same dependability is available to you! Standardize on Solar micas—as well as dry, wet and paper capacitors—for satisfactory, uninterrupted service.

Special Catalog 12-E Available On Letterhead Request

SOLAR MFG. CORP., Bayonne, N. J.

tivity has been previously determined.

Examining the remaining apparatus we find a battery with its center cell grounded and its positive and negative terminals connected across a potentiometer P, the slider arm A of which goes to the free horizontal plate. It is plain, then, that the beam will be moved to the right or left, depending upon the arm position.

This latter member is connected to a lever which follows the contour of a cam, C, being turned by a synchronous motor operating from the line under test.

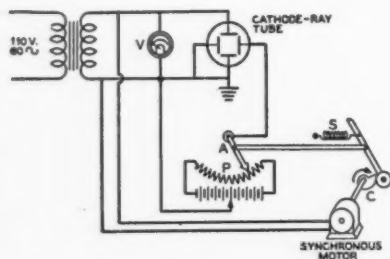


Fig. 11. Mechanical sweep circuit.

As the cam revolves, the slider arm will be drawn from left to right at a uniform rate and the electron beam will follow simultaneously. As the maximum lobe on the cam turns by its follower, the lever L and slider A are instantly snapped back to the left position by the spring S, and the sweep cycle starts all over again.

It will be apparent that during this cycle the beam has been deflected vertically by the voltage under inspection, and horizontally by the sweep circuit mechanism. If the cam is geared to the synchronous motor so as to revolve 60 times per second the beam will trace a pattern upon the screen similar to Fig. 10.

In one second's time the beam will traverse the screen 60 times, making a trace each time. But since the sweep mechanism moves in perfect synchronism, each trace will cover the exact position on the screen as did all preceding traces. Instead of seeing a moving pattern, then, the electrical wave appears to be "stopped in its tracks," permitting study as long as desired.

The above applies, of course, only if the phenomena is recurrent (and the sweep synchronized) but this condition holds true for most electrical phenomena in which we are interested.

Any transient surges occurring during this study will register as a deviation from the normal waveform, and appear as a fine line, diverting from the true waveform. They will glow for an instant, and then disappear.

While such a mechanism as above described might work at very low frequencies, it is quite evident that a better means must be found for sweeping the beam at frequencies varying from 15 to 10,000 cycles per second, or more.

The Relaxation Oscillator

While there are several types of electronic oscillators that will perform the

function of producing a linear sweep, the relaxation oscillator is the simplest and most adaptable to our work. This type oscillator is used in all present-day commercial oscilloscopes.

It is also known as the "saw-tooth" oscillator, linear timing axis, grid-glow or thyatron oscillator, and perhaps another name or two. Its action is quite simple, but because it may be unfamiliar to some, it will be described in detail.

Evolution of Linear Timing Circuit

We have seen from the mechanical arrangement just described that a sweep

oscillator must move the beam at a uniform rate in one direction and return to its starting point instantaneously. It is quite apparent, then, that our usual sine-wave oscillators are not suitable for this particular job.

The problem is to develop a suitable voltage for horizontally deflecting the beam and then to provide a means for instantly reducing this voltage to zero.

A simple neon oscillator is shown in Fig. 12. Current from the d.c. input circuit, flowing through resistor R, charges condenser C. The neon bulb N, has no effect until its flashing voltage (50 or

[Continued on page 56]

this war can't be won without RELAYS

- ★ You need Relays and Solenoids for timing, fusing and releasing bombs . . . Solenoids to fire the guns . . . Relays to control the radio—floodlights—landing gears—navigation aids—turrets.
- ★ GUN SWITCH HANDLES
- ★ REMOTE FIRING EQUIPMENT
- ★ TURRET CONTROLS
- ★ RADIO CONTROLS
- ★ NAVIGATION CONTROLS
- ★ AIRCRAFT CONTROLS
- ★ BOMB RELEASES
- ★ SOLENOID CONTACTORS

Used in practically every type warplane . . . government specified Relays by Guardian are the finest electrical controls we've ever designed . . . more control in less space . . . more room for guns and bombs . . . all done with a "know how" that's unmistakably—Guardian Electric!

P. S. — Samples only available now for that "after it's over" product.

GUARDIAN ELECTRIC
1605 WEST WALNUT STREET CHICAGO, ILLINOIS
LARGEST LINE OF RELAYS SERVING AMERICAN WAR INDUSTRY



A new printing will be ready about August 8th

Your favorite dealer may have a copy left; we haven't.

The radio engineer's and technician's own handbook. More information which you want than in any comparable work. Clothbound, 640 pages, profusely illustrated. See it at your favorite dealers.

\$1.75 postpaid in Continental U.S.A.; elsewhere, \$2.00 postpaid

Published by

The Editors of "Radio" 77 Bedford Street
STAMFORD, CONN.

Theory of 'Scope [Continued from Page 54]

60 volts) is reached. At this point, gas within the bulb ionizes, rendering the bulb a conductor, and instantly discharges condenser C as if it were a short circuit.

When the voltage across condenser C

becomes reduced to almost zero, the neon gas de-ionizes, suddenly restoring the bulb to its former status of an insulator. Here another cycle of operation begins as condenser C begins "filling up" with another charge.

The frequency of operation is determined by the time required for charging condenser C . By selection of proper capacity values, and by making R variable, oscillation of any frequency from a few cycles up to many thousands may be obtained.

While extremely simple, this oscillator has three major faults which must be corrected before it can be used in a first-class oscilloscope.

First; its output, which will be slightly less than the neon bulb's flashing potential, is not sufficient to swing the electron beam completely across the screen.

Second; its frequency is not easily synchronized to the signal frequency. And third; as the condenser becomes more and more charged, its charging rate decreases, hence the output voltage does not increase linearly with respect to time.

Now, what to do about it! The first fault, insufficient output, is overcome simply by hooking on a stage of amplification.

Fault number two is remedied by changing to a thyatron tube, this being a more or less glorified version of the neon bulb. It looks just like a 76 but behaves differently.

A simple thyatron oscillator circuit is shown in Fig. 13. Instead of the neon bulb is a type 884 or 885 gas-triode (thyatron), which has a heater, cathode and plate—but has a little inert gas mixed with its vacuum content. Its action is quite similar to the neon bulb, except that its flashing voltage may be set to any predetermined value by application of proper grid bias potential E_c .

Two more resistors, R_1 and R_2 , have been added to the circuit. The former simply limits the maximum charging rate, while the latter prevents C_1 from discharging more rapidly than the little tube will stand.

It is a characteristic of type 884 and 885 tubes, that discharge will occur whenever the plate potential reaches about seven times the negative grid bias value. Since we will amplify the output voltage anyway, we can fix the flashing voltage at about 20 volts by biasing the grid to about—3 volts. This gives plentiful output and makes the saw-tooth wave linear in the bargain, the explanation of which will follow.

We have already mentioned that a condenser takes its charge in exponential fashion. The curved and dotted line in Fig. 14 shows this charging character-

istic. The condenser starts charging fast but slows down as its potential approaches that of the charging voltage.

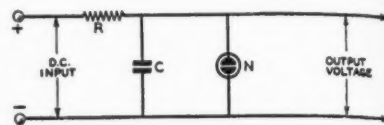


Fig. 12. Simple neon oscillator.

If such tank condenser is "flashed" when about half full its charging curve will be "rounded" like the solid line. Such a curve will make the pretty patterns on our cathode-ray screen rather distorted.

However, if the thyatron is set for a low flashing voltage—that is, only five or ten per cent of the d.c. charging voltage, this charging curve will be essentially linear, as shown in Fig. 15. Here we flash the condenser before its curve starts bending to any appreciable extent.²

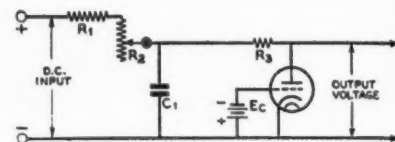


Fig. 13. Simple gas-triode (thyatron) oscillator circuit.

Synchronization

And now, about synchronization. We stated that the flashing voltage was determined by the thyatron's grid bias. If a small potential—less than a volt being required—is fed back from the signal under inspection to this thyatron grid, the tube will flash, always at the instant a certain signal voltage is reached.

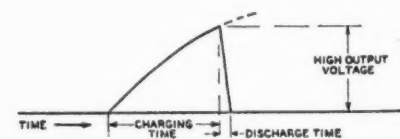


Fig. 14. Effect of operating at a high flashing voltage.

²Another method of obtaining a linear output voltage is frequently found in television receiver designs, and in some of the older oscilloscopes. Instead of flashing the thyatron at a low potential, this method flashes at a much higher value; that is, two or three hundred volts, thereby eliminating the amplifier. By substituting a pentode tube for the current limiting resistor R , current flow to the tank condenser is limited to a constant rate. This method, however, is just as complicated as the low-flash-and-amplify method and is not nearly so flexible. Also, with the low-flashing circuit, the amplifier is also available for amplification of external signals, if desired, making it much more suitable for oscilloscopic use.

[Continued on page 58]



A Fair Sales-Policy

In the bargain-trays of radio stores, there is one make that is conspicuous by its absence . . . Mallory. There are good reasons why Mallory products are not offered at ridiculously low prices.

Mallory Approved Precision Products have always been built up to quality and not down to price. Quality in the materials used. Quality in their fabrication into radio parts. Quality in their inspection.

We believe our sales-policy is a fair one. It is based on high quality without the penalty of high price. The maintenance of this quality costs Mallory real money, but it is your assurance of dependability.

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address — PELMALLO



12 **BIG ISSUES FOR** \$3



"RADIO" Subscription Rates

RADIO is now published twelve times annually.

\$3⁰⁰
for one year

\$5⁰⁰
for two years


in U.S.A. only. To Canada (inclusive of current taxes), Newfoundland, Spain, and Pan-American countries, add 50c per year. Elsewhere, add \$1 per year.

Note: Because of wartime censorship restrictions, we must reserve the right to withhold from foreign subscribers any issue the regular domestic edition of which is not approved by the authorities for export without changes. In such cases subscriptions will be extended so that each subscriber will eventually receive the number of issues to which he is entitled.

The Editors of "Radio" 77 Bedford Street
STAMFORD, CONN.

A potentiometer, R_4 in Fig. 16, provides control of the synchronizing potential. This voltage is usually taken from the signal voltage on the free vertical deflection plate, but in some cases from the signal, itself and occasionally from

Fig. 16. Complete sweep circuit, consisting of sawtooth oscillator and horizontal amplifier.

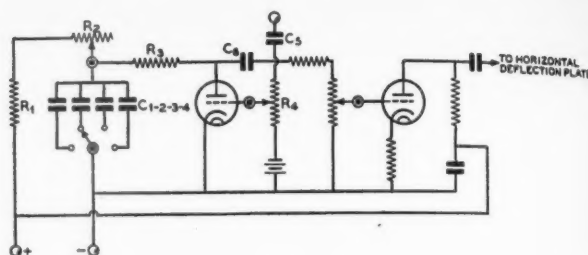

Our experience in building precision crystal units for the United Nations Armed Forces will be reflected in better Bliley Crystal Units

for the Greater Amateur Radio of the Future



BLILEY ELECTRIC CO.
UNION STATION BUILDING ERIE, PA.

the 60-cycle a-c power source.

Something should be said of the polarity of output, both from the tank condenser C , and the complete sweep circuit, with amplifier. Referring to the first portion of Fig. 17 will be found the "saw-tooth" waveform across the tank condenser. This voltage varies from a few volts above ground to the flashing potential of the thyatron. Note that this voltage is *always positive*. The waveform is a saw-tooth pulse, rather than an alternating current wave, at this point. However, the oscillator is coupled to the horizontal amplifier grid through a coupling condenser C_6 , Fig. 16. Here on the amplifier grid we will find the same saw-tooth characteristic. But the amplitude is now divided half above and half below our ground line of zero potential.

Now after amplifying this wave, we find that the amplifier has shifted its phase 180 degrees, as will be seen in the last portion of Fig. 17. This phase reversal is of no real importance, though. If the cathode-ray tube is mounted so the free horizontal plate is at one's left, the sweep cycle will begin at that side, travel to the right, and then snap back to start the cycle all over again. Our cathode-ray screen graphs will be correctly plotted from left to right, in relation to time.

About Amplifiers

In small commercial oscilloscopes one usually finds one vertical and one horizontal amplifier. The larger models, using five-inch tubes or larger, are usually equipped with two vertical amplifiers.

The vertical amplifier simply builds up the signal under test to sufficient amplitude to deflect the electron beam to the desired degree.

The chief purpose of the horizontal amplifier is to amplify the saw-tooth timing wave, as previously described, largely in the interest of linearity.

There is nothing unusual about either of these amplifiers, except that they should operate with as little distortion and have as flat

Fig. 15. Obtaining sweep-circuit linearity by means of a low flashing voltage.


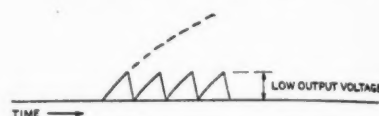


Fig. 17. Pulsating oscillator output becomes a.c. on output side of coupling condenser.

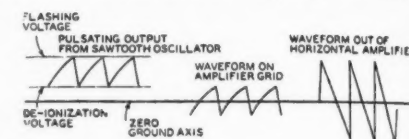

a frequency characteristic as can be obtained.

A flexible switching arrangement is always provided to make the oscilloscope as versatile as possible.

News

SIGNAL CORPS NEEDS INSTRUCTORS

The Board of Education is about to embark upon a new venture of training men for the Signal Corps.

They are interested in securing instructors for this program which will be conducted by the Public Vocational Schools for the various states. Those interested should contact the nearest U. S. Employment Service Office.

★

JEFFERSON-TRAVIS OPENS WASHINGTON OFFICE

The Jefferson-Travis Radio Mfg. Corp. announces the opening of a branch office in Washington, D. C., for the purpose of assisting U.S. Government Departments with respect to radio communication equipment being manufactured by the Company under government contracts.

Mr. F. Lee Hardesty will be in charge of the new office which is conveniently located at 1026 17th Street, N.W. Mr. Hardesty has resigned his position in the radio procurement division of the British Air Commission to accept this new post.

To assist in this work a member of the Jefferson-Travis engineering staff will be permanently stationed at the Washington office, so that the Company's production methods and facilities will be readily available to the U.S. Government Departments.

G. E. SHIPS TRANSMITTER FOR W75NY

General Electric has shipped an f-m. broadcast transmitter and associated equipment to New York City's newest f-m. station, W75NY, to be operated by Metropolitan Television, Inc. The station is the seventh in the New York area and is owned jointly by Bloomingdale's and Abraham & Straus department stores.

Construction of the station, atop the Hotel Pierre, was begun in mid-March under the direction of Louis Thompson, who has been placed in charge of the station.

The FCC assigned a Class B f-m. permit for the use of 47.5 mc. to Metropolitan Television, Inc., last year.

★

REQUIREMENTS FOR AERONAUTICAL STATION OPERATORS RELAXED

The Federal Communications Commission on June 16, through its Order No. 102, upon recommendation of the Defense Communications Board, modified certain of its rules for a period of five years or until further order of the Commission, to provide a relaxation of its operator requirements for aeronautical stations utilizing telegraph transmission. (These are ground stations used in connection with aeronautical operations.) This action permits operation of an aeronautical or an aeronautical fixed station by the holder of a radiotelephone permit or radiotelephone license bearing an endorsement attesting

to the holder's ability to transmit and receive at least 16 code groups, International Morse Code, per minute.

This action is designed to relieve the rapidly growing shortage of skilled operators being caused by war-time conditions and the requirements of the military forces for radio operators. It specifically looks forward to the possibility of training women to assume these duties by providing for such operation without the detailed technical qualifications necessary for the more technical grades of licenses.

It will be necessary, however, at each station where holders of the restricted radiotelephone operator permits are employed as operators, that at least one first or second class radiotelegraph or radiotelephone operator, or, in lieu thereof, in a station using type A-1 or A-2 emission only a holder of a restricted radiotelegraph operator permit, be assigned to the station at all times for the purpose of making proper adjustments to the equipment and who shall be responsible for the proper operation of the station. This provision, however, will not relieve the station licensee of his responsibility for operation of the station in accordance with the Rules and Regulations of the Commission.

Holders of radiotelephone operator permits or licenses may obtain the required radiotelegraph endorsement by appearing at any of the Commission's District Field Offices or at the Wash-

ington, D. C., office and demonstrating their ability to transmit and receive at least 16 code groups per minute in International Morse Code. The endorsement will then be written on the face of the permit by the examining officer.

★


WARTIME CONDENSER CATALOG

This is war. That is the keynote of the new 1942 Aerovox Catalog just off the press. Starting out with a cover that reflects the stern atmosphere of the huge plant working day and night on the radio fighting and home fronts, the catalog lists those essential condensers, resistors and test instruments in popular demand and therefore still produced, stocked and available for prompt delivery. A further wartime note is the inclusion of several pages of motor-starting replacement capacitor listings, in acknowledgment of widespread and growing demand for refrigerator maintenance. A copy of this catalog may be had by addressing Aerovox Corporation, New Bedford, Mass., or through the local Aerovox jobber.

★

SYLVANIA ORGANIZATION CHANGE

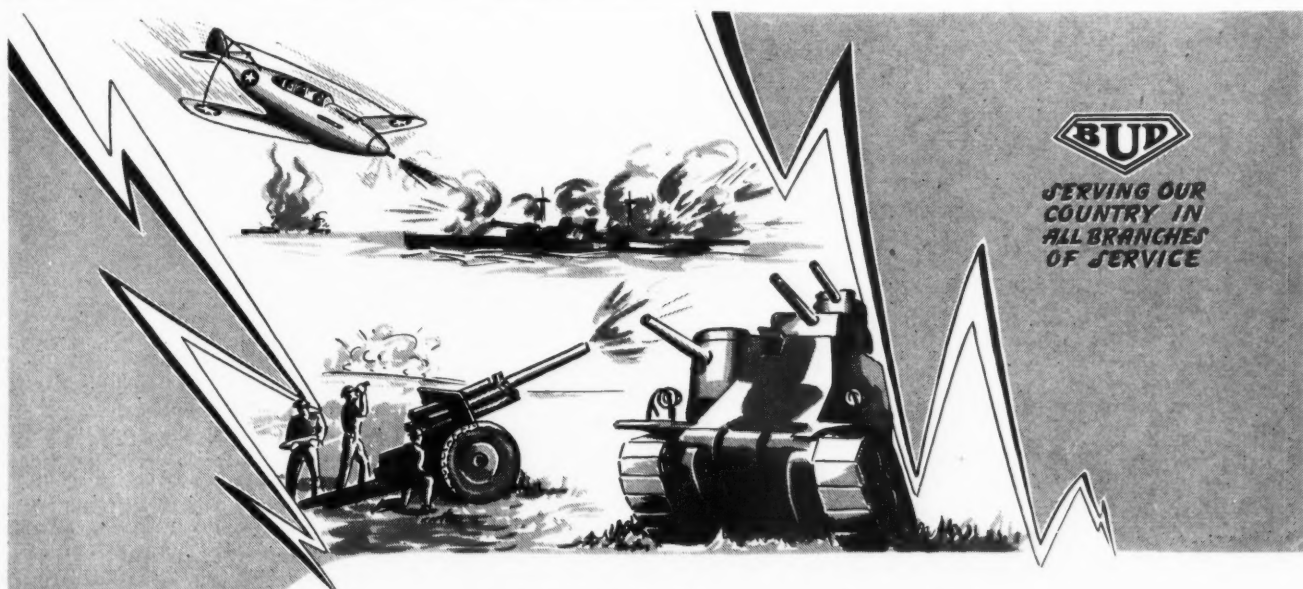
M. F. Balcom, Vice President and General Manager of the Radio Tube Division of the Hygrade Sylvania Corporation, announces two top executive organization changes. This, at the same time, effects a rearrangement of duties down the line which streamlines



BUD Is in the Service

• In modern warfare, radio communications play a vital part in knitting our many combat units into one powerful striking force. As component parts of essential communications units, BUD products are on the firing line, doing their part to assure victory for America.

BUD RADIO, INC.,
CLEVELAND • OHIO

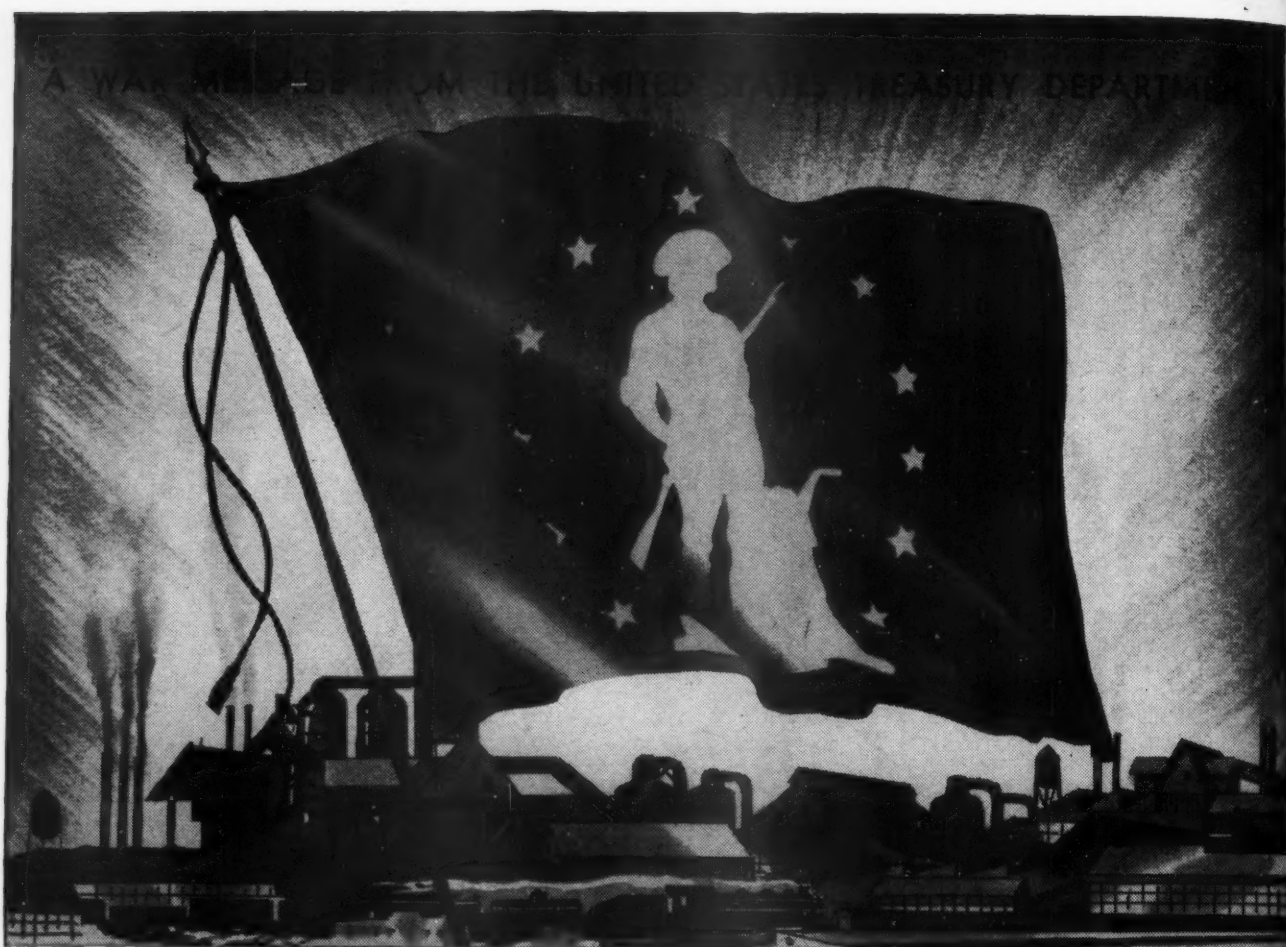

Next to the Stars and Stripes . . .

AS PROUD A FLAG AS INDUSTRY CAN FLY

Signifying 90 Percent or More Employee Participation in the Pay-Roll Savings Plan

IT doesn't go into the smoke of battle, but wherever you see this flag you know that it spells Victory for our boys on the fighting fronts. To everyone, it means that the firm which flies it has attained 90 percent or more employee participation in the Pay-Roll Savings Plan . . . that their employees are turning a part of their earnings into tanks and planes and guns *regularly*, every pay day, through the systematic purchase of U. S. War Bonds.

You don't need to be engaged in war production activity to fly this flag. Any patriotic firm can qualify and make a vital contribution to Victory by making the Pay-Roll Savings Plan available to its employees, and by securing 90 percent or more employee participation. Then notify your State Defense Savings Staff Administrator that

you have reached the goal. He will tell you how you may obtain your flag.

If your firm has already installed the Pay-Roll Savings Plan, now is the time to increase your efforts: (1) To secure wider participation and reach the 90-percent goal; (2) to encourage employees to increase their allotments until 10 percent or more of your gross pay roll is subscribed for Bonds. "Token" allotments will not win this war any more than "token" resistance will keep our enemies from our shores, our homes. If your firm has yet to install the Plan, remember, **TIME IS SHORT.**

Write or wire for full facts and literature on installing your Pay-Roll Savings Plan now. Address Treasury Department, Section D, 709 12th St., NW., Washington, D. C.

Make Every Pay Day "Bond Day"



U. S. WAR Bonds ★ Stamps

This Space is a Contribution to Victory by RADIO

radio tube manufacturing and engineering activities in order to continue to meet the growing demands of war production.

H. Ward Zimmer, General Manufacturing Manager, is appointed General Manager of Operations of the Receiving Tube Division, which includes three plants in Pennsylvania, and one in New England. In continuing his general manufacturing managership, he will be in charge of equipment design and production, and general division purchasing.

R. M. Wise, Chief Radio Tube Engineer, is named General Manager of Operations, Special and Large Tube Division, which includes three other Pennsylvania plants. Continuing his general engineering responsibility as General Engineering Manager, Mr. Wise will be responsible for radio tube research and development engineering, commercial engineering and production development.

★

V. H. FRAENCKEL APPOINTED TO G-E RADIO, TELEVISION AND ELECTRONICS DEPT.

V. H. Fraenckel will have charge of the co-ordination of commercial engineering of all product lines of the General Electric Radio, Television and Electronics Department, according to a recent announcement by Dr. W. R. G. Baker, Vice President. G. F. Metcalf, formerly in charge of this work, has entered the U. S. Army with the rank of Lieutenant Colonel, Signal Corps. Mr. Fraenckel will report to G. W. Henyan, Manager of the Transmitter and Tube Divisions of the Department.

★

W. P. SAUNDERS COMMISSIONED

W. P. Saunders, Senior Business Specialist in the Office of Price Administration in Washington, has been granted leave of absence to assume active duty as a Captain with the U.S. Army Signal Corps.

Captain Saunders has been identified with the radio industry since 1918.

In October of 1941, at the request of Merle Fainsod, now Director of the Retail Trade and Services Division of the Office of Price Administration, he assumed duties with the Radio Unit of the Durable Goods Section, where he has assisted in the administration of prices of radios.

FOREIGN REFERENCES ON CRYSTALLOGRAPHY

(From the book "Piezoelektrizitat des Quarzes")

Curie, J., und P., C.R. Acad. Sci. 91, 294 (1880); Curie, P. Oeuvres Paris 1880.

Hormann, E., ETZ. 56, 1321 (1935). Sawyer, C. B., Proc. Inst. Rad. Eng., 19, 2020 (1931).

Hauy, S. Gehler's Physikal. Worterbuch, III. Bd. (E), 255 (1827).

Bequerel, A. C., Ann. Chim. et Phys. 36, 265 (1827).

Pavlik, B., Z. Physik 107, 458 (1937).

Lippmann, M. G., Ann. Chim. et Phys. (5) 24, 145 (1881).

Schulze-Herringen, E., Z. Techn. Physik 17, 468 (1937).

Bergmann, L., Physik, Z. 36, 31 (1935).

Engl. J., and J. P. Leventer, Ann. Physik 29, 369 (1937).

Hettich, A., und A. Schleede, Z. Physik 50, 249 (1928).

Hartley, L. J., und R. H. Rinaldi, Proc. Phys. Soc. 38, 273 (1926).

Illgen, H., Z. Techn. Physik 18, 470 (1937).

Langevin, A., J. Physique Radium (7) 95 (1936).

Wooster, A. W., Mineral. Mag. 22, 65 (1929).

Knol, K. S., Proc. Amsterdam 35, 99 (1932).

Dawson, L. H., Physic Rev. 29, 532 (1927).

Dye, W. D., Proc. Roy. Soc. 138, 1 (1932).

Tschappat, W. H., Mech. Engg. 48, 819 (1926).

Karcher, J., Physic. Rev., 18, 107 (1921).

Watanabe, S., Scient. Paper, Inst. Phys. Chem. Res., Tokyo 12, 82 (1929).

Hocart, R. J., Physique Radium 9, 95 (1928).

Kluge, J., und E. H. Linckh, Z. Ver. Dtsch. Ing. 73, 1311 (1929).

Kluge, J., und E. H. Linckh, Z. Ver. Dtsch. Ing. 74, 887 (1930).



HELP YOURSELF and YOUR GOVERNMENT

WE PAY highest cash prices immediately for used communications receivers and transmitters.

If you are going into the armed services, or, for any reason wish to convert your equipment into cash, contact us at once. You will receive the same prompt and fair consideration when selling to us as when buying from us. You will help win the war because we are supplying the government with equipment urgently and immediately needed.

Write, telephone or telegraph us description of your used communications receivers and transmitters of standard make; you will be paid cash immediately without bother or red tape.

We also have a store at 2335 Westwood Blvd., West Los Angeles, Calif.

COMPLETE STOCKS

★ We still have large stocks of receivers, 2 1/2 meter equipment, meters, tubes, transformers, resistors, condensers, panels, chassis, and radio parts of all sorts. We sell and rent code teaching equipment. Your orders and inquiries invited.



"WORLD'S LARGEST DISTRIBUTOR OF COMMUNICATIONS RECEIVERS"



2


Handy Aids for Resistance Problems Today!

**New OHMITE
Quick Reference
Catalog 18 FREE**



Gives up-to-date information on the wide range of Ohmite stock resistors, rheostats, chokes and switches used in all types of applications. Helps you select the right units for each job easily, quickly. Send for Catalog 18 now — it's Free.

**Handy OHMITE
Ohm's Law
CALCULATOR**

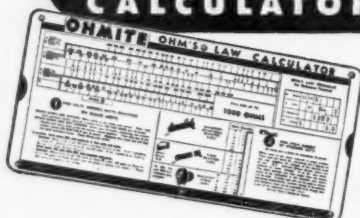

Figures ohms, watts, volts, amperes — quickly, easily. Solves any Ohm's Law problem with one setting of the slide. All values are direct reading. No slide rule knowledge necessary. Size 4½" x 9".

Yours for only 10c. At your Jobber or send coupon.

OHMITE MANUFACTURING CO.
4866 Flournoy St., Chicago, U.S.A.

☐ Send Free Catalog 18.
☐ 10c in coin enclosed. Send Ohm's Law Calculator.

Name _____
Address _____
City _____ State _____ Radio—July, '42

Be Right with OHMITE
RHEOSTATS — RESISTORS — TAP SWITCHES

Kluge, J., und E. H. Linckh, A. Forsch. Ingenieurwes. 2, 1953 (1931).
Kluge, J., und E. H. Linckh, Z. Forsch. Ingenieurwes. 4, 177 (1933).
Kluge, J., und E. H. Linckh, Arch. techn. Messen 5, 132 (1932).
Fahrentholz, S., J. Kluge and H. E. Linckh, Physik. Z. 38, 73 (1937).
Langevin, M., J. Physique Radium 7, 448 (1936).
Muraour, H., A. Langevin und G. Aunis, J. Physique Radium 7, 450 (1936).
Joachim, H., und H. Illgen, Z. ges. Schieb—u. Sprengstoffwesen 27, 76, 121 (1932).
Elings, S. B., und P. Terpstra, Z. Kristallogr. 67, 279 (1928).
Hettich, A., Z. Physik, 65, 506 (1930).
Greenwood, G., Z. Kristallogr. 91, 235, (1935).
Hettich, A., Z. Physik. Chem. 168, 353 (1934).
Hettich, A., und H. Steinmetz, Z. Physik 76, 688 (1932).
Engl. J., und J. P. Leventer, Naturwiss. 24, 217 (1936).
Bergmann, L. Zbl. Mineral., Geol., Palaont. Abt. (a) 1935, 213.
Neuhaus, A., Z. Kristallogr. 90, 415 (1935).
Voigt, W., Lehrbuch der Kristallphysik (Leipzig und Berlin 1910).
Chatelier, H. L., La silice et les silicates (Paris 1914).
Perrier, A., und R. de Mandrot, Arch. Sci. Physiques et Naturelles 4, 367 (1920). —, u. F. Wolfers, ebenda, 2, 372 (1920).
Rinne, F., Crystals and the Fine Structure of Matter (London 1924).
Seidl, F., Z. Physik, 75, 488 (1932).
Joffe, A., La conductibilite electrique des cristaux (Paris 1927).
Sakisaka, Y., Jap. Jour. Phys. 4, 171 (1927).
Fox, G. W., und P. H. Carr, Physic. Rev. 37, 1622 (1931).

Matsumura, S., und S. Kanski, Rep. Rad. Res. and Works Japan 2, 35 (1932).
Fox, G. W., und J. M. Cork, Physic. Rev. 38, 1920, (1931).
Kautter, W., Telefunken-Ztg. 18, Heft 77, 42 (1937).
Malsch, J., Physik, Z. 33, 19 (1932); Ann. Physik 12, 865 (1932).
Debye, P., Physik, Z. 35, 35 (1934).
Hankel und Lindenberg, Abhdig. Kgl. Sachs. Ges. Wissensch. 18, 392 (1893).
Busch, G., und P. Scherrer, Naturwiss. 23, 737 (1935).
Wooster, W. A., Z. Kristallogr. 74, Ref.-Bd. S. 105 (1930).
Curie, P., Traite de Radioactivite 1, 98 (1910).
Rontgen, W. C., Ann. Physik 41, 449 (1913).
Lissauer, W., Diss. (Mucchen 1907).
Perrier, A., Z. Physik 58, 805 (1922).
Fredericksz, V., und G. Michailow, Z. Physik 76, 328 (1932).
Andreeff, A., V. Fredericksz und I. Kazarnowsky, Z. Physik. 54, 482 (1929).
Laue, M. V., Z. Physik 34, 347 (1925).
Dye, D. W., Proc. Phys. Soc. Lond. 38, 399 (1926).
Vigoureux, P., Philos. Mag. 6, 1140 (1928).
Szekely, A., Z. Physik 78, 560 (1932).
Nubbaumer, B. Z. Physik 78, 781 (1932).
Schulwas—Sokokina, R. D., Physic. Rev. 43, 1448 (1929).
Burton, E. F., A. Pitt und D. W. R. McKinley, Nature 137, 708 (1936).
Dobberstein, H., Naturwiss, 24, 414 (1936).
Omnes, H. K., und A. Beckmann, Leiden Comm. 1912, 132f.
Osterberg, H., Physic. Rev. 49, 552 (1936).
Van Dyke, K. X., Physic. Rev. 42, 587 (1932).

HALF PRICE SUBSCRIPTIONS . . .

for Men in the U. S. Armed Services

Subscriptions to "RADIO" addressed to men in the U. S. Army, Navy, Marine Corps, or Coast Guard will be accepted at the below-cost rate of \$1.50 per year. Subscriptions at this rate (whether ordered by the addressee or a donor) must be accompanied by a remittance in full; addressee's rank and military address must be given. This rate applies wherever domestic U. S. postal service extends, including naval units at sea and overseas army postoffices. No cancellations or refunds.

Simply write rank, name, and military address on a slip of paper and send, accompanied by remittance, to

The Editors of Radio, Stamford, Connecticut

Fujimoto, T., Physics 5, 302 (1934).
 Pitt, A., und Jackson, Canad. J. Res.
 12 (Mai 1935).
 Ny Tsi-Ze, J. Physique Radium 9,
 13 (1928).
 Rayleigh, Theorie of Sound 1, 157
 (1877).
 Giebe, E., und E. Blechschmidt,
 Ann. Physik 18, 417, 457 (1933).
 Lack, F. R., Proc. Inst. Rad. Eng.
 17, 1123 (1929).
 Lonn, E., Ann. Physik 30, 429
 (1937).
 Giebe, E., und A. Scheibe, Tat. Ber.
 d. P.T.R. 1926, 31.
 Giebe, E., und A. Scheibe, Z. Physik
 33, 335 (1925).
 Giebe, E., und A. Scheibe, Z. Physik,
 33, 760 (1925).
 Giebe, E., und A. Scheibe, ETZ. 47,
 380 (1926).
 Giebe, E., und A. Scheibe, Z. Physik
 46, 607 (1928).
 Giebe, E., und A. Scheibe, E.N.T. 5,
 65 (1928).
 Giebe, E., und A. Scheibe, Jb. d. dr.
 T. u. T. 35, 165 (1930).
 Giebe, E., und A. Scheibe, Ann.
 Physik 9, 39 (1931).
 Giebe, E., und A. Scheibe, H.F.
 Techn. u. El. Ak. 41, 83 (1933).
 Bechmann, R., Telefunken-Ztg.
 Heft 63, 17 (1933). E.N.T. 10, 371
 (1933).
 Bechmann, R., Naturwiss. 21, 752
 (1933).
 Bechmann, R., Telefunken - Ztg.
 Heft 68, 16 (1934).

Bechmann, R., H.F. Techn. u. El.
 Ak. 44, 145 (1934).
 Bechmann, R., Z. Physik 91, 670
 (1934).
 Bechmann, R., Z. Techn. Physik 16,
 525 (1935).
 Bechmann, R., Telefunken-Ztg.
 Heft 72, 36 (1936).
 Bechmann, R., Telefunken-Ztg.
 Heft 76, 5 (1937).
 Koga, I., Physics 3, 70 (1932).
 Koga, I., E.N.T., 12, 1 (1935).
 Koga, I., und N. Takagi, J.I.E.E.,
 54, 940 (1933); 55, 399 (1934); 55, 82
 (1934) (Japanisch).
 Koga, I., Rep. Rad. Res. a Works
 Japan 2, 157 (1932).
 Koga, I., Philos. Mag. 16, 275 (1933).
 Meibner, A., Z. Techn. Physik 7,
 585 (1926).
 Meibner, A., E.N.T. 3, 401 (1926).
 Meibner, A. Z. Hochfrequenztechn.
 29, 29 (1927).
 Meibner, A., Physik. Z. 28, 621
 (1927).
 Meibner, A., Naturwiss, 17, 25
 (1929).
 Meibner, A. und R. Bechmann, Z.
 Techn. Physik 9, 439 (1928).
 Meibner, A., Telefunken-Ztg. Heft
 10, 5 (1929).
 Meibner, A., Z. Techn. Physik 8, 74
 (1928).
 Meibner, A., Z. Physik 65, 145
 (1930).
 Wood, A. B., G. A. Tomlinson und
 L. Essen, Proc. Roy. Soc. 158, 606
 (1937).

Plug-in CAPACITORS



- Introduced some time ago in the electrolytic type, Aerovox Plug-in Capacitors are now available in wax- and oil-filled paper types as well. Thus more than ever before, these plug-ins are the logical choice for aircraft, military, police, sound system and other equipment where continuity of service is the prime requisite.

ELECTROLYTIC . . .

Available with plain foil and with etched foil sections. Single, dual, triple and quadruple section units, 25 to 500 v. D.C.W. Corrosion-proof internally and externally. Adequately vented. Octal base fits standard octal socket.

WAX-FILLED . . .

Type 71, a wax-impregnated wax-filled paper capacitor in aluminum casing. Octal base. Single and multiple section units. 200, 400 and 600 v. D.C.W.

OIL-FILLED . . .

Type 72, an oil-impregnated oil-filled paper capacitor in aluminum-sprayed tin-plate container with prong base fitting standard UX socket. Hermetically sealed. Positively leakage proof. In single and multiple section units. 400 and 600 v. D.C.W.

• New CATALOG . . .

Our Transmitting Capacitor Catalog listing these and many other electronic-industrial types available to anyone actively engaged in professional communication or electronic fields. Use business stationery when writing.

AEROVOX
 CORPORATION
 NEW BEDFORD, MASS., U. S. A.
 In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
 EXPORT: 100 Varick St., N. Y., Cable "ARLAB"

TWO IRONS IN THE FIRE

- While endeavoring, first, to be of all possible service in the wartime production emergency, The Astatic Corporation, at the same time is making an earnest effort to supply users, through authorized jobbers, with Astatic replacement parts for existing radio, phonograph and sound equipment. *Shortage of certain materials makes it necessary that all purchases of Astatic Pickup or Microphone Cartridges be accompanied by old cartridges of similar type.*



ASTATIC

SEE YOUR RADIO
PARTS JOBBER

THE ASTATIC CORPORATION

YOUNGSTOWN, OHIO

Licensed Under Brush
Development Co. Patents

In Canada:
Canadian Astatic Ltd.
Toronto, Ontario

RADIO

* JULY, 1942

- Straubel, H., H.F. Techn. u. El. Ak. 38, 14 (1931).
 Straubel, H., Physik. Z. 32, 222 (1931).
 Straubel, H., Physik. Z. 35, 179 (1934).
 Straubel, H., Physik. Z. 35, 657 (1934).
 Straubel, H., Z. Techn. Physik 15, 607 (1934).
 Straubel, H., H.F. Techn. u. El. Ak. 46, 4 (1935).
 Straubel, H., Physik. Z. 34, 894 (1933).
 Scheibe, A. und U. Adelsberger, Tat. Ber. d. P.T.R. 1935, 17.
 Scheibe, A., und U. Adelsberger, Physik. Z. 33, 835 (1933).
 Scheibe, A., und U. Adelsberger, Ann. Physik 18, 1 (1933).
 Scheibe, A., und U. Adelsberger, H.F. Techn. u. El. Ak. 43, 47 (1934).
 Scheibe, A., und U. Adelsberger, Physik. Z. 37, 38 (1936).
 Scheibe, A., und U. Adelsberger, Physik. Z. 37, 185 (1936).
 Scheibe, A., und U. Adelsberger, Physik. Z. 37, 415 (1936).
 Scheibe, A., Naturwiss. 21, 505 (1933).
 Scheibe, A., Erg. exakt. Naturwiss. 15, 262 (1936).
 Adelsberger, U., E.N.T. 12, 83 (1935).
 Harding, J. W., und F. W. G. White, Philos. Mag. 8, 169 (1929).
 Tawil, E. P., C.R. Acad. Sci. 183, 1099 (1926).
 Tawil, E. P., C.R. Acad. Sci. 187, 1042 (1928).
 Tawil, E. P., C.R. Acad. Sci. 199, 1025 (1934).
 Tawil, E. P., C.R. Acad. Sci. 200, 1088 (1935).
 Tawil, E. P., C.R. Acad. Sci. 200, 1306 (1935).
 Strong, J. A., Nature 129, 59 (1932).
 Debye, P., und F. W. Sears, Proc. Nat. Acad. Amer. 18, 409 (1932).
 Lucas, R., und P. Biquard, C.R. Acad. Sci. 195, 121 (1932).
 Lucas, R., und P. Biquard, J. Physique Radium 3, 464 (1932).
 Petrzilka, V., Ann. Physik 15, 881 (1932).
 Gruneisen, E., Ann. Physik 22, 807 (1907).
 Jimbo, S., Proc. Inst. Rad. Eng. 18, 1930 (1930).
 Ny Tsi-Ze und Tsien Ling Chao, Nature 134, 214 (1934).
 Ny Tsi-Ze und Tsien Ling Chao, C.R. Acad. Sci. 198, 1395 (1934).
 Ny Tsi-Ze und Tsien Ling Chao, C.R. Acad. Sci. 199, 1101 (1934).
 Ny Tsi-Ze und Tsien Ling Chao, C.R. Acad. Sci. 200, 565 (1935).
 Ny Tsi-Ze und Tsien Ling Chao, C.R. Acad. Sci. 200, 732 (1935).
 Gibbs, E. R., und Tsien Ling Chao, Philos. Mag. 22, 311 (1936).
 Langevin, P., und J. Salomon, C.R. Acad. Sci. 200, 1257 (1935).
 Essen, L., Proc. Roy. Soc. London (A) 155, 498 (1936).
 Tawil, E. P., C.R. Acad. Sci. 192, 274 (1931).
 Tawil, E. P., C.R. Acad. Sci. 185, 114 (1927).
 Namba, Shogo, und Sadao Matsu-
 mura, Res. Electrot. Lab. Tokyo 1929, H. 248.
 Jungnickel, H., Z. VDI 80, 80 (1936).
 Neumann, F., Vorl. u. d. Theorie d. Elastizitat fester Korper u.d. Lichtes im Ather (Leipzig 1885).
 Christoffel, E. W., Ann. di Mat. 11, 8, 193 (1877).
 Koga, I., Rep. of Rad. Res. i. Jap. 6, 1. (1934).
 Buchs, K., und H. Muller, Z. Physik 84, 75 (1933).
 Schumacher, R. O., Telefunken-Ztg. Nr. 76, 16 (1937).
 Matsumura, S., und S. Kanzaki, Rep. of Rad. Res. i. Jap. 4, 105 (1934).
 Decaux, B., L'Onde Electrique 15, 411, (1936).
 Lucas, H. J., J. Inst. Electr. Eng. 68, 855 (1930).
 Roeschen, E., E.N.T. 13, 187 (1936).
 McIlwraith, Nt. Res. Counc. 29 (1931).
 Love, E. A., A Treatise on the Mathematical Theory of Elasticity (Cambridge 1927).
 Petrzilka, V., Ann. Physik, 23, 156 (1935).
 Petrzilka, V., Z. Physik 97, 436 (1935).
 Lissutin, A., Z. Physik, 59, 265 (1930).
 Lissutin, A., Z. Physik 69, 850 (1931).
 Doerffler, H. Z., Physik 63, 30 (1930).
 Bergmann, L., Ann. Physik 21, 553 (1934).
 Watanabe, Y., E.N.T. 5, 45 (1928).

YOUR REFERENCE BOOK BUYING GUIDE AND MASTER FILE

Gives This Important Data

Contained within the hard covers of this 800-page MASTER BOOK are the listings of the products of 90% of all Radio Parts and Equipment Manufacturers in the industry. In it you will find many thousands of items, such as electronic devices, transmitting and receiving sets, public address equipment, speakers, tubes, antennas, transformers, condensers, replacement parts, meters, laboratory test equipment, relays, plugs, coils, wire, and numerous other radio components. Thousands of clear illustrations with descriptions and specifications. Yes, this is your "MUST HAVE BOOK."


Saves Time—Saves Money

WHERE, WHAT AND HOW MUCH: Such information is instantly at your fingertips. This valuable RADIO MASTER eliminates the maintenance of bulky files. It is completely indexed for speedy reference.

If you buy, sell or specify, you will find the RADIO MASTER an indispensable and handy book to have around at all times.

NINTH EDITION IT'S A MASTERPIECE

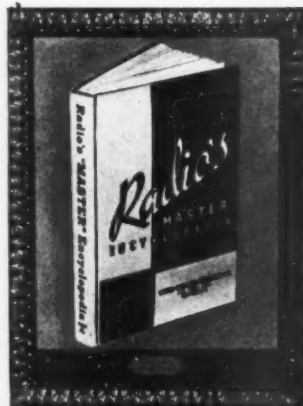Took 6 years and thousands of dollars to develop to its present size—yet it costs you only \$3.50



MONEY BACK GUARANTEE

Order your copy today—look it over. You will find it to be an excellent investment; if not, return it to us in five days for full refund. We prepay transportation charges if remittance accompanies order.


THE ONLY OFFICIAL RADIO & EQUIPMENT MASTER CATALOG

Compiled in co-operation with and approved by the Radio Manufacturers Group as the industry's official source book.

Who Uses It?

Broadcasting Stations
 Department Stores
 Electrical Engineers
 Exporters
 Foreign Governments
 Industrial Plants
 Mail Order Houses
 Mechanical Engineers
 Newspaper Publishers
 Police Departments
 Purchasing Agents
 Radio Distributors
 Radio Service Organizations
 Radio Salesmen and Buyers
 Radio Parts Manufacturers
 Radio Set Manufacturers
 Radio Sales Agents
 Students and Experimenters
 Technical Libraries
 Telephone Companies
 Telegraph Companies
 Universities & Schools
 U.S. Military, Naval
 and Aircraft Depts.

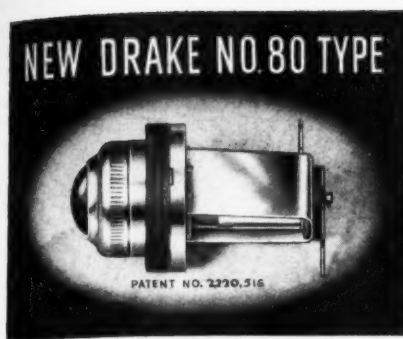UNITED CATALOG PUBLISHERS, Inc.
 106-110 LAFAYETTE STREET, NEW YORK, N. Y., U.S.A.



Polarized JEWEL PILOT LIGHT ASSEMBLY




Now, the brightness of illumination, or colored signal light intensity, can be regulated *instantly*. For, a partial turn of the jewel dims or brightens the light intensity of our new No. 80

Type Assembly! Polarized discs, behind the jewel, arranged to be free to rotate with respect to each other, turn the trick!

HAVE YOU A COPY OF OUR CATALOG? It presents a complete line of standard and special Dial and Jewel Light Assemblies. We supply most of America's leading communications, aircraft and electrical manufacturers.

DRAKE MANUFACTURING CO.
1713 W. HUBBARD ST. • CHICAGO, U. S. A.

MUELLER

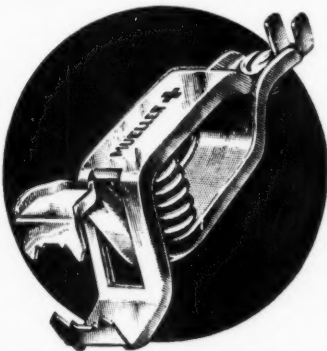

CLIPS

ARE ON THE FIRING LINE
WITH RADIO EVERYWHERE

- Made in 10 sizes—from the tiny wee-pee-wee to the 300 ampere Big Brute
- Offered in both steel and solid copper
- Red and black rubber insulators to fit each size.
- A complete line with

A CLIP FOR EVERY PURPOSE

Send for free samples & catalog 806

Mueller Electric Co.

1565 E. 31st St., Cleveland, Ohio

- Heegner, K., Jb. d. dr. T. u. T. 29, 177 (1927).
Mallet, E., und V. Terry, Wir. World 16, 630 (1925).
Pierce, G. W., Proc. Amer. Acad. Arts Sci. 59, 81 (1923).
Pierce, G. W., Proc. Amer. Acad. Arts Sci. 60, 271 (1925).
Balth, van der Pol, Jb. d. dr. T. U. T. 28, 194 (1926).
Butterworth, Proc. Phys. Soc. 271, 410 (1915).
Van Dyke, K. X., Physic. Rev. 25, 895 (1925).
Guerbilsky, A., J. Physique Radium 8, 165 (1937).
Van Dyke, K. S., und J. P. Hagen, Physic. Rev. 46, 939 (1934).
Van Dyke, K. S., Physic. Rev. 40, 1026 (1932).
Hight, S. C., und Willard, G. W., Proc. Inst. Rad. Eng. 25, 549 (1937).
Gunther, R., H.F. Techn. u. El. Ak. 45, 185 (1935).
Chaikin, S., Jb. d. dr. T. u. T. 35, 6 (1930).
Gockel, H., Physik. Z. 18, 657 (1936).
Boella, M., Proc. Inst. Rad. Eng. 19, 1252 (1931).
Grobmann, E., und M. Wien, Physik. Z. 32, 377 (1931).
Essen, L., Nature 135, 1076 (1935).
V. Handel, P., K. Kruger und H. Plendl, Proc. Inst. Rad. Eng. 18, 307 (1930).
Kautter, W., Telefunken-Ztg. Heft 76, 22 (1937).
Werrmann, H., ETZ, 57, 707, 735 (1936).
Rabanus, W., und S. Rynning-Tonnessen, Europ. Fernsprd. 1935, H. 41.
Lack, F. R., G. W. Willard und I. E. Fair, Bell System. Tech. J., 18, 453 (1934).
Guerbilsky, A., Franz. Patentschr. Nr. 748910.
Zacek, A., und V. Petrzilka, H. F. Techn. u. El. Ak. 46, 157 (1935).
Wagner, K. W., H.F. Tech. u. El. Ak. 47, 28 (1936).
Loomis, A. L., Monthly Not. 91, 569 (1931).
Brown, E. W., und D. Brouwer, Monthly Not. 91, 575 (1931).
Vigoureux, J. E. P., J. Inst. El. Eng. 68, 265 (1930).
Terry, E. M., Proc. Inst. Rad. Eng. 16, 1486 (1928).
Wright, J. W., Proc. Inst. Rad. Eng. 17, 127 (1929).
Heegner, K., E.N.T. 10, 357 (1933).
Handel, P. v., E.N.T., 7, 34 (1930).
Petrzilka, V., und w. Fehr, E.N.T. 9, 283 (1932).
Lapham, E. G., Bur. Stand. J. Res. 11, 59 (1933).
Illgen, H., und H. Hintze, Deutsche Motor-Z. S. 14, Heft 10 (1937).
Clapp, J. K., Rev. Scient. Instr. 3, 106 (1932).
Hall, L. E., V. E. Heaton und E. G. Lapham, Bur. Stand. J. Res. 14, 85 (1935).
Meahl, HLR. Proc. Inst. Rad. Eng. 22, 732 (1934).
Andrew, V. J., Proc. Inst. Rad. Eng. 21, 982 (1933).
Wertli, A., Helv. Phys. Acta 6, 495 (1933).

MAILING LISTS



GET OUR FREE
REFERENCE
BOOK and
MAILING
LIST CATALOG
FREE

Gives counts and prices on accurate guaranteed mailing lists of all classes of business enterprises in the U. S. Wholesalers—Retailers—Manufacturers by classification and state. Also hundreds of selections of individuals such as professional men, auto owners, income lists, etc.

Write today for your copy

R. L. POLK & CO.


Polk Bldg.—Detroit, Mich.

Branches in Principal Cities

World's Largest City Directory Publishers

Mailing List Compilers, Business Statistics, Producers of Direct Mail Advertising.

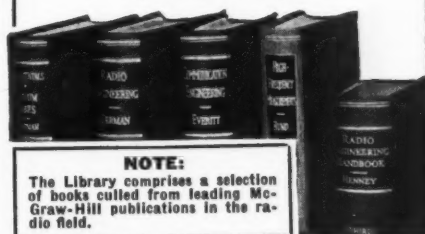NOW—A REALLY HIGH-POWERED— Radio Engineering Library



NOTE:

The Library comprises a selection of books culled from leading McGraw-Hill publications in the radio field.

- especially selected by radio specialists of McGraw-Hill publications
- to give most complete, dependable coverage of facts needed by all whose fields are grounded on radio fundamentals
- available at a special price and terms

THESE books cover circuit phenomena, tube theory, networks, measurements, and other subjects—give specialized treatments of all fields of practical design and application. They are books of recognized position in the literature—books you will refer to and be referred to often. If you are a practical designer, researcher or engineer in any field based on radio, you want these books for the help they give in hundreds of problems throughout the whole field of radio engineering.

5 VOLUMES, 3319 PAGES, 2289 ILLUSTRATIONS

1. Eastman's FUNDAMENTALS OF VACUUM TUBES
2. Terman's RADIO ENGINEERING
3. Everitt's COMMUNICATION ENGINEERING
4. Hund's HIGH FREQUENCY MEASUREMENTS
5. Henney's RADIO ENGINEERING HANDBOOK

10 days' examination. Easy terms. Special price under this offer less than books bought separately. Add these standard works to your library now; pay small monthly installments, while you use the books.

10 DAYS' FREE EXAMINATION—SEND COUPON

McGraw-Hill Book Co., 330 W. 42nd Street, N. Y. C.

Send me Radio Engineering Library, 5 vols., for 10 days' examination on approval. In 10 days I will send \$3.00 plus few cents postage, and \$3.00 monthly till \$24.00 is paid, or return books postpaid. (We pay postage on orders accompanied by remittance of first installment.)

Name


Address

City and State

Position

Company..... R-7-42

QUANTITY DELIVERY NOW

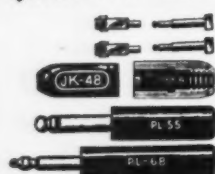

For Govt. contr. and sub-contr. for land, sea and other field communications devices.

Types PL-54, PL-55, PL-68, JK-26, JK-48 and companion plug, and SW-141.

UNIVERSAL MICROPHONE CO., LTD.
Inglewood Calif.



BIG FREE CATALOG

EVERYTHING IN RADIO

Sets, parts, supplies, public address systems, amateur equipment, testers, kits and fluorescent lighting at lowest prices. Huge stocks, bought months ago... ready for shipment the same day your order is received. The Defense Program is making big demands on our industry but because of our advance buying we are able to fill your orders promptly and efficiently.

PACKED WITH VALUES!

BURSTEIN-APPLEBEE COMPANY
1012-14 MCGEE STREET, KANSAS CITY, MISSOURI

Advertising Index

Aerovox Corp.	63
Astatic Corp.	63
Bliley Electric Co.	58
Bud Radio, Inc.	59
Burstein-Applebee Co.	66
Candler System Co.	66
Centralab	6
Drake Electric Co.	65
Eitel-McCollough, Inc.	49
Guardian Electric Co.	54
Hallicrafters, Inc., The	3
Henry Radio Shop	61
Jefferson-Travis Radio Mfg. Co.	IV Cover
Mallory & Co., Inc., P. R.	56
McGraw-Hill Book Co., Inc.	65
Meissner Manufacturing Co.	47
Mueller Electric Co.	65
National Co., Inc.	III Cover
Ohmite Manufacturing Co.	62
Polk & Co., R. L.	65
RADIO Handbook	55
RADIO Publications	57
Raytheon Manufacturing Co.	5
Solar Manufacturing Corp.	53
United Transformer Corp.	II Cover
United Catalog Publishers, Inc.	64
Universal Microphone Co., Ltd.	66
U. S. Treasury Dept.	60
Utah Radio Products Co.	51

Worrall, R. H. und R. B. Owens, Proc. Inst. Rad. Eng. 16, 778 (1928).
Sabaroff, S. Proc. Inst. Rad. Eng. 25, 623 (1937).
Jakobs, H., Lorenz-Berichte, H. 1, 38 (1936).
Schultze-Herringen, E., Lorenz-Berichte, H. 3/4, 39 (1936).
Lorenz-Berichte, H. 1, 17 (1933).
Rayner, E. H., J. Inst. El. Eng. 72, 519 (1933).
Osterberg H., J. Opt. Soc. Amer. 22, 19 (1932).
Osterberg, H., J. Opt. Soc. Amer. 23, 30 (1933).
Osterberg, H., Rev. Scient. Instr. 5, 183 (1934).
Osterberg, H., Physic. Rev. 43, 819 (1933).
Petrzilka V., Ann. Physik 11, 623 (1931).
Petrzilka, V., und L. Zachoval, Z. Physik 90, 700 (1934).
Tawil, E. P., C.R. Acad. Sci. 191, 998 (1930).
Bergmann, L., H.F. Techn. u. El. Ak. 43, 83 (1934).
Eichhorn, K., Z. Techn. Physik 17, 276 (1936).
Laimbock, J., Mitt. Inst. Radiumforsch., (1928), Nr. 221 a.
Seidl, F., Mitt. Inst. Radiumforsch. (1928), Nr. 325.
Seidl, F. und E. Huber, Z. Physik 97, 671 (1935).
Schaefer, C. L., und L. Bergmann, Berliner Ber. (1928), Nr. 11, 155 Nr 13/14, 192.
Schaefer, Cl., und L. Bergmann, Naturwiss. 22, 685 (1934).
Lucas, R., und P. Biquard, C.R. Acad. Sci. 194, 2132 (1932).
Hiedemann, E., und N. Seifen, Z. Physik 91, 413 (1934).
Hiedemann, E., Erg. exakt, Naturwiss., 14, 201 (1935).
Hiedemann, E., H. R. Asbach und K. H. Hoesch, Z. Physik 90, 322 (1934).
Barrett, C. S., und C. E. Howe, Physic. Rev. 38, 2290 (1931).
Cork, J. M., Physic. Rev. 41, 391 (1932).
Cork, J. M., Physic. Rev. 42, 749 (1932).
Fox, G. W., und W. A. Fraser, Physic. Rev. 37, 1622 (1931).
Fox, G. W., und W. A. Fraser, Physic. Rev. 47, 200 (1935).
Bleichschmidt, E., und W. Boas, Z. Kristallogr. 85, 329, 478 (1933).
Klauser, F., Physik. Z. 36, 208 (1935).
Jauncey, G. E. M., und J. H. Deming, Physic. Rev. 48, 462 (1935).
Langevin, M. P., Spec. Publ. Bureau Hydrogr. Intern. Monaco (1924) Nr. 3.
Sokoloff, X., E.N.T. 6, 454 (1929).
Florisson, C., Bull. Soc. Belg. Electr. 1-3 (1936).
Gruetzmacher, J., Z. Physik 96, 342 (1935).
Gruetzmacher, J., Z. Techn. Physik 17, 166 (1936).
Wood, R. W., und A. L. Loomis, Physik 17, 166 (1936).
Freundlich, H., K. Sollner und F. Rogowski, Kolloid-Beih. 37, 223 (1933).

Freundlich, H., K. Sollner und F. Rogowski, Flin. Wschr. 11, 1512 (1932).
Boyle, R. W., Sci. Progress 23, 75 (1928).
Claus, B., Z. Techn. Physik 16, 202 (1935).
Hehigans, F. W., Ann. Physik 86, 587 (1928).
Kuntze, A., Ann. Physik 26, 349 (1936).
Abello, T. P., Physic. Rev. 31, 1083 (1928).
Wood, A. B., Philos. Mag. 50, 631 (1925).
Balamuth, L., Physic. Rev. 45, 714 (1934).
Field, G. S., Canad. J. Res. 8, 563, (1933).
Cillerier, J. F., C. R. Acad. Sci. 190, 45 (1930).
Kruger, f., Ann. Physik 26, 167 (1936).
Gruetzmacher, J. Arch. Elektro-techn. 30, 122 (1936).
Illgen, H., Z. Nitrocellulose, Okto-berheft (1937).
Theilacker, W., A. f. Krist. 90, 51 (1935).
Kalb, G., Z. f. Krist. 90, 163, (1935).
Gunther, R., H. F. Tech. u. El. ak. 50, 200 (1937).
Herrmann, H., und O. Meiber, Z. Geophysik 11, 152 (1935).
Schneider, W., Z. Physik 51, 263 (1928); er fand positiv: Isohydrobenzoin C₁₄ H₁₄ O₂, Rebidiumsaratrat Rb₂C₄H₆O₆, Bernsteinsaureanhydrid C₄H₆O₃, Phthalsaeureanhydrid C₈H₆O₃, Azetamid C₂H₅ON.
Greenwood, G., und D. Tambouliau, Z. Krist. 81, 30 (1932) sie fanden positiv: Strontium-Chlorate Sr(CIO₃)₂, p-Chlorazetanilide C₆H₄Cl.NH(CH₂CO), Cinchonine C₂₀H₂₀ON₂. Lead antimonyl tartrate Pb(SbO)₂(C₄H₄O₆)₂. 4 H₂O, Chalcopyrite CuFeS₂; ferner 4C₄H₄O₆(SbO)K. NaCl; sie fanden negativ: Scolicite Si₂O₁₀Al₂Ca. 3 H₂O.
Rontegen, W.C., Wied. Ann. 39, 16 (1890).
Scheibe, A., und E. v. Ferroni, Tat. Ber. PTR 1937 in Physik Z. 1938.

THIS IS YOUR CHANCE!

★ YOU may never have another chance to step into a real paying position where opportunity is unlimited... RADIO CODE OPERATORS are wanted right now!... The Army, Navy and our Merchant Marine need trained operators; you can train for one of these positions now!—right in your own home—by the Candler System. Thousands of code operators have been trained by the Candler System during the past quarter of a century. Today you, too, can learn by using this easy, practical system. Courses for beginners and operators wishing maximum code proficiency. It's up to you—if you want a real future send a post card or letter today—no salesman will call.

Get a FREE Book

Write today and get the free BOOK OF FACTS. Tells you all the facts about being a Radio Code Operator—your copy is waiting for you, send for it today! There's no obligation.

CANDLER SYSTEM CO.

Box 928
Dept. R-7 Denver, Colo.





DOING A JOB



NATIONAL COMPANY, INC.

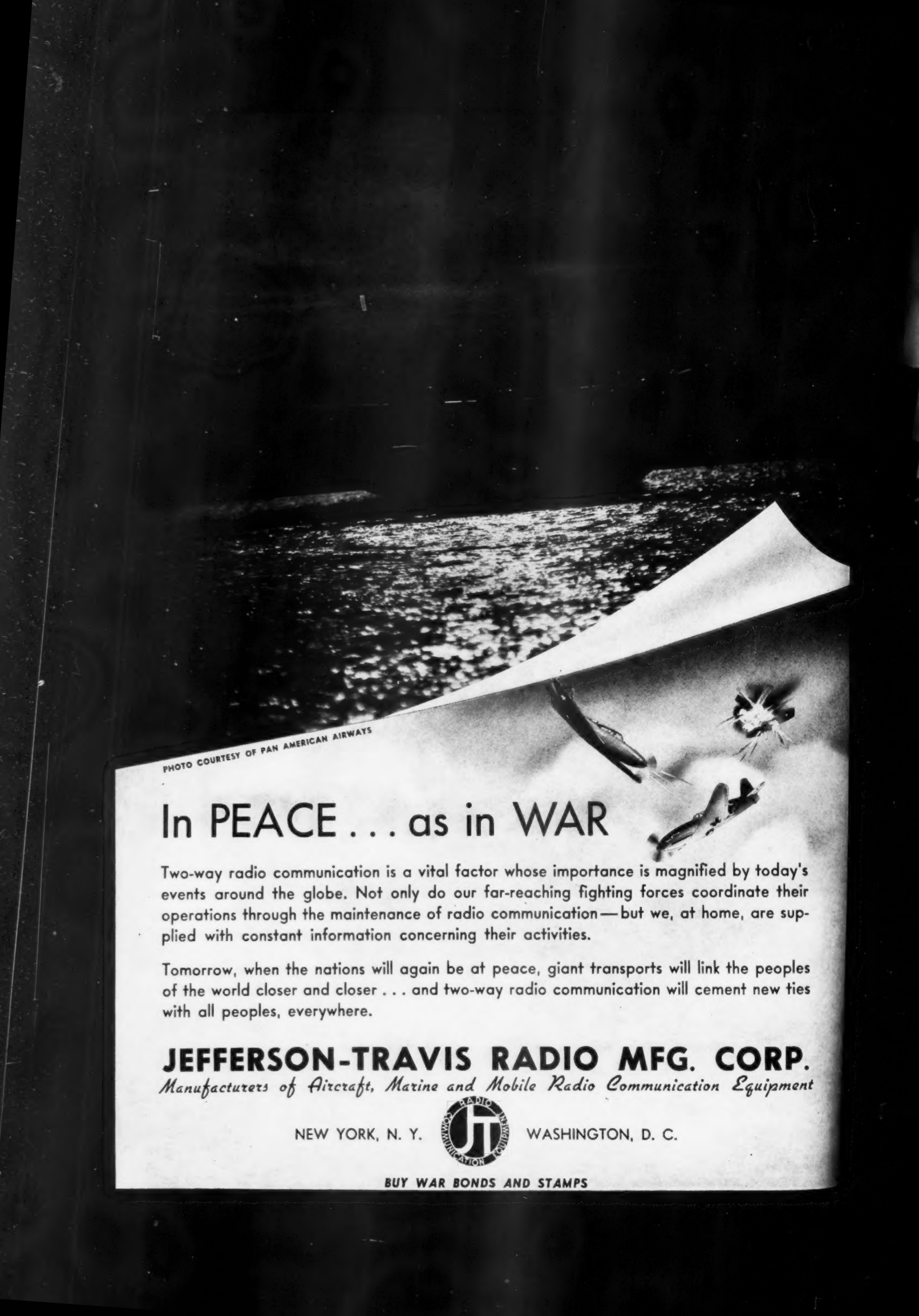


PHOTO COURTESY OF PAN AMERICAN AIRWAYS

In PEACE . . . as in WAR

Two-way radio communication is a vital factor whose importance is magnified by today's events around the globe. Not only do our far-reaching fighting forces coordinate their operations through the maintenance of radio communication—but we, at home, are supplied with constant information concerning their activities.

Tomorrow, when the nations will again be at peace, giant transports will link the peoples of the world closer and closer . . . and two-way radio communication will cement new ties with all peoples, everywhere.

JEFFERSON-TRAVIS RADIO MFG. CORP.

Manufacturers of Aircraft, Marine and Mobile Radio Communication Equipment

NEW YORK, N. Y.



WASHINGTON, D. C.

BUY WAR BONDS AND STAMPS